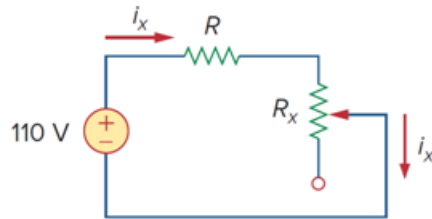


Problem

The potentiometer (adjustable resistor) R_x in Fig. 2.126 is to be designed to adjust current i_x from 10 mA to 1 A. Calculate the values of R and R_x to achieve this.

Figure 2.126:



Step-by-step solution

Step 1 of 2

Refer to Figure 2.126 in the textbook.

The design constraint of the potentiometer is that the current i_x should be in the range from 10 mA to 1 A.

For the current i_x to be maximum (1 A), the potentiometer should be at its minimum resistance, that is, zero.

Now the resistance in the circuit is R .

The current through the circuit, i_x is equal to the current through the resistance, R . Thus,

$$\frac{110}{R} = i_x$$

$$\frac{110}{R} = 1$$

$$R = \frac{110}{1}$$

$$R = 110 \, \Omega$$

Therefore, the value of resistance R is $110 \, \Omega$.

Step 2 of 2

For the current i_x to be minimum (10 mA), the potentiometer should be at its maximum resistance, that is, R_x .

Now, the resistance in the circuit is $R + R_x$.

The current through the circuit, i_x is equal to the current through the resistance, $R + R_x$.

Thus,

$$\frac{110}{R + R_x} = i_x$$

$$\frac{110}{R + R_x} = 10 \times 10^{-3}$$

Substitute 110Ω for R .

$$\frac{110}{110 + R_x} = 0.01$$

$$110 = 1.1 + 0.01R_x$$

$$0.01R_x = 108.9$$

$$R_x = 10.89 \text{ k}\Omega$$

Therefore, the value of resistance R_x is $10.89 \text{ k}\Omega$.