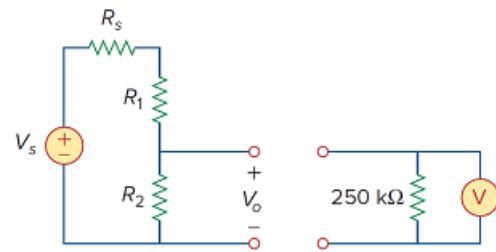


Problem

A voltmeter is used to measure V_o in the circuit in Fig. 2.129. The voltmeter model consists of an ideal voltmeter in parallel with a $250\text{-k}\Omega$ resistor. Let $V_s = 95\text{ V}$, $R_s = 25\text{ k}\Omega$, and $R_1 = 40\text{ k}\Omega$. Calculate V_o with and without the voltmeter when

- (a) $R_2 = 5\text{ k}\Omega$
- (b) $R_2 = 25\text{ k}\Omega$
- (c) $R_2 = 250\text{ k}\Omega$

Figure 2.129:



Step-by-step solution

Step 1 of 8

Refer to Figure 2.129 in the textbook.

Draw the circuit diagram by combining both the circuits.

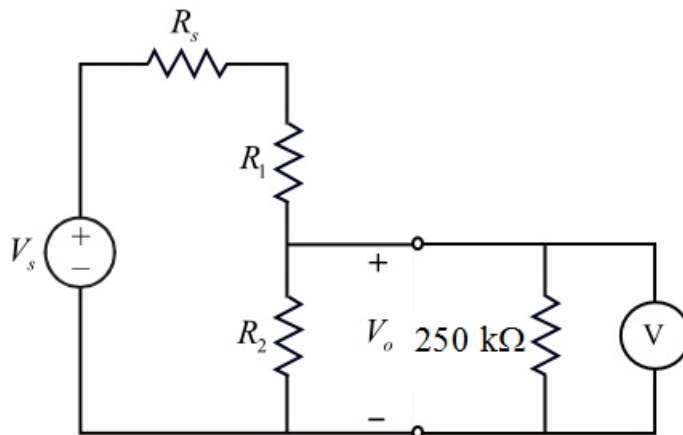


Figure 1

From the Figure 1, calculate the voltage V_o using voltage divider rule.

$$V_o = (V_s) \left(\frac{(R_2 \parallel R_m)}{R_s + R_1 + (R_2 \parallel R_m)} \right) \dots\dots (1)$$

Step 2 of 8

Consider the following circuit diagram without voltmeter.

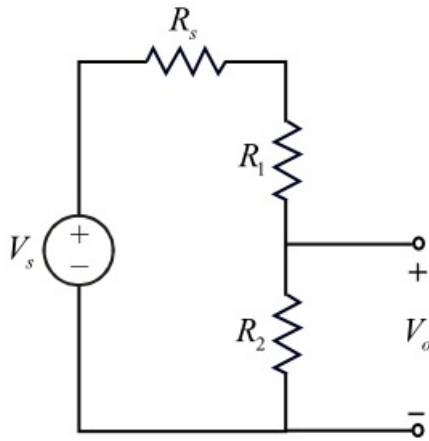


Figure 2

From the Figure 2, calculate the voltage V_o using voltage divider rule.

$$V_o = (V_s) \left(\frac{R_2}{R_s + R_1 + R_2} \right) \dots\dots (2)$$

Step 3 of 8

(a)

Consider the following data:

The value of resistor, $R_2 = 5 \text{ k}\Omega$

Calculate the voltage V_o with the voltmeter when $R_2 = 5 \text{ k}\Omega$ using equation (1).

$$\begin{aligned} V_o &= (95) \left(\frac{(5\text{k} \parallel 250\text{k})}{25\text{k} + 40\text{k} + (5\text{k} \parallel 250\text{k})} \right) \\ &= (95) \left(\frac{\frac{(5\text{k})(250\text{k})}{5\text{k} + 250\text{k}}}{65\text{k} + \left(\frac{(5\text{k})(250\text{k})}{5\text{k} + 250\text{k}} \right)} \right) \\ &= (95) \left(\frac{4.9\text{k}}{65\text{k} + 4.9\text{k}} \right) \\ &= 6.66 \text{ V} \end{aligned}$$

Therefore, the voltage V_o with the voltmeter when $R_2 = 1 \text{ k}\Omega$ is 6.66 V.

Step 4 of 8

Calculate the voltage V_o without voltmeter when $R_2 = 5 \text{ k}\Omega$ using equation (2).

$$\begin{aligned} V_o &= (95) \left(\frac{5\text{k}}{25\text{k} + 40\text{k} + 5\text{k}} \right) \\ &= (95) \left(\frac{5\text{k}}{70\text{k}} \right) \\ &= 6.786 \text{ V} \end{aligned}$$

Therefore, the voltage V_o without voltmeter when $R_2 = 5 \text{ k}\Omega$ is 6.786 V.

Step 5 of 8

(b)

Calculate the voltage V_o with the voltmeter when $R_2 = 25 \text{ k}\Omega$ using equation (1).

$$\begin{aligned} V_o &= (95) \left(\frac{(25\text{k} \parallel 250\text{k})}{25\text{k} + 40\text{k} + (25\text{k} \parallel 250\text{k})} \right) \\ &= (95) \left(\frac{\frac{(25\text{k})(250\text{k})}{25\text{k} + 250\text{k}}}{65\text{k} + \left(\frac{(25\text{k})(250\text{k})}{25\text{k} + 250\text{k}} \right)} \right) \\ &= (95) \left(\frac{22.73\text{k}}{65\text{k} + 22.73\text{k}} \right) \\ &= 24.61 \text{ V} \end{aligned}$$

Therefore, the voltage V_o with the voltmeter when $R_2 = 25 \text{ k}\Omega$ is 24.61 V.

Step 6 of 8

Calculate the voltage V_o without voltmeter when $R_2 = 25 \text{ k}\Omega$ using equation (2).

$$\begin{aligned} V_o &= (95) \left(\frac{25\text{k}}{25\text{k} + 40\text{k} + 25\text{k}} \right) \\ &= (95) \left(\frac{25\text{k}}{90\text{k}} \right) \\ &= 26.39 \text{ V} \end{aligned}$$

Therefore, the voltage V_o without voltmeter when $R_2 = 25 \text{ k}\Omega$ is 26.39 V.

Step 7 of 8

(c)

Calculate the voltage V_o with the voltmeter when $R_2 = 250 \text{ k}\Omega$ using equation (1).

$$\begin{aligned} V_o &= (95) \left(\frac{(250\text{k} \parallel 250\text{k})}{25\text{k} + 40\text{k} + (250\text{k} \parallel 250\text{k})} \right) \\ &= (95) \left(\frac{\frac{(250\text{k})(250\text{k})}{250\text{k} + 250\text{k}}}{65\text{k} + \left(\frac{(250\text{k})(250\text{k})}{250\text{k} + 250\text{k}} \right)} \right) \\ &= (95) \left(\frac{125\text{k}}{65\text{k} + 125\text{k}} \right) \\ &= 62.5 \text{ V} \end{aligned}$$

Therefore, the voltage V_o with the voltmeter when $R_2 = 250 \text{ k}\Omega$ is 62.5 V.

Step 8 of 8

Calculate the voltage V_o without voltmeter when $R_2 = 250 \text{ k}\Omega$ using equation (2).

$$\begin{aligned} V_o &= (95) \left(\frac{250\text{k}}{25\text{k} + 40\text{k} + 250\text{k}} \right) \\ &= (95) \left(\frac{250\text{k}}{315\text{k}} \right) \\ &= 75.4 \text{ V} \end{aligned}$$

Therefore, the voltage V_o without voltmeter when $R_2 = 250 \text{ k}\Omega$ is 75.4 V.

