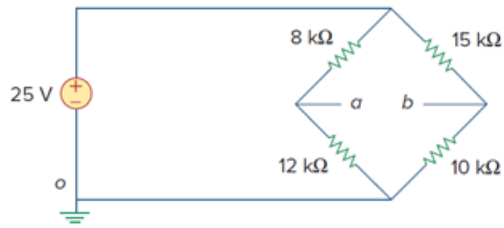


Problem

(a) Consider the Wheatstone bridge shown in Fig. 2.130. Calculate v_a , v_b , and v_{ab} .

(b) Rework part (a) if the ground is placed at a instead of o .

Figure 2.130



Step-by-step solution

Step 1 of 6

(a)

Consider the following circuit diagram:

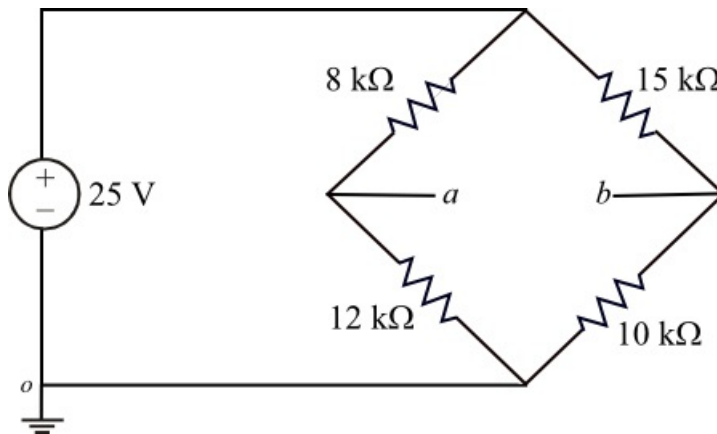


Figure 1

Step 2 of 6

Apply Kirchhoff's current law node a .

$$\frac{v_a - 25}{8 \times 10^3} + \frac{v_a}{12 \times 10^3} = 0$$

$$\frac{3v_a - 75 + 2v_a}{24 \times 10^3} = 0$$

$$5v_a - 75 = 0$$

$$v_a = 15 \text{ V}$$

Therefore, the voltage at node ' a ', v_a is 15 V.

Step 3 of 6

Apply Kirchhoff's current law node b .

$$\frac{v_b - 25}{15 \times 10^3} + \frac{v_b}{10 \times 10^3} = 0$$

$$\frac{2v_b - 50 + 3v_b}{30 \times 10^3} = 0$$

$$5v_b - 50 = 0$$

$$v_b = 10 \text{ V}$$

Therefore, the voltage at node ' b ', v_b is 10 V.

Calculate the voltage between node a and b .

$$v_{ab} = v_a - v_b$$

$$= 15 - 10$$

$$= 5 \text{ V}$$

Therefore, the voltage between node a and b , v_{ab} is 5 V.

Step 4 of 6

(b)

Consider the following circuit diagram with interchange ground from o to a .

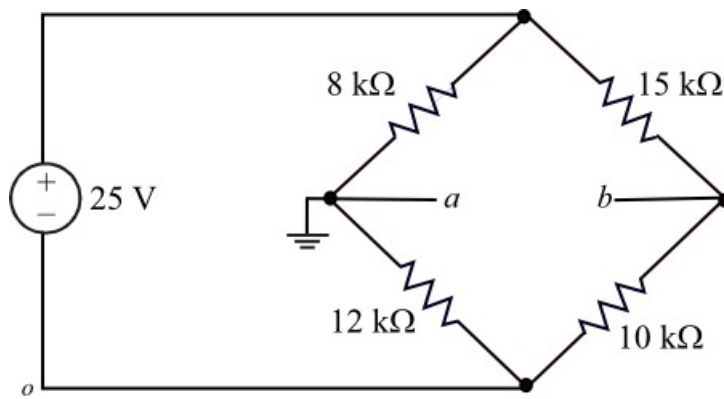


Figure 2

Step 5 of 6

From the Figure 2, it is clear that, the voltage at node ' a ' is zero.

That is, $v_a = 0$.

Apply Kirchhoff's current law node b in Figure 2.

$$\frac{v_b - 25}{15 \times 10^3} + \frac{v_b - (-25)}{10 \times 10^3} = 0$$

$$\frac{2v_b - 50 + 3v_b + 75}{30 \times 10^3} = 0$$

$$5v_b + 25 = 0$$

$$v_b = -5 \text{ V}$$

Therefore, the voltage at node ' b ', v_b is -5 V.

Step 6 of 6

Calculate the voltage between node a and b .

$$\begin{aligned}v_{ab} &= v_a - v_b \\&= 0 - (-5) \\&= 5 \text{ V}\end{aligned}$$

Therefore, the voltage between node a and b , v_{ab} is 5 V.