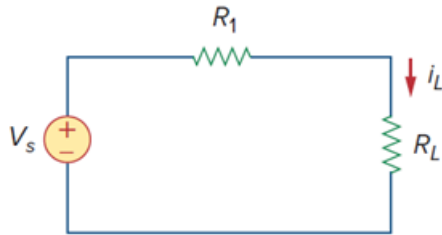


Chapter 2, Problem 71P

Problem

Figure 2.131 represents a model of a solar photovoltaic panel. Given that $V_s = 95\text{ V}$, $R_1 = 25\text{ }\Omega$, and $i_L = 2\text{ A}$, find R_L .

Figure 2.131:



Step-by-step solution

Step 1 of 2

Consider the circuit of textbook Figure 2.131.

It is given that $V_s = 95\text{ V}$, $R_1 = 25\text{ }\Omega$ and $i_L = 2\text{ A}$.

Apply Kirchhoff's voltage law to the circuit.

$$-V_s + i_L R_1 + i_L R_L = 0$$

$$V_s = i_L R_1 + i_L R_L$$

Step 2 of 2

Substitute 95 V for V_s , $25\text{ }\Omega$ for R_1 and 2 A for i_L .

$$95 = (2)(25) + 2R_L$$

$$2R_L = 95 - 50$$

$$2R_L = 45$$

$$R_L = 22.5\text{ }\Omega$$

Therefore, the value of unknown resistance R_L is $\boxed{22.5\text{ }\Omega}$.