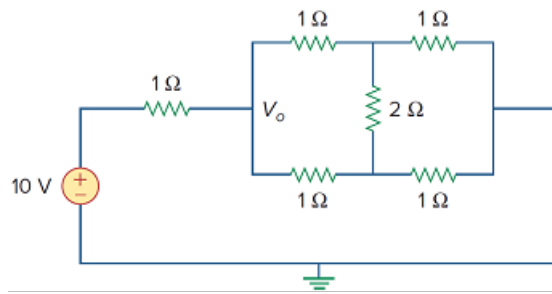


Problem

Find V_o in the two-way power divider circuit in Fig. 2.132.

Figure 2.132:



Step-by-step solution

Step 1 of 7

(a)

Consider the following circuit diagram:

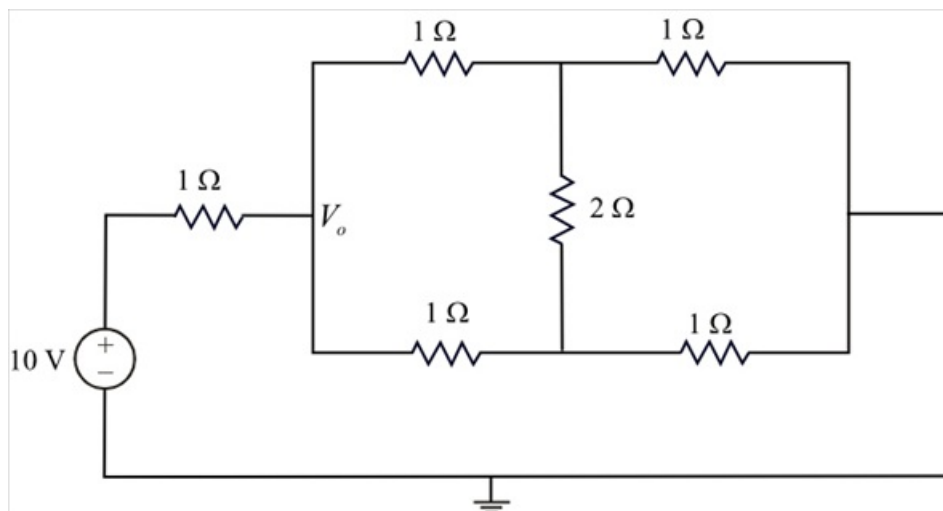


Figure 1

Step 2 of 7

Convert the delta sub network in wye network.

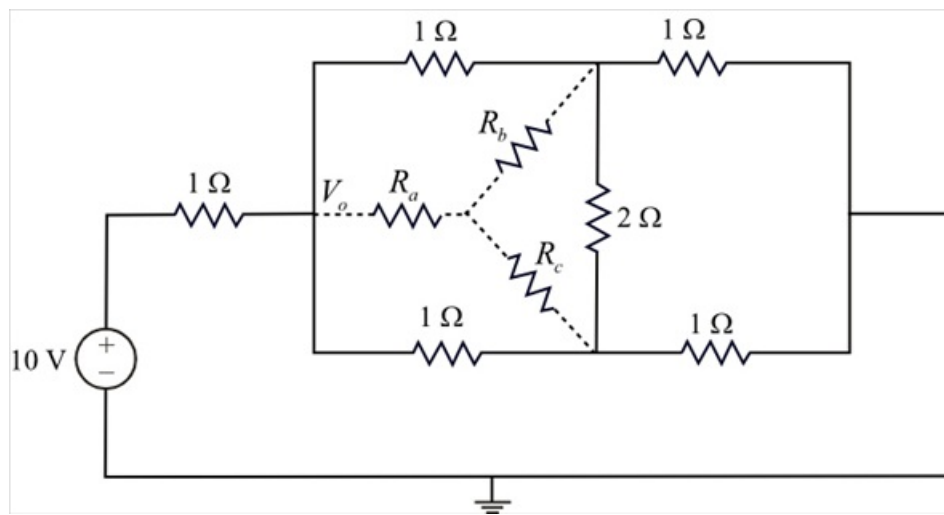


Figure 2

Step 3 of 7

Calculate the star connected resistances.

$$R_a = \frac{(1)(1)}{1+1+2}$$

$$= \frac{1}{4} \Omega$$

$$R_b = \frac{(1)(2)}{1+1+2}$$

$$= \frac{2}{4}$$

$$= \frac{1}{2} \Omega$$

$$R_c = \frac{(1)(2)}{1+1+2}$$

$$= \frac{2}{4}$$

$$= \frac{1}{2} \Omega$$

Step 4 of 7

Consider the modified circuit of Figure 1:

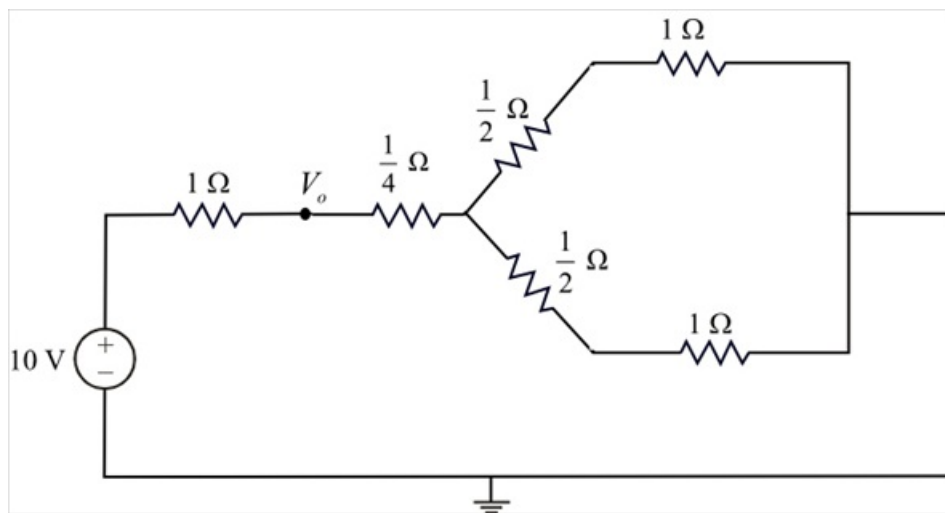


Figure 3

In the Figure 3, the resistors $\frac{1}{2}\Omega$ and 1Ω are connected in parallel series. Therefore, the resultant equivalent resistance is,

$$\frac{1}{2} + 1 = \frac{3}{2}\Omega$$

Draw the reduced circuit of Figure 3.

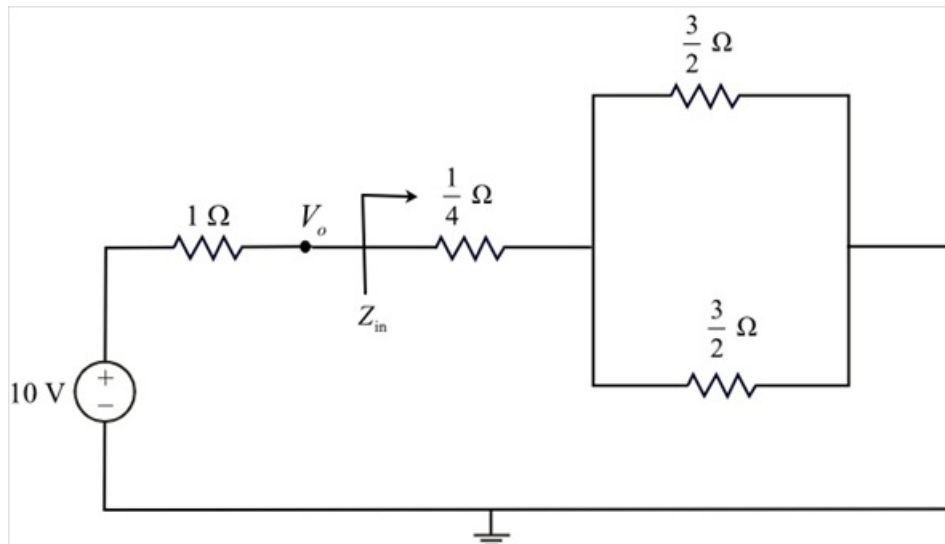


Figure 4

Step 5 of 7

Calculate the impedance Z_{in} in Figure 4.

$$\begin{aligned} Z_{in} &= \left(\frac{3}{2} \parallel \frac{3}{2} \right) + \frac{1}{4} \\ &= \left(\frac{\left(\frac{3}{2} \right) \left(\frac{3}{2} \right)}{\frac{3}{2} + \frac{3}{2}} \right) + \frac{1}{4} \\ &= \frac{3}{4} + \frac{1}{4} \\ &= 1\Omega \end{aligned}$$

Step 6 of 7

Draw the reduced circuit of Figure 4.

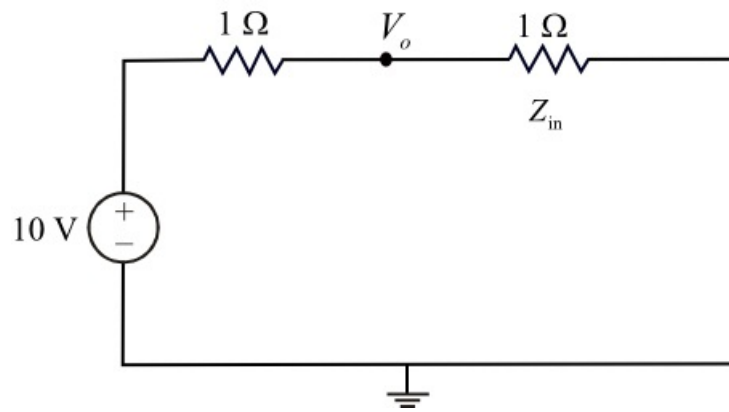


Figure 5

Step 7 of 7

Calculate the voltage V_o in Figure 5 using voltage divider rule.

$$\begin{aligned} V_o &= (10) \left(\frac{1}{1+1} \right) \\ &= (10) \left(\frac{1}{2} \right) \\ &= 5\text{ V} \end{aligned}$$

Therefore, the voltage V_o is 5 V.