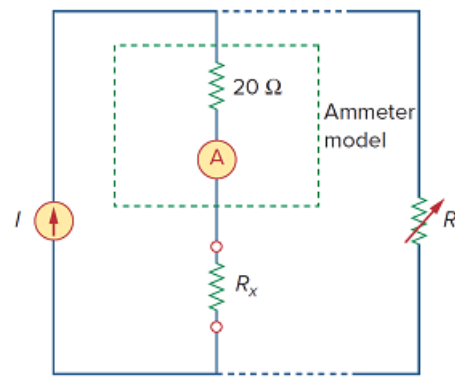


## Problem

An ammeter model consists of an ideal ammeter in series with a  $20\text{-}\Omega$  resistor. It is connected with a current source and an unknown resistor  $R_x$  as shown in Fig. 2.133. The ammeter reading is noted. When a potentiometer  $R$  is added and adjusted until the ammeter reading drops to one half its previous reading, then  $R = 65\text{ }\Omega$ . What is the value of  $R_x$ ?

Figure 2.133:



## Step-by-step solution

## Step 1 of 2

Consider the following circuit diagram:

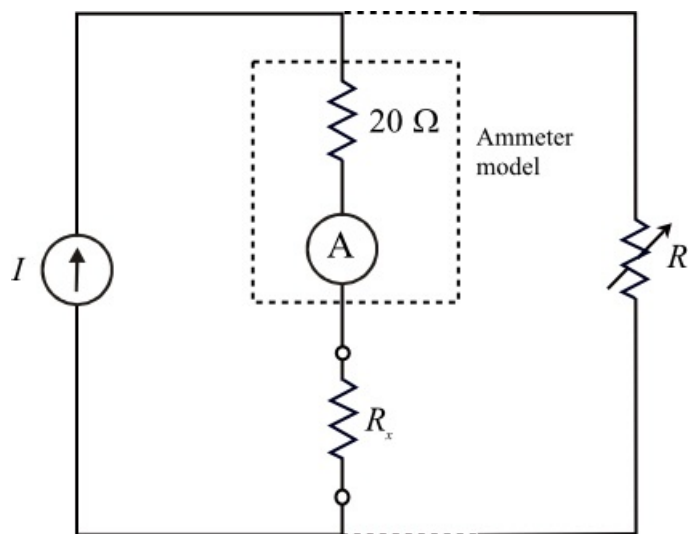


Figure 1

## Step 2 of 2

Consider the following data:

Potentiometer value is,  $R = 65 \Omega$

Ammeter reading without potentiometer is  $I$ .

After adding the potentiometer, the ammeter reading is one half its previous value.

That is,  $\frac{I}{2}$ .

From the above statement, it is clear that the current flowing through ammeter and potentiometer is same.

Write current expressions using current divider rule.

$$I \left( \frac{20 + R_x}{20 + R_x + R} \right) = I \left( \frac{R}{20 + R_x + R} \right)$$

$$\frac{20 + R_x}{20 + R_x + R} = \frac{R}{20 + R_x + R}$$

$$20 + R_x = R$$

$$R_x = R - 20$$

$$= 65 - 20$$

$$= 45 \Omega$$

Therefore, the value of  $R_x$  is  $\boxed{45 \Omega}$ .