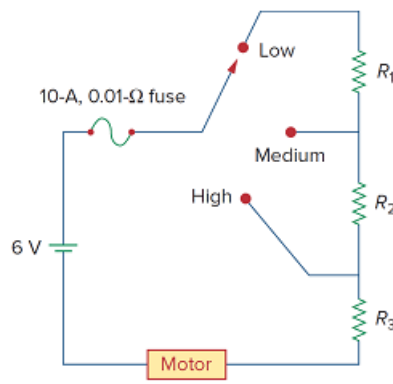


Problem

The circuit in Fig. 2.134 is to control the speed of a motor such that the motor draws currents 5 A, 3 A, and 1 A when the switch is at high, medium, and low positions, respectively. The motor can be modeled as a load resistance of $20\text{ m}\Omega$. Determine the series dropping resistances R_1 , R_2 , and R_3 .

Figure 2.134:



Step-by-step solution

Step 1 of 8

Consider the following circuit diagram:

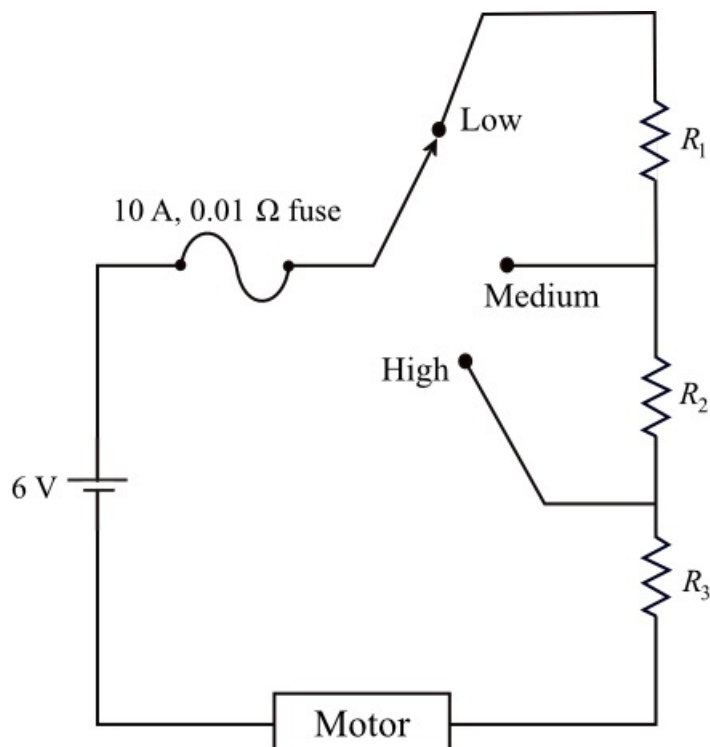


Figure 1

Step 2 of 8

Consider the following data:

Current drawn by the motor when switch is at high position, $I_{\text{high}} = 5 \text{ A}$

Current drawn by the motor when switch is at medium position, $I_{\text{medium}} = 3 \text{ A}$

Current drawn by the motor when switch is at low position, $I_{\text{low}} = 1 \text{ A}$

Load resistance of the motor, $R_L = 20 \text{ m}\Omega$

Fuse resistance, $R_{\text{fuse}} = 0.01 \Omega$

Step 3 of 8

Draw the circuit diagram, when switch is at high position.

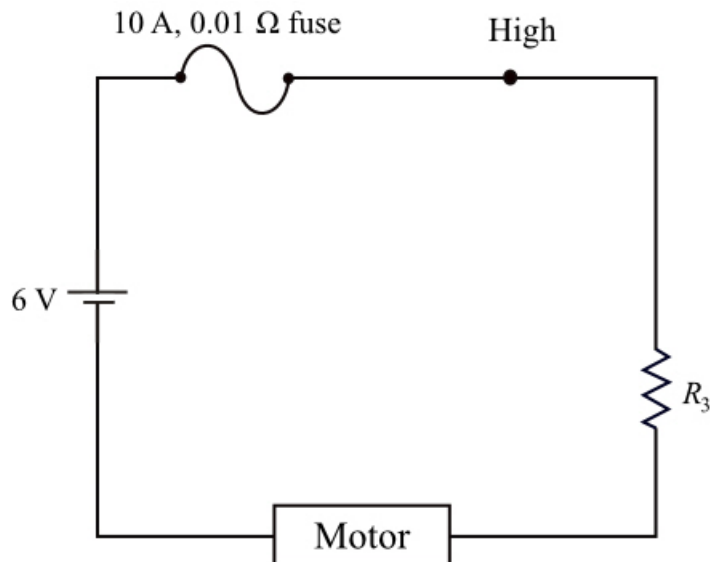


Figure 2

Step 4 of 8

Apply Kirchhoff's voltage law to loop in Figure 2.

$$-6 + (0.01 + R_3 + 20 \times 10^{-3}) I_{\text{high}} = 0$$

$$(0.01 + R_3 + 0.02)(5) = 6$$

$$(0.03 + R_3)(5) = 6$$

$$0.03 + R_3 = 1.2$$

$$R_3 = 1.17 \Omega$$

Therefore, the series dropping resistance, R_3 is 1.17Ω .

Step 5 of 8

Draw the circuit diagram, when switch is at medium position.

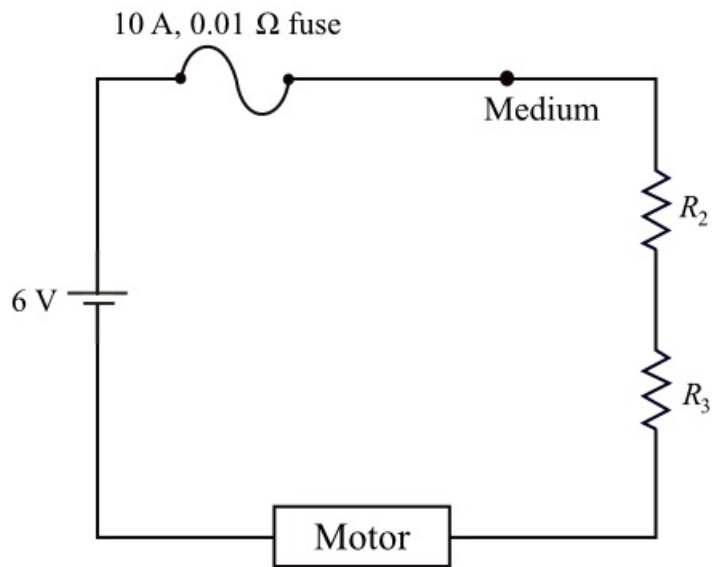


Figure 3

Step 6 of 8

Apply Kirchhoff's voltage law to loop in Figure 3.

$$-6 + (0.01 + R_3 + R_2 + 20 \times 10^{-3}) I_{\text{medium}} = 0$$

$$(0.01 + 1.17 + R_2 + 0.02)(3) = 6$$

$$(1.2 + R_2)(3) = 6$$

$$1.2 + R_2 = 2$$

$$R_2 = 0.8 \, \Omega$$

Therefore, the series dropping resistance, R_2 is .

Step 7 of 8

Draw the circuit diagram, when switch is at low position.

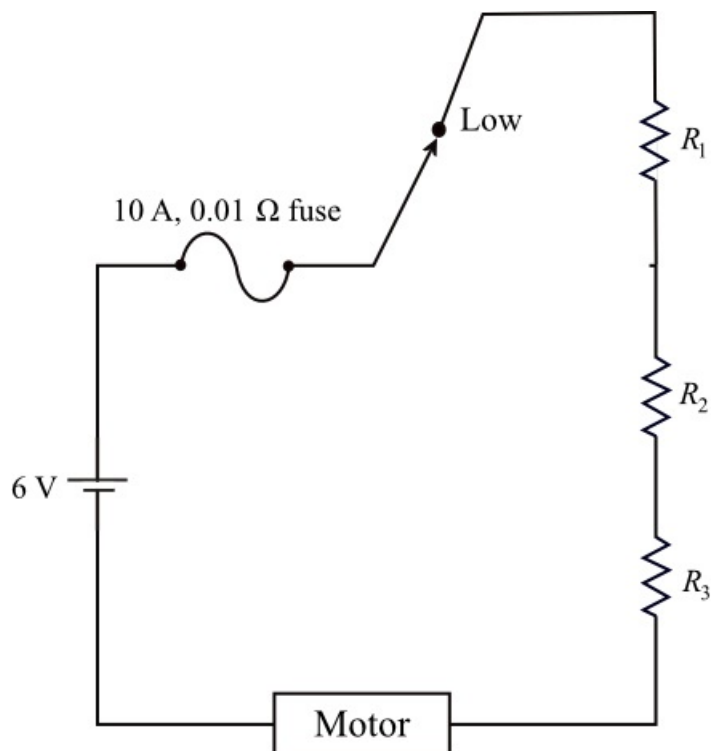


Figure 4

Step 8 of 8

Apply Kirchhoff's voltage law to loop in Figure 4.

$$-6 + (0.01 + R_3 + R_2 + R_1 + 20 \times 10^{-3}) I_{low} = 0$$

$$(0.01 + 1.17 + 0.8 + R_1 + 0.02)(1) = 6$$

$$(2 + R_1)(1) = 6$$

$$2 + R_1 = 6$$

$$R_1 = 4 \Omega$$

Therefore, the series dropping resistance, R_1 is 4Ω .