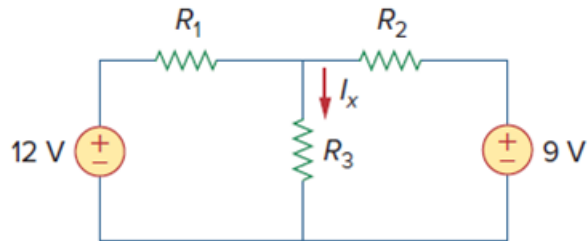


Problem

Using Fig. 3.50, design a problem to help other students better understand nodal analysis.


Figure 3.50:



Step-by-step solution

Step 1 of 3

Given circuit is

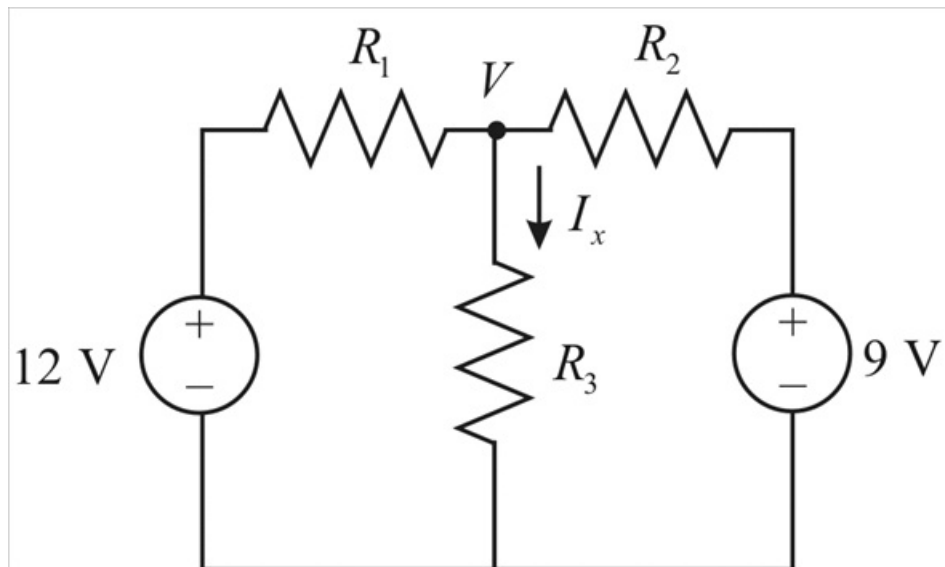

Step 2 of 3

By nodal analysis's we have the equation

$$\frac{V-12}{R_1} + \frac{V}{R_3} + \frac{V-9}{R_2} = 0 \quad \dots\dots (1)$$

From the circuit we have $I_x = \frac{V}{R_3} \quad \dots\dots (2)$

Solving the equation (1)

$$\frac{R_2 R_3 (V-12) + R_1 R_2 V + R_1 R_3 (V-9)}{R_1 R_2 R_3} = 0$$

$$R_2 R_3 V - 12 R_2 R_3 + R_1 R_2 V + R_1 R_3 V - 9 R_1 R_3 = 0$$

$$V (R_2 R_3 + R_1 R_2 + R_1 R_3) = 9 R_1 R_3 + 12 R_2 R_3$$

Step 3 of 3

$$V = \frac{9R_1R_3 + 12R_2R_3}{R_2R_3 + R_1R_2 + R_1R_3}$$

$$V = \frac{3R_3(3R_1 + 4R_2)}{R_2R_3 + R_1R_2 + R_1R_3}$$

From (2) we have $I_x = \frac{V}{R_3}$

Then $I_x = \frac{3(3R_1R_3 + 4R_2R_3)}{R_3(R_2R_3 + R_1R_2 + R_1R_3)}$