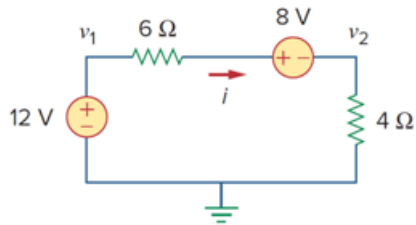


Problem

In the circuit of Fig. 3.47, the voltage v_2 is:

- (a) -8 V
- (b) -1.6 V
- (c) 1.6 V
- (d) 8 V

Figure 3.47




Step-by-step solution

Step 1 of 3

Answer: (c)

Given circuit diagram

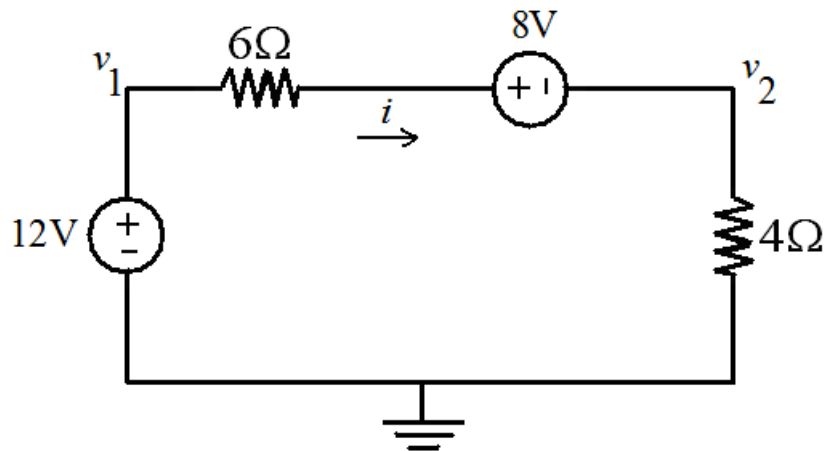

Step 2 of 3

From the circuit by using KVL we can write

$$-12 + 6i + 8 + 4i = 0$$

$$10i = 4$$

$$i = \frac{4}{10}$$

$$i = 0.4\text{ A}$$

Step 3 of 3

Voltage $v_2 = 4i$

$$v_2 = 4(0.4)$$

$$v_2 = 1.6\text{V}$$