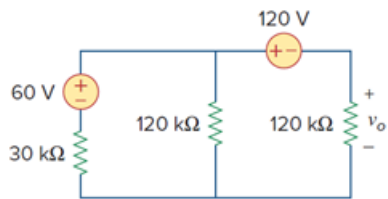


Problem

Obtain v_o in the circuit of Fig. 3.54.


Figure 3.54:



Step-by-step solution

Step 1 of 4

Refer to Figure 3.54 in the text book.

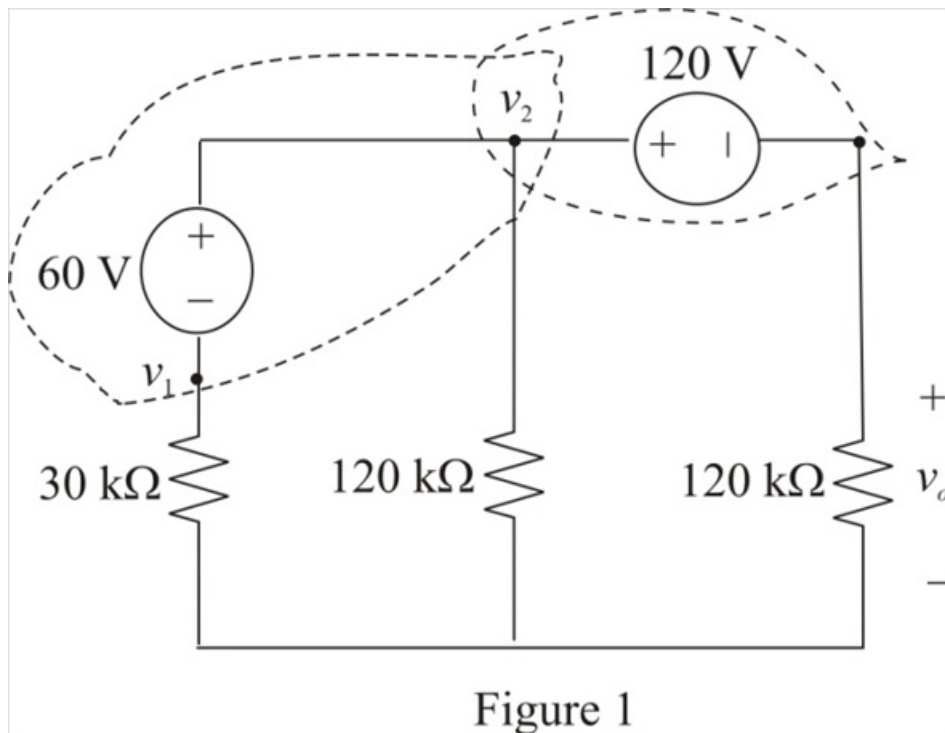

[Comments \(3\)](#)



Anonymous

Why were these nodes chosen?



Anonymous

^^^



Anonymous

Why are the nodes placed there?

Step 2 of 4

Consider the relation between the voltages v_o and v_2 .

$$v_2 - v_o = 120$$

$$v_2 = 120 + v_o$$

Therefore, the expression for the voltage v_2 is, $120 + v_o$.

Step 3 of 4

Consider the relation between the voltages v_1 and v_2 .

$$v_2 - v_1 = 60$$

$$v_1 = v_2 - 60$$

Substitute $120 + v_o$ for v_2 in the equation.

$$v_1 = 120 + v_o - 60$$

$$= 60 + v_o$$

Therefore, the expression for the voltage v_1 is, $60 + v_o$.

Step 4 of 4

Apply super node analysis at all indicated nodes.

$$\frac{v_2}{120 \text{ k}} + \frac{v_o}{120 \text{ k}} + \frac{v_1}{30 \text{ k}} = 0$$

$$\frac{v_2 + v_o + 4v_1}{120 \text{ k}} = 0$$

$$v_2 + v_o + 4v_1 = 0$$

Substitute $60 + v_o$ for v_1 and $120 + v_o$ for v_2 in the equation.

$$120 + v_o + v_o + 4(60 + v_o) = 0$$

$$120 + v_o + v_o + 240 + 4v_o = 0$$

$$360 + 6v_o = 0$$

$$6v_o = -360$$

$$v_o = -\frac{360}{6}$$

$$= -60 \text{ V}$$

Therefore, the value of the voltage, v_o is -60 V .

[Comments \(3\)](#)



Anonymous

where did the 120k go?



Anonymous

the second equation in step 4



Anonymous

nvm i got it