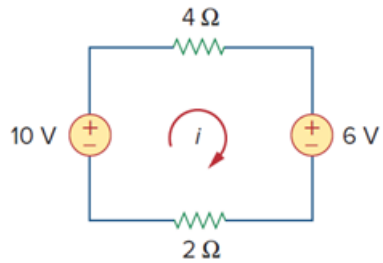


Problem

The loop equation for the circuit in Fig. 3.48 is:

- (a) $-10 + 4i + 6 + 2i = 0$
- (b) $10 + 4i + 6 + 2i = 0$
- (c) $10 + 4i - 6 + 2i = 0$
- (d) $-10 + 4i - 6 + 2i = 0$

Figure 3.48



Step-by-step solution

Step 1 of 1

Answer: (a)

$$-10 + 4i + 6 + 2i = 0$$