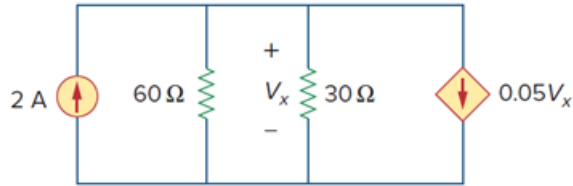


Problem

Apply nodal analysis to solve for V_x in the circuit of Fig. 3.56.

Figure 3.56:



Step-by-step solution

Step 1 of 2

Refer to Figure 3.56 in the text book.

Assume a node at the resistances $60\ \Omega$ and $30\ \Omega$.

The 2 A current enters into the node.

The current through the $60\ \Omega$ and $30\ \Omega$ resistances, and $0.05V_x$ dependent current source leaves the node.

Step 2 of 2

Apply Kirchhoff's current law for the circuit; the sum of the currents entering the node is equal to the sum of the currents leaving the node.

$$\frac{V_x}{30} + \frac{V_x}{60} + 0.05V_x - 2 = 0$$

$$\frac{2V_x + V_x + 3V_x - 120}{60} = 0$$

$$2V_x + V_x + 3V_x - 120 = 0$$

$$6V_x = 120$$

$$V_x = \frac{120}{6}$$

$$= 20\text{ V}$$

Therefore, the value of the voltage V_x is, 20 V.