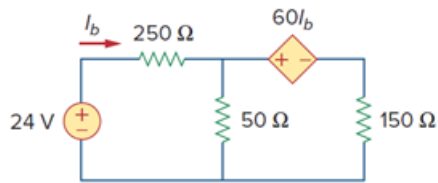


Problem

Determine I_b in the circuit in Fig. 3.58 using nodal analysis.

Figure 3.58:



Step-by-step solution

Step 1 of 4

Refer to Figure 3.58 in the textbook.

Draw the circuit with node notations.

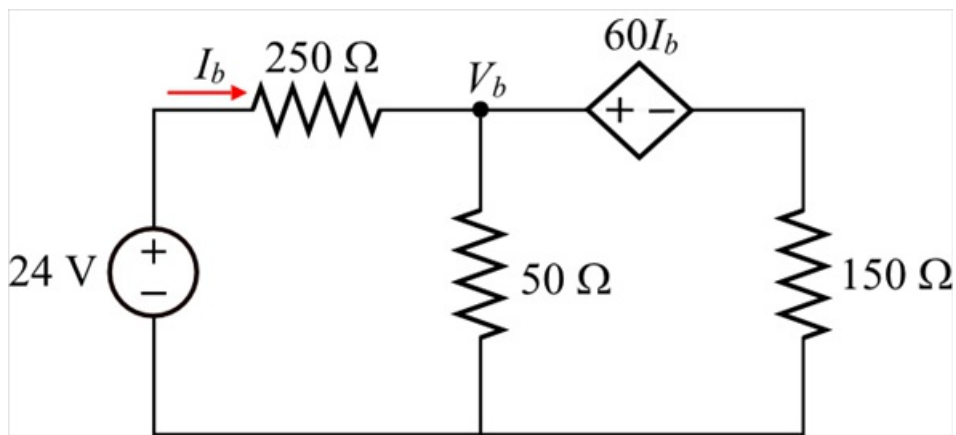


Figure 1

Step 2 of 4

Write the Kirchhoff's current law equation at node, V_b .

$$\begin{aligned} \frac{V_b - 24}{250} + \frac{V_b}{50} + \frac{V_b - 60I_b}{150} &= 0 \\ \frac{3V_b - 72 + 15V_b + 5V_b - 300I_b}{750} &= 0 \\ 23V_b - 300I_b &= 72 \quad \dots\dots (1) \end{aligned}$$

Step 3 of 4

From Figure 1, the current through 250Ω resistor is,

$$\begin{aligned} I_b &= \frac{24 - V_b}{250} \\ 250I_b &= 24 - V_b \\ V_b &= 24 - 250I_b \quad \dots\dots (2) \end{aligned}$$

Substitute $24 - 250I_b$ for V_b in equation (1).

$$23(24 - 250I_b) - 300I_b = 72$$

$$552 - 5750I_b - 300I_b = 72$$

$$(-5750 - 300)I_b = 72 - 552$$

$$-6050I_b = -480$$

$$I_b = \frac{-480}{-6050}$$

$$= 0.07934 \text{ A}$$

$$= 79.34 \text{ mA}$$

Therefore, the value of current, I_b is 79.34 mA.