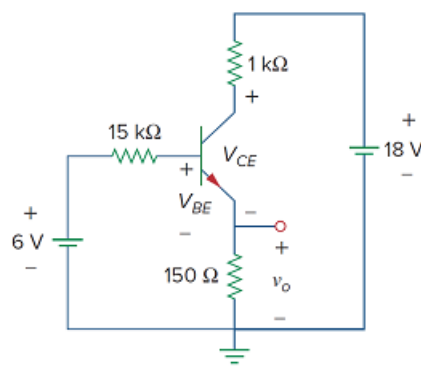


Problem

For the transistor circuit in Fig. 3.42, let $\beta = 100$ and $V_{BE} = 0.7$ V. Determine v_o and V_{CE} .

Figure 3.42:



Step-by-step solution

Step 1 of 6

Refer to Figure 3.42 in the textbook.

Draw the circuit diagram with current directions and voltages as shown in Figure 1.

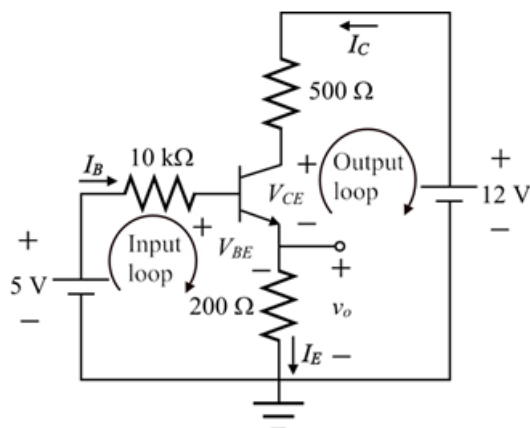


Figure 1

Step 2 of 6

The circuit shown in Figure 1, contains an *npn* transistor.

For the *npn* transistor,

$$I_E = I_B + I_C \dots\dots (1)$$

Write the expression for collector current I_C .

$$I_C = \beta I_B$$

Substitute 100 for β .

$$I_C = 100 I_B$$

Substitute $100 I_B$ for I_C in equation (1).

$$I_E = I_B + 100 I_B$$

$$I_E = 101 I_B$$

Step 3 of 6

Apply Kirchhoff's voltage law to the input loop.

$$-5 + (10 \times 10^3) I_B + V_{BE} + (200 \, \Omega) I_E = 0$$

Substitute 0.7 V for V_{BE} and $101 I_B$ for I_E .

$$-5 + (10 \times 10^3) I_B + 0.7 + (200 \, \Omega)(101 I_B) = 0$$

$$I_B (10 \times 10^3 + (200)(101)) = 4.3$$

$$30200 I_B = 4.3$$

$$I_B = 0.1424 \text{ mA}$$

Step 4 of 6

Write the expression for collector current I_C .

$$I_C = \beta I_B$$

Substitute 100 for β and 0.1424 mA for I_B .

$$\begin{aligned} I_C &= (100)(0.1424 \text{ mA}) \\ &= 14.24 \text{ mA} \end{aligned}$$

Write the expression for emitter current I_E .

$$I_E = 101 I_B$$

Substitute 0.1424 mA for I_B ,

$$\begin{aligned} I_E &= 101(0.1423 \times 10^{-3}) \\ &= 14.38 \text{ mA} \end{aligned}$$

Step 5 of 6

v_o is the voltage across $200\ \Omega$ resistance.

Write the expression for output voltage v_o using ohms law.

$$v_o = 200I_E$$

Substitute 14.38 mA for I_E .

$$\begin{aligned} v_o &= (200)(14.38 \times 10^{-3}) \\ &= 2.876\text{ V} \end{aligned}$$

Therefore, the output voltage, v_o is $\boxed{2.876\text{ V}}$.

Step 6 of 6

Apply Kirchhoff's voltage law to the outer loop.

$$-12 + 500I_C + V_{CE} + v_o = 0$$

Substitute 2.876 V for v_o and 14.24 mA for I_C .

$$-12 + (500)(14.24 \times 10^{-3}) + V_{CE} + 2.876 = 0$$

$$V_{CE} = 12 - 7.12 - 2.876$$

$$V_{CE} = 2.004\text{ V}$$

Therefore, the voltage, V_{CE} is $\boxed{2.004\text{ V}}$.