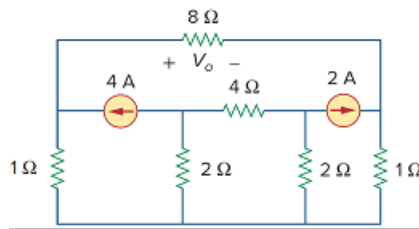


Problem

Use nodal analysis and *MATLAB* to find V_o in the circuit of Fig. 3.73.

Figure 3.73:



Step-by-step solution

Step 1 of 7

Consider the following circuit diagram:

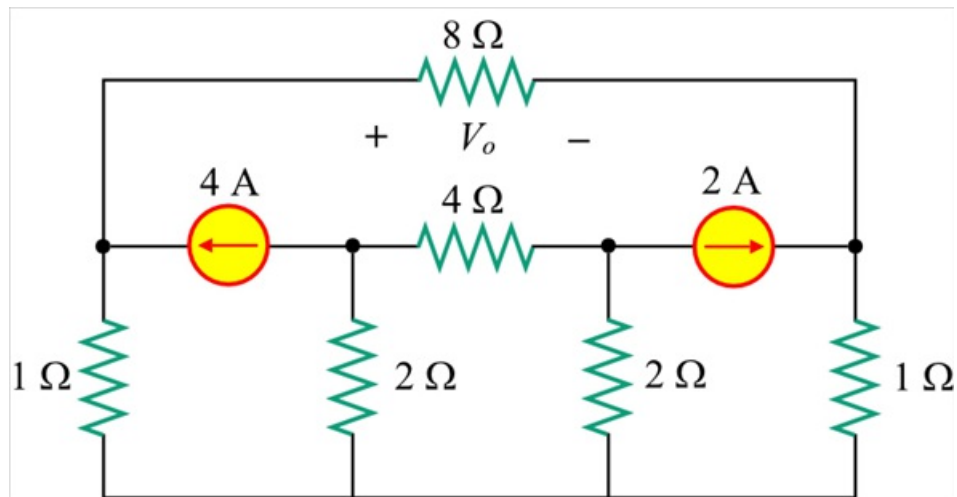


Figure 1

Step 2 of 7

Draw the circuit with node notations.

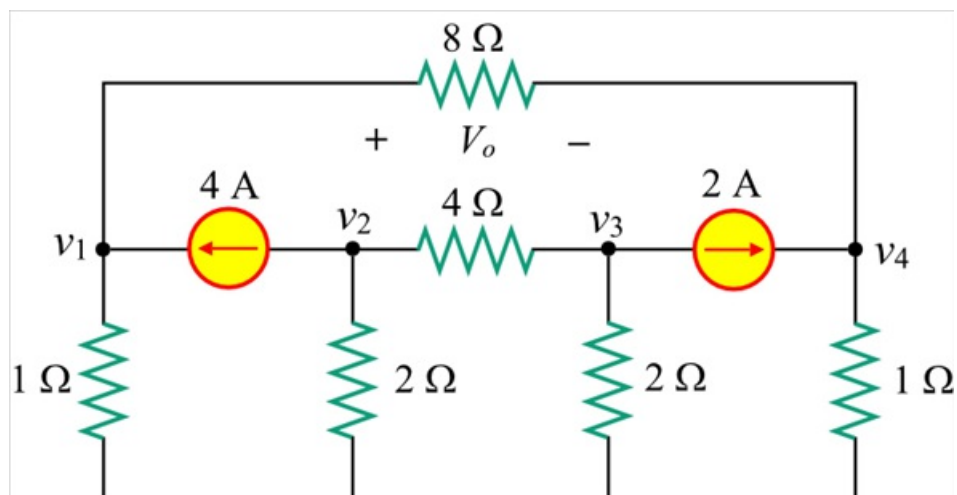


Figure 2

Step 3 of 7

Apply Kirchhoff's current law at node 1.

$$\begin{aligned}\frac{v_1}{1} + \frac{v_1 - v_4}{8} &= 4 \\ \left(\frac{1}{1} + \frac{1}{8}\right)v_1 - \frac{v_4}{8} &= 4 \\ \left(\frac{8+1}{8}\right)v_1 - \frac{v_4}{8} &= 4 \\ (8+1)v_1 - v_4 &= (4)(8) \\ 9v_1 - v_4 &= 32 \quad \dots\dots (1)\end{aligned}$$

Step 4 of 7

Apply Kirchhoff's current law at node 2.

$$\begin{aligned}\frac{v_2}{2} + \frac{v_2 - v_3}{4} &= -4 \\ \left(\frac{1}{2} + \frac{1}{4}\right)v_2 - \frac{v_3}{4} &= -4 \\ \left(\frac{2+1}{4}\right)v_2 - \frac{v_3}{4} &= -4 \\ 3v_2 - v_3 &= (-4)(4) \\ 3v_2 - v_3 &= -16 \quad \dots\dots (2)\end{aligned}$$

Step 5 of 7

Apply Kirchhoff's current law at node 3.

$$\begin{aligned}\frac{v_3}{2} + \frac{v_3 - v_2}{4} &= -2 \\ \left(\frac{1}{2} + \frac{1}{4}\right)v_3 - \frac{v_2}{4} &= -2 \\ \left(\frac{2+1}{4}\right)v_3 - \frac{v_2}{4} &= -2 \\ v_2 - 3v_3 &= (2)(4) \\ v_2 - 3v_3 &= 8 \quad \dots\dots (3)\end{aligned}$$

Step 6 of 7

Apply Kirchhoff's current law at node 4.

$$\frac{v_4}{1} + \frac{v_4 - v_1}{8} = 2$$

$$\left(\frac{1}{1} + \frac{1}{8}\right)v_4 - \frac{v_1}{8} = 2$$

$$\left(\frac{8+1}{8}\right)v_4 - \frac{v_1}{8} = 2$$

$$-v_1 + 9v_4 = (2)(8)$$

$$v_1 - 9v_4 = -16 \dots\dots (4)$$

Write equations (1), (2), (3) and (4) in Matrix form.

$$\begin{bmatrix} 9 & 0 & 0 & -1 \\ 0 & 3 & -1 & 0 \\ 0 & 1 & -3 & 0 \\ 1 & 0 & 0 & -4 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix} = \begin{bmatrix} 32 \\ -16 \\ 8 \\ -16 \end{bmatrix}$$

The following is the MATLAB code for calculating node voltages.

```
>>a=[9 0 0 -1;0 3 -1 0;0 1 -3 0;1 0 0 -9];>>b=[32;-16;8;-16];>>c=inv(a)*b
```

MATLAB output:

```
c =3.8000-7.0000i-5.0000i2.2000
```

Step 7 of 7

The node voltages are,

$$v_1 = 3.8 \text{ V}$$

$$v_2 = -7 \text{ V}$$

$$v_3 = -5 \text{ V}$$

$$v_4 = 2.2 \text{ V}$$

Now calculate the value of voltage, V_o .

$$\begin{aligned} V_o &= v_1 - v_4 \\ &= 3.8 - 2.2 \\ &= 1.6 \text{ V} \end{aligned}$$

Therefore, the value of voltage, V_o is 1.6 V.