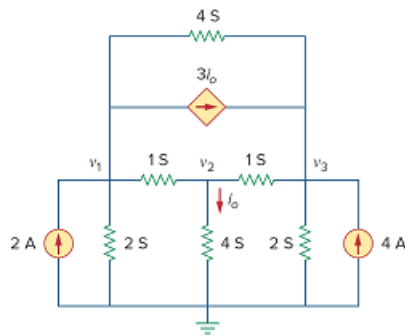


Problem

Use nodal analysis to determine voltages v_1 , v_2 , and v_3 in the circuit of Fig. 3.76.

Figure 3.76:



Step-by-step solution

Step 1 of 10

Refer to Figure 3.76 in the textbook.

Apply nodal analysis at node v_1 .

From Figure 3.76,

$$i_o = 4v_2 \dots\dots (1)$$

$$-2 + \frac{v_1}{(1/2)} + \frac{v_1 - v_2}{(1/1)} + 3i_o + \frac{v_1 - v_3}{(1/4)} = 0$$

$$2v_1 + v_1 - v_2 + 3i_o + 4v_1 - 4v_3 = 2 \dots\dots (2)$$

Step 2 of 10

Replace equation 2 in equation 1.

$$2v_1 + v_1 - v_2 + 3(4v_2) + 4v_1 - 4v_3 = 2$$

$$2v_1 + v_1 - v_2 + 12v_2 + 4v_1 - 4v_3 = 2$$

$$7v_1 + 11v_2 - 4v_3 = 2 \dots\dots (3)$$

Apply nodal analysis at node 2.

$$1(v_2 - v_1) + 4v_2 + v_2 - v_3 = 0$$

$$6v_2 - v_1 - v_3 = 0 \dots\dots (4)$$

Step 3 of 10

Apply nodal analysis at node 3.

$$1(v_3 - v_2) + 4(v_3 - v_1) - 3i_o + 2v_3 - 4 = 0$$

$$7v_3 - v_2 - 4v_1 - 3(4v_2) - 4 = 0$$

$$7v_3 - v_2 - 4v_1 - 12v_2 - 4 = 0$$

$$7v_3 - 4v_1 - 13v_2 = 4 \dots\dots (5)$$

Step 4 of 10

Consider the matrix as,

$$\begin{bmatrix} 7 & 11 & -4 \\ -1 & 6 & -1 \\ -4 & -13 & 7 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \\ 4 \end{bmatrix}$$

Determine the value of Δ .

$$\begin{aligned} \Delta &= (7(42-13) - 11(-7-4) - 4(13+24)) \\ &= 176 \end{aligned}$$

Step 5 of 10

Determine the value of Δ_1 .

Consider the matrix as,

$$\begin{bmatrix} 2 & 11 & -4 \\ 0 & 6 & -1 \\ 4 & -13 & 7 \end{bmatrix}$$

$$\begin{aligned} \Delta_1 &= (2(42-13) - 11(4) - 4(-24)) \\ &= 110 \end{aligned}$$

Step 6 of 10

Determine the value of Δ_2 .

Consider the matrix as,

$$\begin{bmatrix} 7 & 2 & -4 \\ -1 & 0 & -1 \\ -4 & 4 & 7 \end{bmatrix}$$

$$\begin{aligned} \Delta_2 &= (7(4) - 2(-7-4) - 4(-4)) \\ &= 66 \end{aligned}$$

Step 7 of 10

Determine the value of Δ_3 .

Consider the matrix as,

$$\begin{bmatrix} 7 & 11 & 2 \\ -1 & 6 & 0 \\ -4 & -13 & 4 \end{bmatrix}$$

$$\begin{aligned} \Delta_3 &= (7(24) - 11(-4) + 2(13+24)) \\ &= 286 \end{aligned}$$

Step 8 of 10

Determine the value of the voltage v_1 .

Consider the equation for the v_1 .

$$v_1 = \frac{\Delta_1}{\Delta} \dots\dots (6)$$

Replace 110 for Δ_1 , and 176 for Δ in equation 6.

$$\begin{aligned} v_1 &= \frac{110}{176} \\ &= 0.625 \text{ V} \end{aligned}$$

Therefore, the value of the voltage v_1 is 625 mV.

Step 9 of 10

Determine the value of the voltage v_2 .

Consider the equation for the v_2 .

$$v_2 = \frac{\Delta_2}{\Delta} \dots\dots (7)$$

Replace 66 for Δ_2 , and 176 for Δ in equation 7.

$$\begin{aligned} v_2 &= \frac{66}{176} \\ &= 0.375 \text{ V} \end{aligned}$$

Therefore, the value of the voltage v_1 is 375 mV.

Step 10 of 10

Determine the value of the voltage v_3 .

Consider the equation for the v_3 .

$$v_3 = \frac{\Delta_3}{\Delta} \dots\dots (8)$$

Replace 286 for Δ_3 , and 176 for Δ in equation 8.

$$\begin{aligned} v_3 &= \frac{286}{176} \\ &= 1.625 \text{ V} \end{aligned}$$

Therefore, the value of the voltage v_3 is 1.625 V.