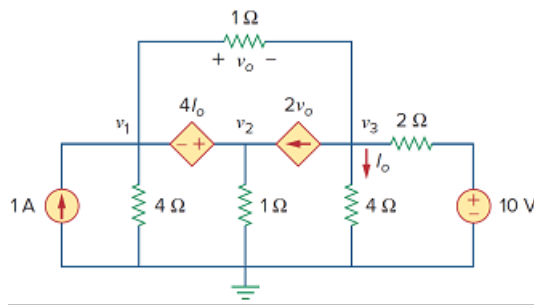


Problem

Find the node voltages for the circuit in Fig. 3.80.

Figure 3.80:



Step-by-step solution

Step 1 of 2

Refer to Figure 3.80 in the textbook.

There is a dependent voltage source present between the nodes with node voltages V_1 and V_2 .

The two nodes are considered as a single node called the super node.

Write the Kirchhoff's Current Law equation at the super node.

$$-1 + \frac{v_1 - v_3}{1} + \frac{v_1}{4} + \frac{v_2}{1} + -2v_o = 0$$

$$1 + 2v_o = \frac{v_1}{4} + \frac{v_2}{1} + \frac{v_1 - v_3}{1} \dots\dots (1)$$

But, $v_o = v_1 - v_3$

Substitute $v_1 - v_3$ for v_o in equation (1).

$$1 + 2(v_1 - v_3) = \frac{v_1}{4} + \frac{v_2}{1} + \frac{v_1 - v_3}{1}$$

$$1 + 2(v_1 - v_3) = \frac{v_1 + 4v_2 + 4(v_1 - v_3)}{4}$$

$$4 + 8(v_1 - v_3) = v_1 + 4v_2 + 4(v_1 - v_3)$$

$$4 + 8v_1 - 8v_3 = v_1 + 4v_2 + 4v_1 - 4v_3$$

$$4 + 8v_1 - 8v_3 = 5v_1 + 4v_2 - 4v_3$$

$$4 = -8v_1 + 8v_3 + 5v_1 + 4v_2 - 4v_3$$

$$4 = -3v_1 + 4v_2 + 4v_3 \dots\dots (2)$$

Step 2 of 2

Write the Kirchhoff's Current Law equation at the node 3, node labeled with node voltage v_3 .

$$2v_o + \frac{v_3}{4} + \frac{v_3 - v_1}{1} + \frac{v_3 - 10}{2} = 0$$

$$8v_o + v_3 + 4(v_3 - v_1) + 2(v_3 - 10) = 0$$

$$8v_o + 7v_3 - 4v_1 - 20 = 0$$

Substitute $v_1 - v_3$ for v_o in the above equation.

$$8(v_1 - v_3) + 7v_3 - 4v_1 - 20 = 0$$

$$8v_1 - 8v_3 + 7v_3 - 4v_1 - 20 = 0$$

$$4v_1 - v_3 = 20 \dots\dots (3)$$

Write the expression for the voltage v_2 .

$$v_2 = v_1 + 4I_o, \text{ where } I_o = \frac{v_3}{4}.$$

$$v_2 = v_1 + 4\left(\frac{v_3}{4}\right)$$

$$= v_1 + v_3$$

$$v_1 - v_2 + v_3 = 0 \dots\dots (4)$$

Solve equations (2), (3) and (4) to obtain v_1 , v_2 and v_3 .

$$v_1 = 4.97 \text{ V}$$

$$v_2 = 4.8484 \text{ V}$$

$$v_3 = -0.12 \text{ V}$$

Thus, the required node voltages are,

$v_1 = 4.97 \text{ V}$
$v_2 = 4.8484 \text{ V}$
$v_3 = -0.12 \text{ V}$