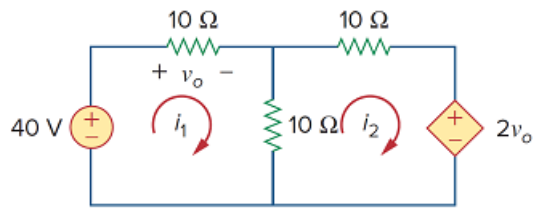


Problem

Calculate the mesh currents i_1 and i_2 in Fig. 3.92.

Figure 3.92:



Step-by-step solution

Step 1 of 4

Refer to Figure 3.92 in the text book.

Consider the expression for the voltage v_o .

$$v_o = i_1(10)$$

Therefore, the expression for the voltage v_o is, $i_1(10)$.

Step 2 of 4

Applying Kirchhoff's voltage law, the algebraic sum of all voltages around a closed path (or loop) is zero.

For mesh 1, Kirchhoff's voltage law gives,

$$-40 + i_1(10) + (i_1 - i_2)(10) = 0$$

$$-40 + 10i_1 + 10i_1 - 10i_2 = 0$$

$$20i_1 - 10i_2 - 40 = 0$$

$$2i_1 - i_2 - 4 = 0$$

$$i_2 = 2i_1 - 4 \dots\dots (1)$$

Therefore, the expression for the current i_2 is, $2i_1 - 4$.

Step 3 of 4

For mesh 2, Kirchhoff's voltage law gives,

$$i_2(10) + (i_2 - i_1)(10) + 2v_o = 0$$

$$10i_2 + 10i_2 - 10i_1 + 2v_o = 0$$

$$20i_2 - 10i_1 + 2v_o = 0$$

Substitute $i_1(10)$ for v_o and $2i_1 - 4$ for i_2 .

$$20(2i_1 - 4) - 10i_1 + 2i_1(10) = 0$$

$$40i_1 - 80 - 10i_1 + 20i_1 = 0$$

$$50i_1 - 80 = 0$$

$$50i_1 = 80$$

$$i_1 = \frac{80}{50}$$

$$= 1.6 \text{ A}$$

Therefore, the value of the mesh current i_1 is, 1.6 A.

[Comments \(2\)](#)

☐

Anonymous

why when I sub in $10i_1$ for V_o and solve for i_1 in terms of i_2 it gives me the wrong answer. I got $i_1 = -2i_2$. I would then sub that into the last equation to solve for i_2 .

☐

Anonymous

never mind I got it

Step 4 of 4

Recall equation (1).

$$i_2 = 2i_1 - 4$$

Substitute 1.6 A for i_1 .

$$i_2 = 2(1.6) - 4$$

$$= 3.2 - 4$$

$$= -0.8 \text{ A}$$

Therefore, the value of the mesh current i_2 is, -0.8 A.