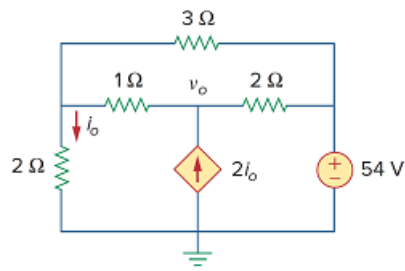


Problem

Find v_o and i_o in the circuit of Fig. 3.94.

Figure 3.94:



Step-by-step solution

Step 1 of 8

Refer to Figure 3.94 in the text book.

Draw the circuit diagram shown in Figure 1.

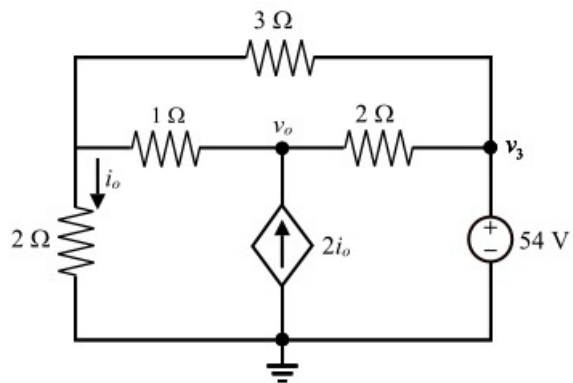


Figure 1

Step 2 of 8

The circuit is labeled and meshes 1 and 2 form a super mesh as shown in Figure 2.

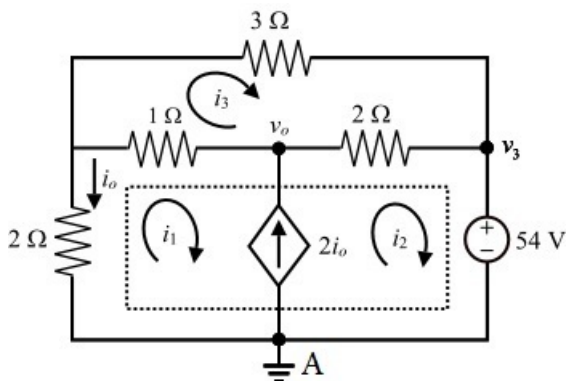


Figure 2

Step 3 of 8

Apply Kirchhoff's voltage law to the super mesh,

$$2i_1 + (i_1 - i_3) + 2(i_2 - i_3) + 54 = 0$$

$$3i_1 + 2i_2 - 3i_3 = -54$$

Therefore $3i_1 + 2i_2 - 3i_3 = -54$ (1)

Apply Kirchhoff's voltage law to mesh 3,

$$3i_3 + 2(i_3 - i_2) + (i_3 - i_1) = 0$$

$$-i_1 - 2i_2 + 6i_3 = 0$$

Therefore $-i_1 - 2i_2 + 6i_3 = 0$ (2)

Apply Kirchhoff's current law at node A,

$$i_2 - i_1 = 2i_o$$

But $i_o = -i_1$

Substitute $-i_1$ for i_o .

$$i_2 - i_1 = -2i_1$$

$$i_2 = -i_1$$

Therefore $i_2 = -i_1$ (3)

[Comments \(3\)](#)



Anonymous

Why does $i_0 = -i_1$?



Anonymous

look at the direction of mesh i_1 and compare it to the current i_0 .



Anonymous

i_0

Step 4 of 8

Substitute equation (3) in equation (1),

$$3i_1 + 2i_2 - 3i_3 = -54$$

$$3i_1 + 2(-i_1) - 3i_3 = -54$$

$$i_1 - 3i_3 = -54$$

Therefore $i_1 - 3i_3 = -54$ (4)

Substitute equation (3) in equation (2),

$$-i_1 - 2i_2 + 6i_3 = 0$$

$$-i_1 - 2(-i_1) + 6i_3 = 0$$

$$i_1 + 6i_3 = 0$$

Therefore $i_1 + 6i_3 = 0$ (5)

Step 5 of 8

Subtract equation (5) from equation (4),

$$i_1 - 3i_3 = -54$$

$$\underline{i_1 + 6i_3 = 0}$$

$$-9i_3 = -54$$

$$i_3 = 6 \text{ A}$$

Substitute 6 A for i_3 in equation (5),

$$i_1 + 6i_3 = 0$$

$$i_1 + 6(6) = 0$$

$$i_1 = -36 \text{ A}$$

Substitute -36 A for i_1 in equation (3),

$$i_2 = -i_1$$

$$= -(-36)$$

$$= 36 \text{ A}$$

Step 6 of 8

But

$$i_o = -i_1$$

$$= -(-36)$$

$$= 36 \text{ A}$$

Therefore the current i_o is $\boxed{36 \text{ A}}$.

Step 7 of 8

To get v_o , the circuit is shown in Figure 3.

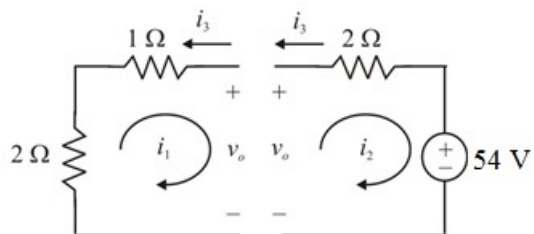


Figure 3

Step 8 of 8

Apply Kirchhoff's voltage law to the loop 1,

$$2i_1 + 1(i_1 - i_3) + v_o = 0$$

$$3i_1 - i_3 + v_o = 0$$

Substitute 6 A for i_3 and -36 A for i_1 .

$$v_o = i_3 - 3i_1$$

$$= 6 - 3(-36)$$

$$= 6 + 108$$

$$= 114 \text{ V}$$

Therefore the node voltage v_o is, $\boxed{114 \text{ V}}$.