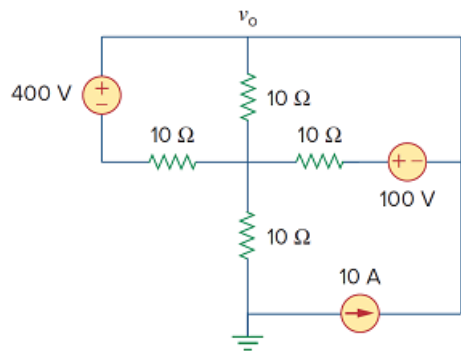


Problem

Apply mesh analysis to find v_o in the circuit of Fig. 3.96.

Figure 3.96:



Step-by-step solution

Step 1 of 4

Refer to Figure 3.96 in the text book.

Identify the loops and currents in the circuit diagram shown in Figure 1.

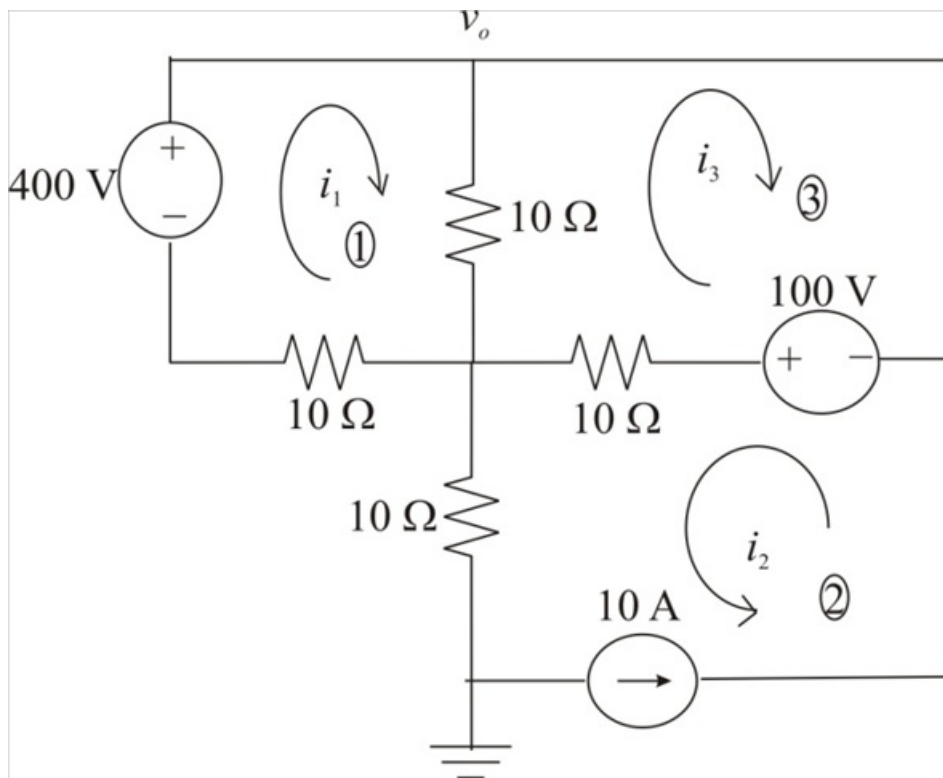


Figure 1

Step 2 of 4

Notice that the current i_2 is, 10 A .

Apply mesh analysis in loop 3.

Apply Kirchhoff's voltage law, the algebraic sum of all voltages around a closed path (or loop) is zero.

$$-100 + (i_2 + i_3)(10) + (i_3 - i_1)(10) = 0$$

$$-100 + 10i_2 + 10i_3 + 10i_3 - 10i_1 = 0$$

$$-100 + 10i_2 + 20i_3 - 10i_1 = 0$$

$$-10 + i_2 + 2i_3 - i_1 = 0$$

Substitute 10 A for i_2 .

$$-10 + 10 + 2i_3 - i_1 = 0$$

$$2i_3 - i_1 = 0$$

$$i_1 = 2i_3$$

Therefore, the expression for the current i_1 is, $2i_3$.

Step 3 of 4

Apply mesh analysis in loop 1.

For mesh 1, Kirchhoff's voltage law gives,

$$i_1(10) - 400 + (i_1 - i_3)(10) = 0$$

$$i_1 - 40 + i_1 - i_3 = 0$$

$$2i_1 - 40 - i_3 = 0$$

Substitute $2i_3$ for i_1 .

$$2(2i_3) - 40 - i_3 = 0$$

$$4i_3 - 40 - i_3 = 0$$

$$3i_3 - 40 = 0$$

$$3i_3 = 40$$

$$i_3 = \frac{40}{3}$$

$$= 13.33\text{ A}$$

Therefore, the value of the current i_3 is, 13.33 A .

Step 4 of 4

Calculate the value of voltage v_o .

$$v_o = i_2(10) + (i_1 - i_3)(10)$$

Substitute $2i_3$ for i_1 .

$$\begin{aligned} v_o &= i_2(10) + (2i_3 - i_3)(10) \\ &= i_2(10) + i_3(10) \\ &= (i_2 + i_3)(10) \end{aligned}$$

Substitute 13.33 A for i_3 and 10 A for i_2 .

$$\begin{aligned} v_o &= (10 + 13.33)(10) \\ &= (23.33)(10) \\ &= 233.3 \text{ V} \end{aligned}$$

Therefore, the value of the voltage v_o is, 233.3 V.

[Comments \(2\)](#)

☐

Anonymous

How on earth does the voltage in the top and bottom 10 ohm resistors equal to V_0 ?

☐

Anonymous

Because if you measure the voltage across point V_0 and ground then you are measuring the drop across those middle resistors only