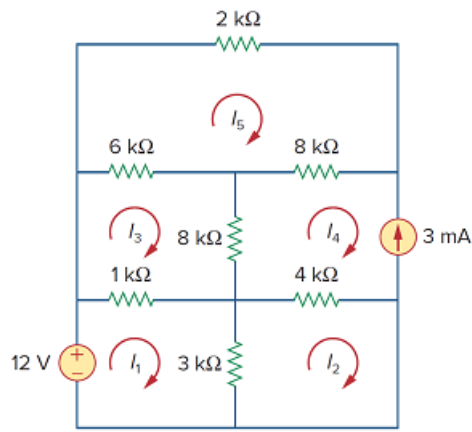


Problem

Find the mesh currents in the circuit of Fig. 3.98 using *MATLAB*.

Figure 3.98:



Step-by-step solution

Step 1 of 6

Consider the following circuit diagram:

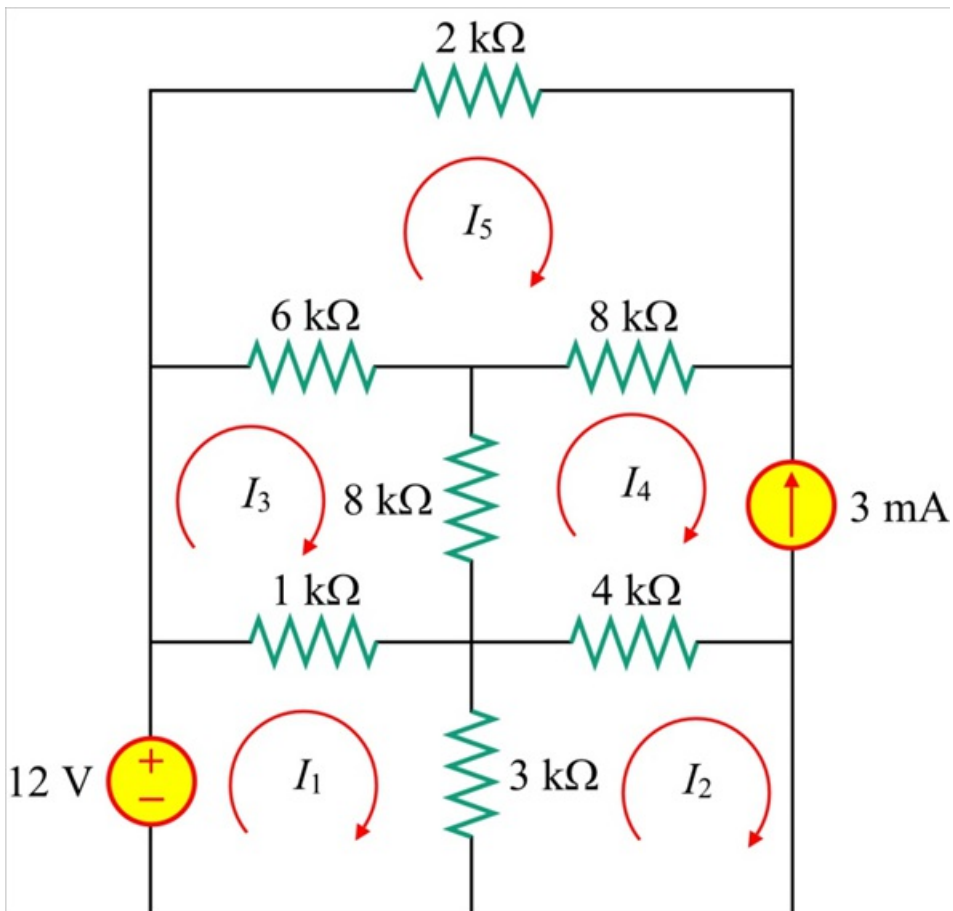


Figure 1

Step 2 of 6

From the Figure 1, the current in the mesh 4 is 3 mA.

$$I_4 = -3 \text{ mA} \dots\dots (1)$$

Apply Kirchhoff's voltage law to the loop 1.

$$(1 \text{ k})(I_1 - I_3) + (3 \text{ k})(I_1 - I_2) = 12$$

$$(1 \text{ k} + 3 \text{ k})I_1 - (1 \text{ k})I_3 - (3 \text{ k})I_2 = 12$$

$$(4 \text{ k})I_1 - (3 \text{ k})I_2 - (1 \text{ k})I_3 = 12$$

$$4I_1 - 3I_2 - I_3 = 12 \text{ mA} \dots\dots (2)$$

Step 3 of 6

Apply Kirchhoff's voltage law to the loop 2.

$$(3 \text{ k})(I_2 - I_1) + (4 \text{ k})(I_2 - I_4) = 0$$

$$-(3 \text{ k})I_1 + (3 \text{ k} + 4 \text{ k})I_2 - (4 \text{ k})I_4 = 0$$

$$-(3 \text{ k})I_1 + (7 \text{ k})I_2 - (4 \text{ k})I_4 = 0$$

$$3I_1 - 7I_2 + 4I_4 = 0 \dots\dots (3)$$

Apply Kirchhoff's voltage law to the loop 3.

$$(1 \text{ k})(I_3 - I_1) + (8 \text{ k})(I_3 - I_4) + (6 \text{ k})(I_3 - I_5) = 0$$

$$-(1 \text{ k})I_1 + (1 \text{ k} + 8 \text{ k} + 6 \text{ k})I_3 - (8 \text{ k})I_4 - (6 \text{ k})I_5 = 0$$

$$-(1 \text{ k})I_1 + (15 \text{ k})I_3 - (8 \text{ k})I_4 - (6 \text{ k})I_5 = 0$$

$$I_1 - 15I_3 + 8I_4 + 6I_5 = 0 \dots\dots (4)$$

Step 4 of 6

Apply Kirchhoff's voltage law to the loop 5.

$$(6 \text{ k})(I_5 - I_3) + (8 \text{ k})(I_5 - I_4) + (2 \text{ k})(I_5) = 0$$

$$-(6 \text{ k})I_3 - (8 \text{ k})I_4 + (6 \text{ k} + 8 \text{ k} + 2 \text{ k})I_5 = 0$$

$$-(6 \text{ k})I_3 - (8 \text{ k})I_4 + (16 \text{ k})I_5 = 0$$

$$3I_3 + 4I_4 - 8I_5 = 0 \dots\dots (5)$$

Write equations (1), (2), (3), (4), and (5) in the matrix form:

$$\begin{bmatrix} 0 & 0 & 0 & 1 & 0 \\ 4 & -3 & -1 & 0 & 0 \\ 3 & -7 & 0 & 4 & 0 \\ 1 & 0 & -15 & 8 & 6 \\ 0 & 0 & 3 & 4 & -8 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \\ I_5 \end{bmatrix} = \begin{bmatrix} -3 \text{ mA} \\ 12 \text{ mA} \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Step 5 of 6

The following is the MATLAB code for calculating loop currents.

```
a=[0 0 0 1 0;4 -3 -1 0 0;3 -7 0 4 0;1 0 -15 8 6;0 0 3 4 -8];b=[-0.003;0.012;0;0;0];c=inv(a)*b
```

Step 6 of 6

MATLAB output:

$c = 0.001619553666312 - 0.001020191285866i - 0.002461211477152i - 0.003000000000000i - 0.002422954303932i$

The values of the mesh currents are,

$$I_1 = 1.6195 \text{ mA}$$

$$I_2 = -1.0202 \text{ mA}$$

$$I_3 = -2.4612 \text{ mA}$$

$$I_4 = -3 \text{ mA}$$

$$I_5 = -2.423 \text{ mA}$$

Therefore, the values of the mesh currents, I_1, I_2, I_3, I_4, I_5 in the circuit shown in Figure 1 are

$1.6195 \text{ mA}, -1.0202 \text{ mA}, -2.4612 \text{ mA}, -3 \text{ mA}, -2.423 \text{ mA}$ respectively.