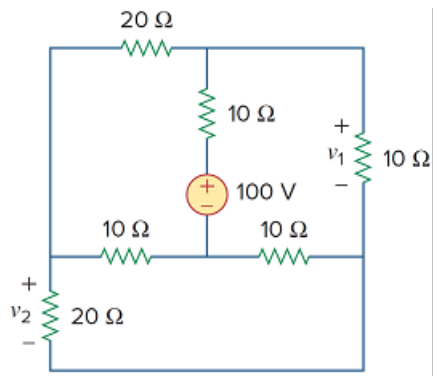


Problem

Determine v_1 and v_2 in the circuit of Fig. 3.101.

Figure 3.101:



Step-by-step solution

Step 1 of 7

Refer to circuit diagram in Figure 3.101 in the text book.

Identify the loops and currents in the circuit diagram shown in Figure 1.

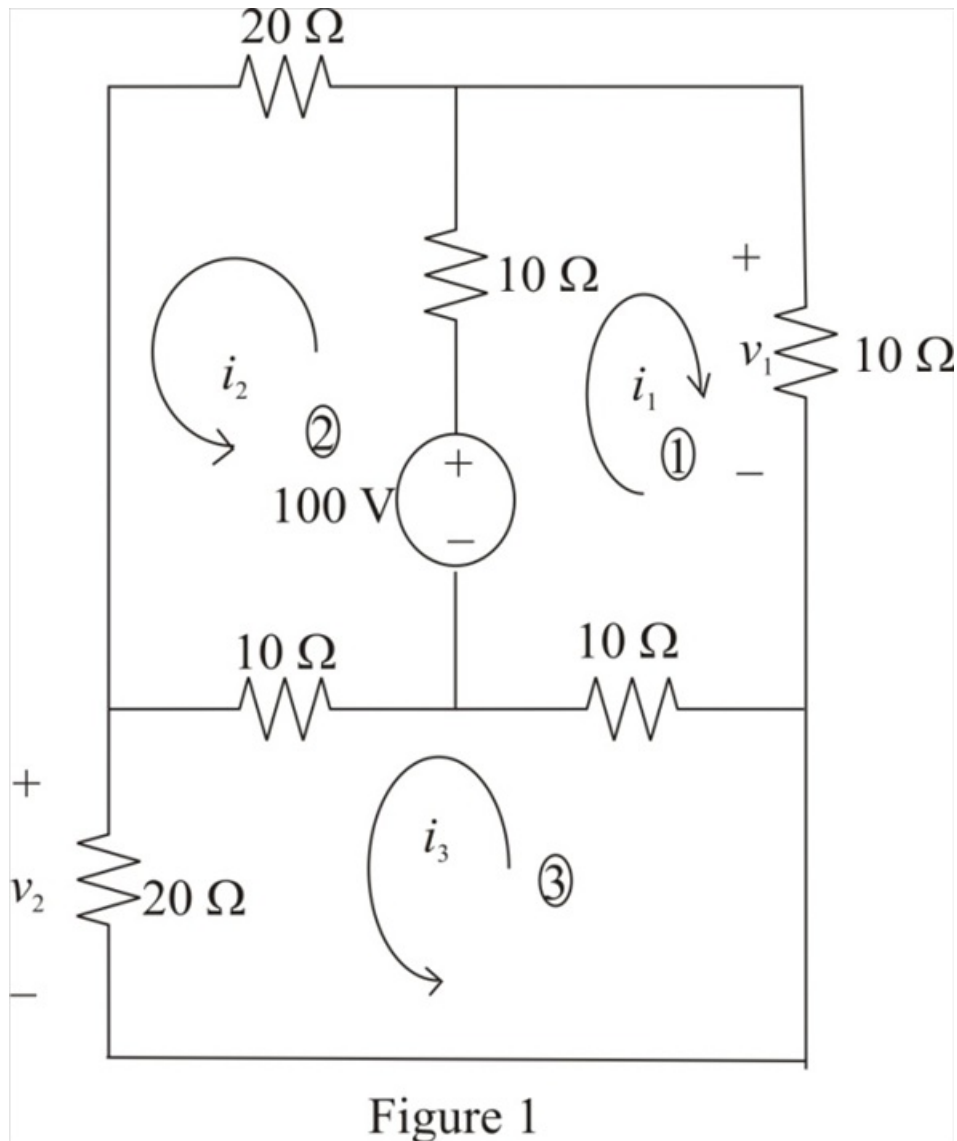


Figure 1

Step 2 of 7

Apply Kirchhoff's Voltage Law to Loop-1.

$$-100 + (i_1 + i_2)(10) + i_1(10) + (i_1 + i_3)(10) = 0$$

$$-100 + (10 + 10 + 10)i_1 + 10i_2 + 10i_3 = 0$$

$$30i_1 + 10i_2 + 10i_3 = 100$$

$$3i_1 + i_2 + i_3 = 10$$

$$i_2 = 10 - i_3 - 3i_1 \dots\dots (1)$$

Step 3 of 7

Apply Kirchhoff's Voltage Law to Loop-2.

$$-100 + (i_1 + i_2)(10) + i_2(20) + (i_2 - i_3)(10) = 0$$

$$-100 + 10i_1 + (10 + 20 + 10)i_2 - 10i_3 = 0$$

$$10i_1 + 40i_2 - 10i_3 = 100$$

$$i_1 + 4i_2 - i_3 = 10$$

Substitute $10 - i_3 - 3i_1$ for i_2 .

$$i_1 + 4(10 - i_3 - 3i_1) - i_3 - 10 = 0$$

$$i_1 + 40 - 4i_3 - 12i_1 - i_3 - 10 = 0$$

$$-11i_1 - 5i_3 + 30 = 0$$

$$5i_3 = 30 - 11i_1$$

$$i_3 = \frac{30 - 11i_1}{5} \dots\dots (2)$$

Step 4 of 7

Apply Kirchhoff's Voltage Law to Loop-3.

$$(i_3 - i_2)(10) + i_3(20) + (i_3 + i_1)(10) = 0$$

$$(10 + 20 + 10)i_3 - 10i_2 + 10i_1 = 0$$

$$40i_3 - 10i_2 + 10i_1 = 0$$

$$4i_3 - i_2 + i_1 = 0$$

Substitute $10 - i_3 - 3i_1$ for i_2 .

$$4i_3 - (10 - i_3 - 3i_1) + i_1 = 0$$

$$4i_3 - 10 + i_3 + 3i_1 + i_1 = 0$$

$$5i_3 - 10 + 4i_1 = 0$$

Substitute $\frac{30 - 11i_1}{5}$ for i_3 .

$$5\left(\frac{30 - 11i_1}{5}\right) - 10 + 4i_1 = 0$$

$$30 - 11i_1 - 10 + 4i_1 = 0$$

$$20 - 7i_1 = 0$$

$$7i_1 = 20$$

$$i_1 = \frac{20}{7}$$

$$= 2.857 \text{ A}$$

Step 5 of 7

Calculate the value of the voltage v_1 .

$$v_1 = i_1(10)$$

Substitute 2.857 A for i_1 .

$$v_1 = (2.857 \text{ A})(10 \Omega)$$

$$= 28.57 \text{ V}$$

Therefore, the value of the voltage v_1 is, 28.57 V .

Step 6 of 7

Recall equation (2).

$$i_3 = \frac{30 - 11i_1}{5}$$

Substitute 2.857 A for i_1 .

$$\begin{aligned} i_3 &= \frac{30 - (11)(2.857)}{5} \\ &= \frac{30 - 31.427}{5} \\ &= \frac{-1.427}{5} \\ &= -0.2857 \text{ A} \end{aligned}$$

Step 7 of 7

Calculate the value of the voltage v_2 .

$$v_2 = i_3 (20)$$

Substitute -0.2857 A for i_3 .

$$\begin{aligned} v_2 &= (-0.2857 \text{ A})(20 \Omega) \\ &= -5.714 \text{ V} \end{aligned}$$

Therefore, the value of the voltage v_2 is $\boxed{-5.714 \text{ V}}$.