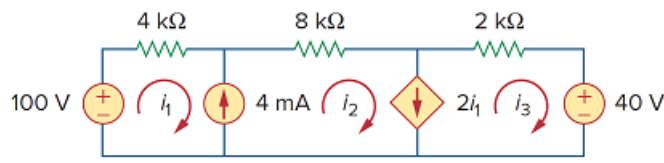


Problem

Find the mesh currents i_1 , i_2 , and i_3 in the network of Fig. 3.106.

Figure 3.106:



Step-by-step solution

Step 1 of 4

Refer to Figure 3.106 in the textbook.

From the Figure 3.106,

$$i_2 - i_1 = 4 \text{ mA}$$

$$-i_1 + i_2 = 4 \times 10^{-3} \text{ (1)}$$

Write the super mesh equation.

$$-100 + 4ki_1 + 8ki_2 + 2ki_3 + 40 = 0$$

$$4ki_1 + 8ki_2 + 2ki_3 = 60$$

$$2i_1 + 4i_2 + i_3 = 30 \times 10^{-3} \text{ (2)}$$

From the Figure 3.106,

$$i_2 - i_3 = 2i_1$$

$$-2i_1 + i_2 - i_3 = 0 \text{ (3)}$$

Step 2 of 4

Write the equations (1), (2) and (3) in matrix form.

$$\begin{bmatrix} -1 & 1 & 0 \\ 2 & 4 & 1 \\ -2 & 1 & -1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 4 \times 10^{-3} \\ 30 \times 10^{-3} \\ 0 \end{bmatrix}$$

Calculate the determinants.

$$\begin{aligned} \Delta &= \begin{vmatrix} -1 & 1 & 0 \\ 2 & 4 & 1 \\ -2 & 1 & -1 \end{vmatrix} \\ &= -1(-4-1) - (1)(-2+2) + 0(2+8) \\ &= 5 \end{aligned}$$

$$\begin{aligned} \Delta_1 &= \begin{vmatrix} 4 \times 10^{-3} & 1 & 0 \\ 30 \times 10^{-3} & 4 & 1 \\ 0 & 1 & -1 \end{vmatrix} \\ &= 4 \times 10^{-3}(-4-1) - (1)(-30 \times 10^{-3}) + 0(30 \times 10^{-3}) \\ &= -20 \times 10^{-3} + 30 \times 10^{-3} \\ &= 10 \times 10^{-3} \end{aligned}$$

Step 3 of 4

Calculate the determinants.

$$\begin{aligned}\Delta_2 &= \begin{vmatrix} -1 & 4 \times 10^{-3} & 0 \\ 2 & 30 \times 10^{-3} & 1 \\ -2 & 0 & -1 \end{vmatrix} \\ &= -1(-30 \times 10^{-3}) - (4 \times 10^{-3})(-2 + 2) + 0(0 + 60 \times 10^{-3}) \\ &= 30 \times 10^{-3} \\ \Delta_3 &= \begin{vmatrix} -1 & 1 & 4 \times 10^{-3} \\ 2 & 4 & 30 \times 10^{-3} \\ -2 & 1 & 0 \end{vmatrix} \\ &= -1(0 - 30 \times 10^{-3}) + (-1)(0 + 60 \times 10^{-3}) + 4 \times 10^{-3}(2 + 8) \\ &= 30 \times 10^{-3} - 60 \times 10^{-3} + 40 \times 10^{-3} \\ &= 10 \times 10^{-3}\end{aligned}$$

Step 4 of 4

Calculate the mesh currents using Cramer's rule.

$$\begin{aligned}i_1 &= \frac{\Delta_1}{\Delta} \\ &= \frac{10 \times 10^{-3}}{5} \\ &= 2 \text{ mA} \\ i_2 &= \frac{\Delta_2}{\Delta} \\ &= \frac{30 \times 10^{-3}}{5} \\ &= 6 \text{ mA} \\ i_3 &= \frac{\Delta_3}{\Delta} \\ &= \frac{10 \times 10^{-3}}{5} \\ &= 2 \text{ mA}\end{aligned}$$

Therefore, the mesh currents, i_1 , i_2 and i_3 are 2 mA, 6 mA and 2 mA respectively.