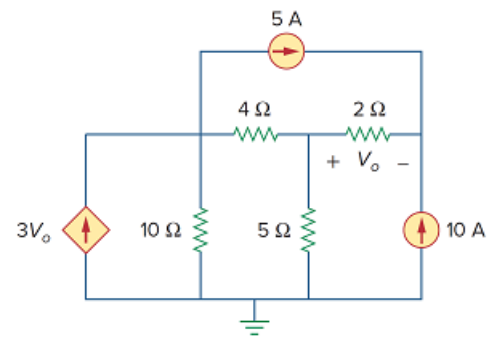


## Problem

Obtain the node-voltage equations for the circuit in Fig. 3.111 by inspection. Then solve for  $V_o$ .

Figure 3.111:



## Step-by-step solution

## Step 1 of 7

Consider the following circuit diagram:

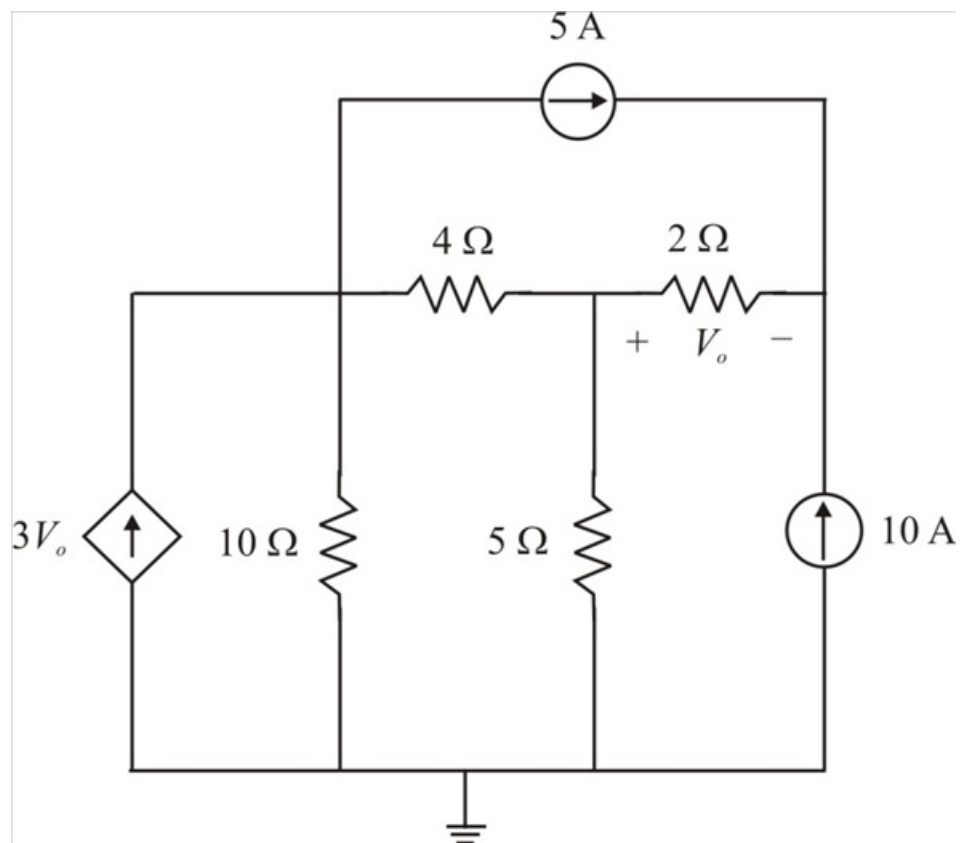


Figure 1

## Step 2 of 7

Label the nodes on the circuit as shown in Figure 2:

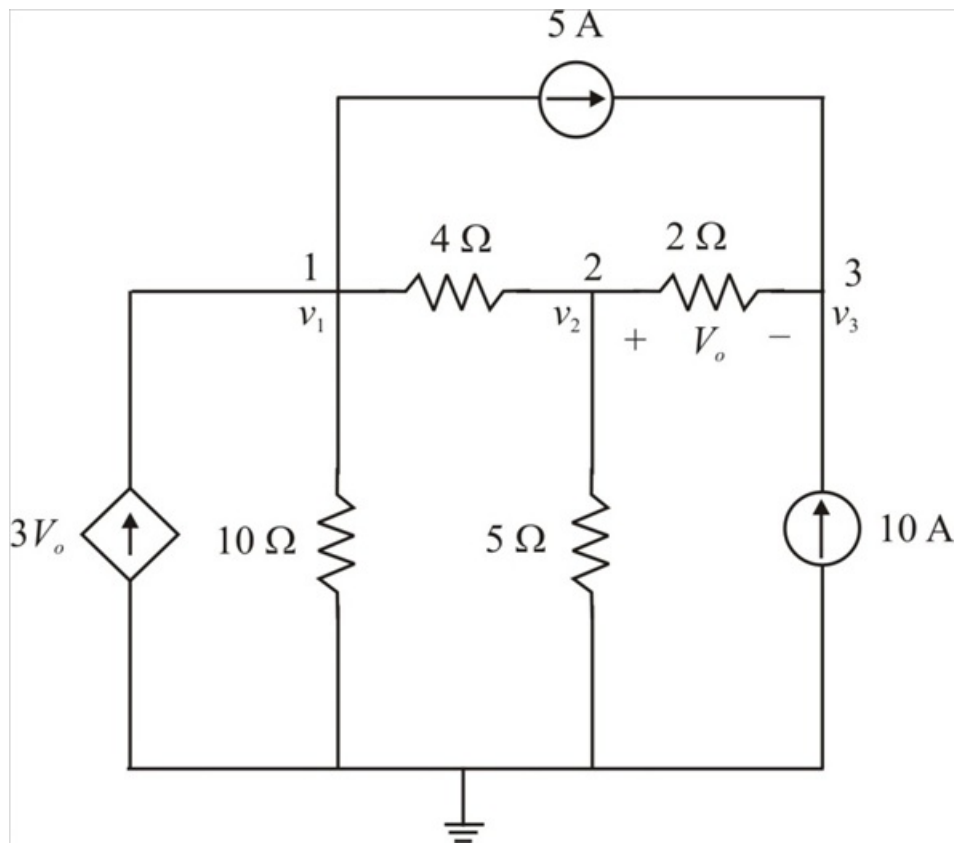


Figure 2

### Step 3 of 7

If a circuit has  $N$  non-reference nodes, the node-voltage equations can be expressed in terms of conductance:

$$\begin{pmatrix} G_{11} & \cdots & G_{1N} \\ \vdots & \ddots & \vdots \\ G_{N1} & \cdots & G_{NN} \end{pmatrix} \begin{pmatrix} v_1 \\ \vdots \\ v_N \end{pmatrix} = \begin{pmatrix} i_1 \\ \vdots \\ i_N \end{pmatrix} \text{ or simply } \mathbf{G}\mathbf{v}=\mathbf{i}.$$

Where,

Sum of the conductance connected to node  $k$  is  $G_{kk}$

Negative of the sum of the conductance directly connecting nodes  $k$  and  $j$ ,  $k \neq j$  is  $G_{kj} = G_{jk}$

Unknown voltage at node  $k$  is  $i_k$

Sum of all independent current sources directly connected to node  $k$ , with currents entering the node treated as positive is  $v_k$ .

### Step 4 of 7

Each of the diagonal terms is the sum of the conductance in the related to node, while each of the off-diagonal terms is the negative of the conductance common to nodes.

The circuit in Figure 1 has three non-reference nodes, so we need three node equations. This implies that the size of the conductance matrix  $\mathbf{G}$ , is 3 by 3.

Find the diagonal terms of  $\mathbf{G}$  in Siemens:

$$G_{11} = \frac{1}{4} + \frac{1}{10}$$

$$= 0.35$$

$$G_{22} = \frac{1}{4} + \frac{1}{2} + \frac{1}{5}$$

$$= 0.95$$

$$G_{33} = \frac{1}{2}$$

$$= 0.5$$

Find the off-diagonal terms in the first row:

$$G_{12} = -\frac{1}{4}$$

$$= -0.25$$

$$G_{13} = 0$$

Find the off-diagonal terms in the second row:

$$G_{21} = -\frac{1}{4}$$

$$= -0.25$$

$$G_{23} = -\frac{1}{2}$$

$$= -0.5$$

Find the off-diagonal terms in the third row:

$$G_{31} = 0$$

$$G_{32} = -\frac{1}{2}$$

$$= -0.5$$

The input current vector  $\mathbf{i}$  has the following terms, in amperes:

$$i_1 = 3v_o - 5$$

$$i_2 = 0$$

$$i_3 = 10 + 5$$

$$= 15$$

Therefore, write the node-voltage equations:

$$\begin{pmatrix} 0.35 & -0.25 & 0 \\ -0.25 & 0.95 & -0.5 \\ 0 & -0.5 & 0.5 \end{pmatrix} \begin{pmatrix} v_1 \\ v_2 \\ v_3 \end{pmatrix} = \begin{pmatrix} 3v_o - 5 \\ 0 \\ 15 \end{pmatrix}$$

Write the first row equation:

$$0.35v_1 - 0.25v_2 = 3v_o - 5$$

$$0.35v_1 - 0.25v_2 = 3(v_2 - v_3) - 5$$

$$0.35v_1 - 0.25v_2 = 3v_2 - 3v_3 - 5$$

$$0.35v_1 - 3.25v_2 + 3v_3 = -5$$

Therefore, the node-voltage equations are

$$\begin{pmatrix} 0.35 & -3.25 & 3 \\ -0.25 & 0.95 & -0.5 \\ 0 & -0.5 & 0.5 \end{pmatrix} \begin{pmatrix} v_1 \\ v_2 \\ v_3 \end{pmatrix} = \begin{pmatrix} -5 \\ 0 \\ 15 \end{pmatrix}.$$

Use Cramer's rule to find the determinant  $\Delta$  of the matrix:

$$\begin{aligned}\Delta &= \begin{vmatrix} 0.35 & -3.25 & 3 \\ -0.25 & 0.95 & -0.5 \\ 0 & -0.5 & 0.5 \end{vmatrix} \\ &= 0.35(0.475 - 0.25) + 0.25(-1.625 + 1.5) + 0 \\ &= 0.35(0.225) + 0.25(-0.125) \\ &= 0.0475\end{aligned}$$

Use Cramer's rule to find determinant  $\Delta_1$  of the matrix:

$$\begin{aligned}\Delta_1 &= \begin{vmatrix} -5 & -3.25 & 3 \\ 0 & 0.95 & -0.5 \\ 15 & -0.5 & 0.5 \end{vmatrix} \\ &= -5(0.475 - 0.25) - 0 + 15(1.625 - 2.85) \\ &= -1.125 - 18.375 \\ &= -19.5\end{aligned}$$

**Step 6** of 7

Use Cramer's rule to find determinant  $\Delta_2$  of the matrix:

$$\begin{aligned}\Delta_2 &= \begin{vmatrix} 0.35 & -5 & 3 \\ -0.25 & 0 & -0.5 \\ 0 & 15 & 0.5 \end{vmatrix} \\ &= 0.35(0 + 7.5) + 0.25(-2.5 - 45) + 0 \\ &= 2.625 - 11.875 \\ &= -9.25\end{aligned}$$

Use Cramer's rule to find determinant  $\Delta_3$  of the matrix:

$$\begin{aligned}\Delta_3 &= \begin{vmatrix} 0.35 & -3.25 & -5 \\ -0.25 & 0.95 & 0 \\ 0 & -0.5 & 15 \end{vmatrix} \\ &= 0.35(14.25 + 0) + 0.25(-48.75 - 2.5) + 0 \\ &= 4.9875 - 12.8125 \\ &= -7.825\end{aligned}$$

**Step 7** of 7

Calculate the node-voltage  $v_1$ :

$$\begin{aligned}v_1 &= \frac{\Delta_1}{\Delta} \\&= \frac{-19.5}{0.0475} \\&= -410.52 \text{ V}\end{aligned}$$

Calculate the node-voltage  $v_2$ :

$$\begin{aligned}v_2 &= \frac{\Delta_2}{\Delta} \\&= \frac{-9.25}{0.0475} \\&= -194.73 \text{ V}\end{aligned}$$

Calculate the node-voltage  $v_3$ :

$$\begin{aligned}v_3 &= \frac{\Delta_3}{\Delta} \\&= \frac{-7.825}{0.0475} \\&= -164.73 \text{ V}\end{aligned}$$

Calculate the voltage  $V_o$ :

$$\begin{aligned}V_o &= v_2 - v_3 \\&= -194.73 - (-164.73) \\&= -30 \text{ V}\end{aligned}$$

Therefore, the voltage  $V_o$  is -30 V.