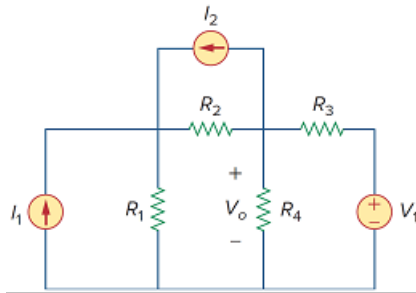


Problem

Using Fig. 3.112, design a problem, to solve for V_o , to help other students better understand nodal analysis. Try your best to come up with values to make the calculations easier.


Figure 3.112:



Step-by-step solution

Step 1 of 7

Considering the circuit

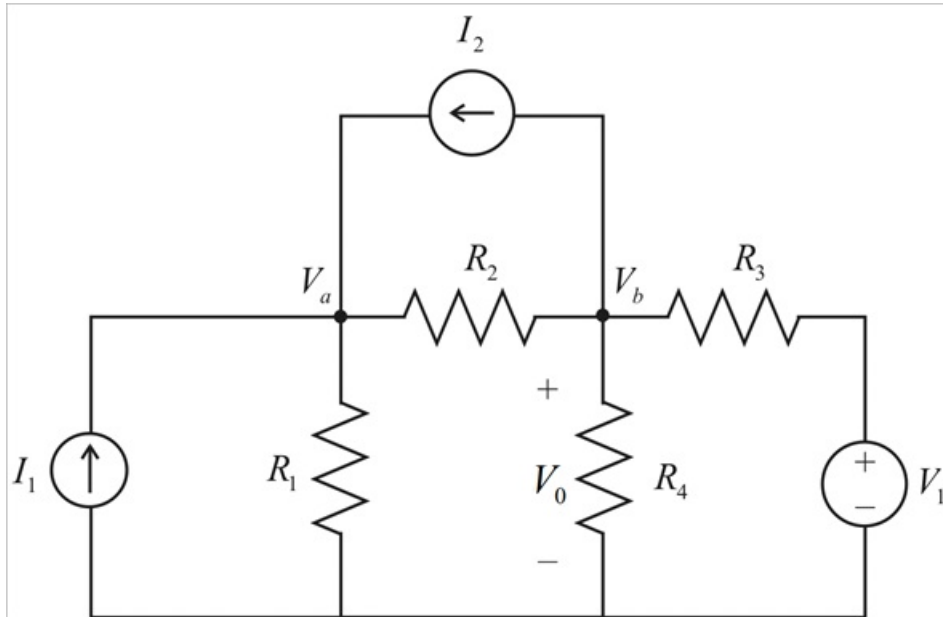

Step 2 of 7

By applying KCL at node a we get

$$-I_1 + \frac{V_a}{R_1} + \frac{V_a - V_b}{R_2} - I_2 = 0$$

$$-I_1 + \frac{V_a}{R_1} + \frac{V_a}{R_2} + \frac{-V_b}{R_2} - I_2 = 0$$

$$-I_1 + V_a \left(\frac{1}{R_1} + \frac{1}{R_2} \right) - \frac{V_b}{R_2} - I_2 = 0$$

$$-I_1 + V_a \left(\frac{R_1 + R_2}{R_1 R_2} \right) - \frac{V_b}{R_2} - I_2 = 0 \dots\dots (1)$$

Step 3 of 7

By applying KCL at node b we get

$$I_2 + \frac{V_b}{R_4} + \frac{V_b - V_a}{R_2} + \frac{V_b - V_1}{R_3} = 0$$

$$I_2 + \frac{V_b}{R_4} + \frac{V_b}{R_2} + \frac{V_b}{R_3} - \frac{V_a}{R_2} - \frac{V_1}{R_3} = 0$$

$$I_2 + V_b \left(\frac{1}{R_4} + \frac{1}{R_2} + \frac{1}{R_3} \right) - \frac{V_a}{R_2} - \frac{V_1}{R_3} = 0 \dots\dots (2)$$

Step 4 of 7

By simplifying equation (1) we get

$$-R_1 R_2 I_1 + V_a R_2 + R_1 V_a - R_1 V_b - R_1 R_2 I_2 = 0$$

$$V_a (R_1 + R_2) = R_1 R_2 I_1 + R_1 V_b + R_1 R_2 I_2$$

$$V_a = \frac{R_1 R_2 I_1 + R_1 V_b + R_1 R_2 I_2}{R_1 + R_2} \dots\dots (3)$$

Step 5 of 7

Substituting V_a in equation (2) then we get

$$I_2 + V_b \left(\frac{1}{R_4} + \frac{1}{R_2} + \frac{1}{R_3} \right) - \frac{V_a}{R_2} - \frac{V_1}{R_3} = 0$$

$$I_2 + V_b \left(\frac{R_2 R_3 + R_4 R_3 + R_2 R_4}{R_2 R_3 R_4} \right) - \frac{V_a}{R_2} - \frac{V_1}{R_3} = 0$$

$$I_2 R_2 R_3 R_4 + V_b (R_2 R_3 + R_4 R_3 + R_2 R_4) - V_a R_3 R_4 - V_1 R_2 R_4 = 0$$

Step 6 of 7

From (3) we have $V_a = \frac{R_1 R_2 I_1 + R_1 V_b + R_1 R_2 I_2}{R_1 + R_2}$

By substituting this value we get

$$I_2 R_2 R_3 R_4 + V_b (R_2 R_3 + R_4 R_3 + R_2 R_4) - \left(\frac{R_1 R_2 I_1 + R_1 V_b + R_1 R_2 I_2}{R_1 + R_2} \right) R_3 R_4 - V_1 R_2 R_4 = 0$$

$$\Rightarrow R_2 R_3 R_4 I_2 + R_2 R_3 V_b + R_3 R_4 V_b + R_2 R_4 V_b - R_3 R_4 \left[\frac{R_1 R_2 I_1 + R_1 V_b + R_1 R_2 I_2}{R_1 + R_2} \right] - R_2 R_4 V_1 = 0$$

$$\Rightarrow R_2 R_3 R_4 I_2 + R_2 R_3 V_b + R_3 R_4 V_b + R_2 R_4 V_b + \frac{-R_3 R_4 R_1 R_2 I_1 - R_3 R_4 R_1 R_2 V_b - R_3 R_4 R_1 R_2 I_2}{R_1 + R_2} - R_2 R_4 V_1 = 0$$

Step 7 of 7

$$\Rightarrow (R_1 + R_2)(R_2 R_3 R_4 I_2) + (R_1 + R_2)(R_2 R_3 V_b) + (R_1 + R_2)(R_3 R_4 V_b) + (R_1 + R_2)(R_2 R_4 V_b) - R_3 R_4 R_1 R_2 I_1 - R_3 R_4 R_1 V_b - R_3 R_4 R_1 R_2 I_2 - (R_1 + R_2)(R_2 R_4 V_1) = 0$$

$$\Rightarrow R_1 R_2 R_3 R_4 I_2 + R_2^2 R_3 R_4 I_2 + R_1 R_2 R_3 V_b + R_2^2 R_3 V_b + R_1 R_3 R_4 V_b + R_2 R_3 R_4 V_b + R_1 R_2 R_4 V_1 + R_2^2 R_4 V_1 - R_1 R_2 R_3 R_4 I_1 - R_1 R_3 R_4 V_b - R_1 R_2 R_3 R_4 I_2 + R_1 R_2 R_4 V_b + R_2^2 R_4 V_b + R_1 R_2 R_3 I_2 + R_2 R_3 R_4 I_2 = 0$$

$$\Rightarrow R_2^2 R_3 R_4 I_2 + R_1 R_2 R_3 V_b + R_2^2 R_3 V_b + R_2 R_3 R_4 V_b + R_1 R_2 R_4 V_1 + R_2^2 R_4 V_1 - R_1 R_2 R_3 R_4 I_1 + R_1 R_2 R_4 V_b + R_2^2 R_4 V_b + R_1 R_2 R_3 I_2 + R_2 R_3 R_4 I_2 = 0$$

$$\Rightarrow R_2^2 R_3 R_4 I_2 + (R_1 R_2 R_3 + R_2^2 R_3 + R_2 R_3 R_4 + R_1 R_2 R_4 + R_2^2 R_4) V_b - R_1 R_2 R_4 V_1 - R_2^2 R_4 V_1 - R_2^2 R_3 R_4 I_2 - R_1 R_2 R_3 R_4 I_1 = 0$$

$$\Rightarrow (R_1 R_2 R_3 + R_2^2 R_3 + R_2 R_3 R_4 + R_1 R_2 R_4 + R_2^2 R_4) V_b = \left(-R_2^2 R_3 R_4 I_2 + R_1 R_2 R_4 V_1 + R_2^2 R_4 V_1 + R_1 R_2 R_3 R_4 I_1 \right)$$

$$\Rightarrow V_b = \frac{-R_2^2 R_3 R_4 I_2 + R_1 R_2 R_4 V_1 + R_2^2 R_4 V_1 + R_1 R_2 R_3 R_4 I_1}{(R_1 R_2 R_3 + R_2^2 R_3 + R_2 R_3 R_4 + R_1 R_2 R_4 + R_2^2 R_4)}$$

From the circuit the output voltage is

$$\Rightarrow V_0 = V_b$$

$$\therefore V_0 = \frac{-R_2^2 R_3 R_4 I_2 + R_1 R_2 R_4 V_1 + R_2^2 R_4 V_1 + R_1 R_2 R_3 R_4 I_1}{(R_1 R_2 R_3 + R_2^2 R_3 + R_2 R_3 R_4 + R_1 R_2 R_4 + R_2^2 R_4)}$$