

Problem

Use *PSpice* or *MultiSim* to solve Prob. 3.58.

Step-by-step solution

Step 1 of 1

Schematics netlist

R - R4 \$ N_0002 \$ N_0001 30

R - R2 \$ N_0001 \$ N_0003 10

R - R1 \$ N_0005 \$ N_0004 30

R - R3 \$ N_0003 \$ N_0004 10

R - R5 \$ N_0003 \$ N_0004 30

V - V4 \$N-0003 0 120 V

V - V3 \$N-0005 \$N- 0001 0

V - V2 0 \$N- 0006 0

V - V1 0 \$N - 0002 0

