

Problem

Use *PSpice* or *MultiSim* to solve Prob. 3.27.

Step-by-step solution

Step 1 of 1

Schematics netlist:-

I – I2 0 \$N_0001 DC 4A

R – R1 \$ N_0002 \$N_0001 0.25

R – R3 \$ N_0003 \$N_0001 1

R – R2 \$ N_0002 \$N_0003 1

F – F1 \$ N_0002 \$N_0001 VF – F1 3


VF – F1 \$ N_0003 \$N_0004 0V

R – R4 0 \$N_0002 0.5

R – R6 0 \$N_0001 0.5

I – I1 0 \$N_0002 DC 2A

R – R5 0 \$N_0004 0.25

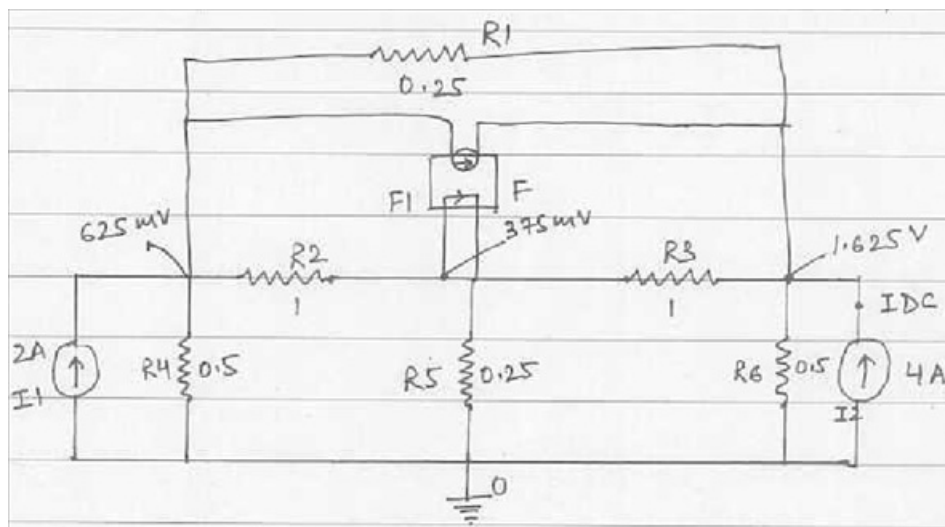

Clearly,

$$V_1 = 625 \text{ mVolts} , \quad V_2 = 375 \text{ mVolts} , \quad V_3 = 1.625 \text{ Volts} .$$

Which agrees with the solution obtained in problem 3.27 .