

## Problem


Solve Prob. 3.20 using *PSpice* or *MultiSim*.

## Step-by-step solution
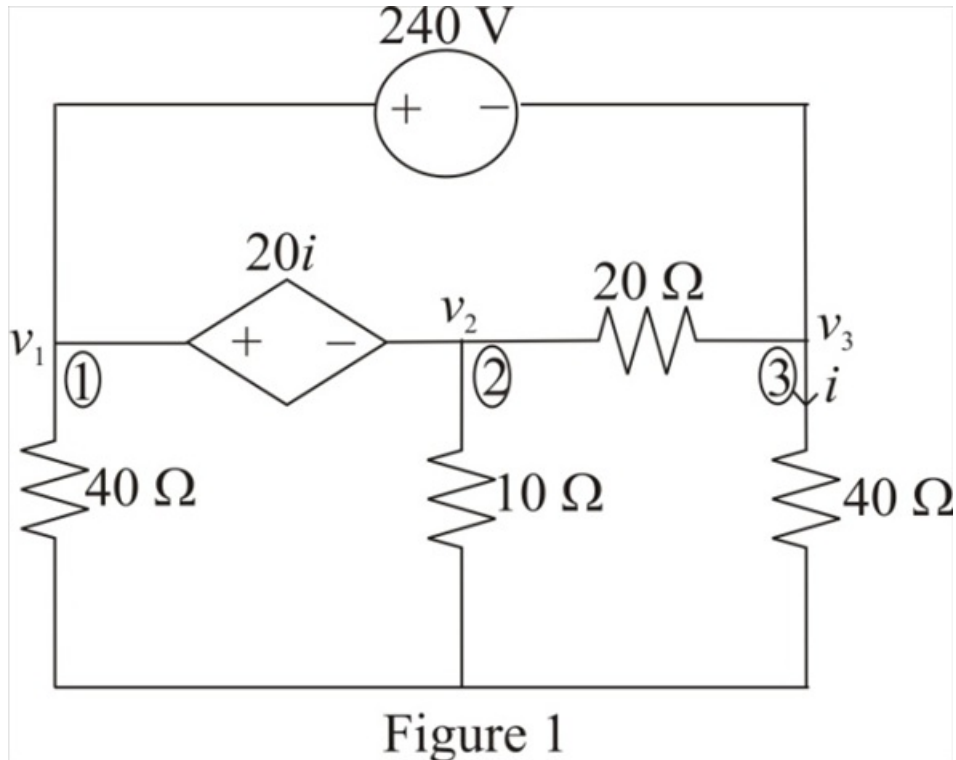
## Step 1 of 10

Refer to Figure 3.69 in the text book.

Identify the nodes and voltage in the circuit shown in Figure 1.



## Step 2 of 10

Notice that the nodes 1, 2 and 3 represent the super node.

Consider the relation between the voltages  $v_1$  and  $v_3$ .

$$v_1 - v_3 = 240$$

$$v_3 = -240 + v_1 \dots\dots (1)$$

Therefore, the expression for the voltage  $v_3$  is  $-240 + v_1$ .

## Step 3 of 10

Consider the expression for the current  $i$ .

$$i = \frac{v_3}{40}$$

Therefore, the expression for the current  $i$  is  $\frac{v_3}{40}$ .

**Step 4** of 10

Consider the relation between the voltages  $v_1$  and  $v_2$ .

$$v_1 - v_2 = 20i$$

Substitute  $\frac{v_3}{40}$  for  $i$ .

$$\begin{aligned} v_1 - v_2 &= 20 \left( \frac{v_3}{40} \right) \\ &= \frac{v_3}{2} \end{aligned}$$

Substitute  $-240 + v_1$  for  $v_3$ .

$$v_1 - v_2 = \frac{(-240 + v_1)}{2}$$

$$v_1 - v_2 = -120 + \frac{v_1}{2}$$

$$v_2 = 120 - \frac{v_1}{2} + v_1$$

$$v_2 = \frac{v_1}{2} + 120 \dots\dots (2)$$

Therefore, the expression for the voltage  $v_2$  is  $\frac{v_1}{2} + 120$ .

**Step 5** of 10

Apply super node analysis at nodes 1, 2 and 3.

$$\frac{v_1}{40} + \frac{v_2}{10} + \frac{v_2 - v_3}{20} + \frac{v_3 - v_2}{20} + \frac{v_3}{40} = 0$$

$$\frac{v_1 + 4v_2 + 2v_2 - 2v_3 + 2v_3 - 2v_2 + v_3}{40} = 0$$

$$v_1 + 4v_2 + 2v_2 - 2v_3 + 2v_3 - 2v_2 + v_3 = 0$$

$$v_1 + 4v_2 + v_3 = 0$$

Substitute  $\frac{v_1}{2} + 120$  for  $v_2$  and  $-240 + v_1$  for  $v_3$ .

$$v_1 + 4 \left( \frac{v_1}{2} + 120 \right) + (-240 + v_1) = 0$$

$$v_1 + 2v_1 + 480 - 240 + v_1 = 0$$

$$4v_1 + 240 = 0$$

$$4v_1 = -240$$

$$\begin{aligned} v_1 &= -\frac{240}{4} \\ &= -60 \text{ V} \end{aligned}$$

Therefore, the value of the voltage  $v_1$  is,  $-60 \text{ V}$ .

**Step 6** of 10

Recall equation (1).

$$v_3 = -240 + v_1$$

Substitute  $-60\text{ V}$  for  $v_1$ .

$$\begin{aligned} v_3 &= -240 - 60 \\ &= -300\text{ V} \end{aligned}$$

Therefore, the value of the voltage  $v_3$  is,  $\boxed{-300\text{ V}}$ .

#### Step 7 of 10

Recall equation (2).

$$v_2 = \frac{v_1}{2} + 120$$

Substitute  $-60\text{ V}$  for  $v_1$ .


$$\begin{aligned} v_2 &= \frac{-60}{2} + 120 \\ &= -30 + 120 \\ &= 90\text{ V} \end{aligned}$$

Therefore, the value of the voltage  $v_2$  is,  $\boxed{90\text{ V}}$ .
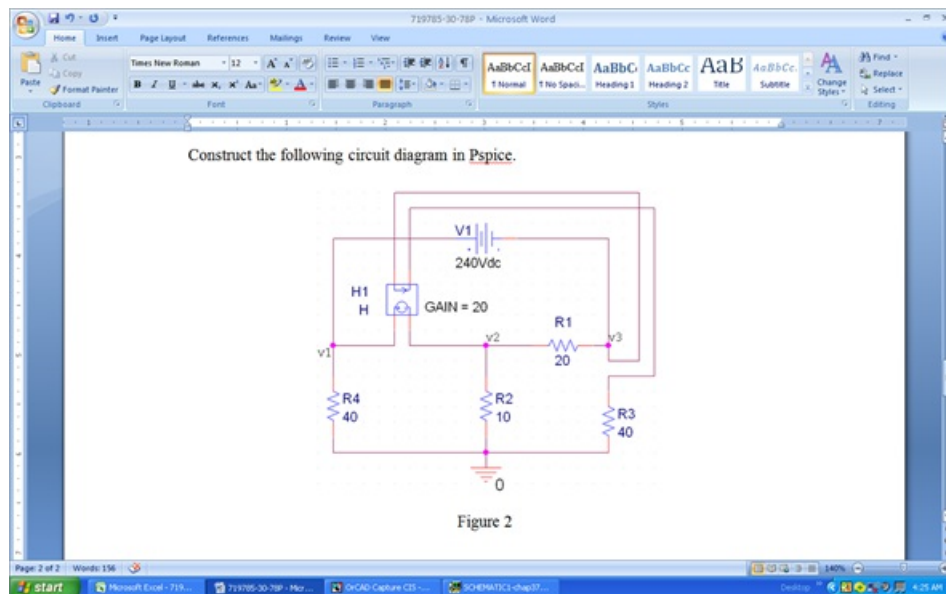
#### Step 8 of 10

Pspice simulation:

Construct the following circuit diagram in Pspice.



#### Step 9 of 10

Go to Pspice and create a new simulation profile. Edit the simulations profile and select 'Bias point' simulation as shown in Figure 3. Click on ok.

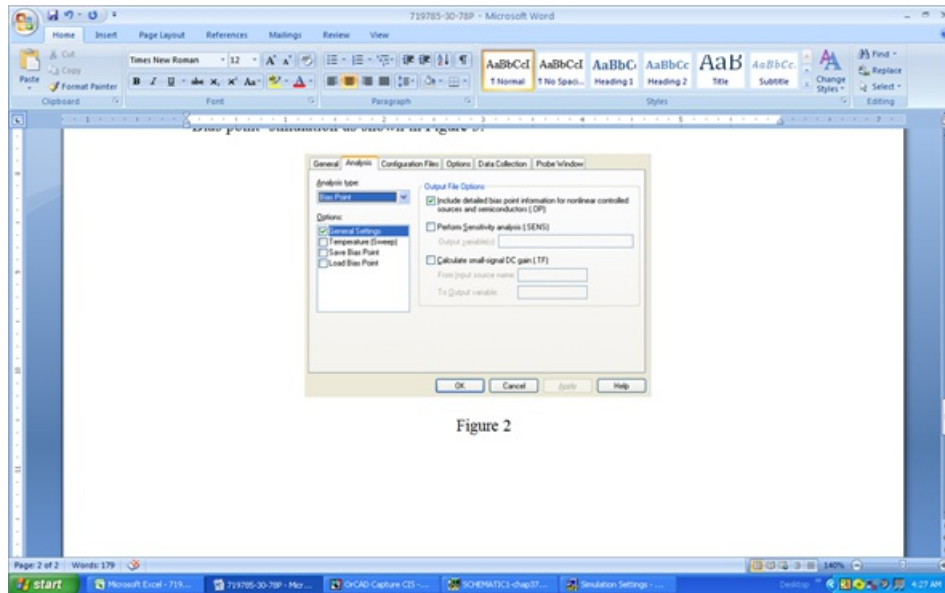


Figure 2

### Step 10 of 10

Click on Voltage bias simulation display. Press F11 to simulate the circuit.

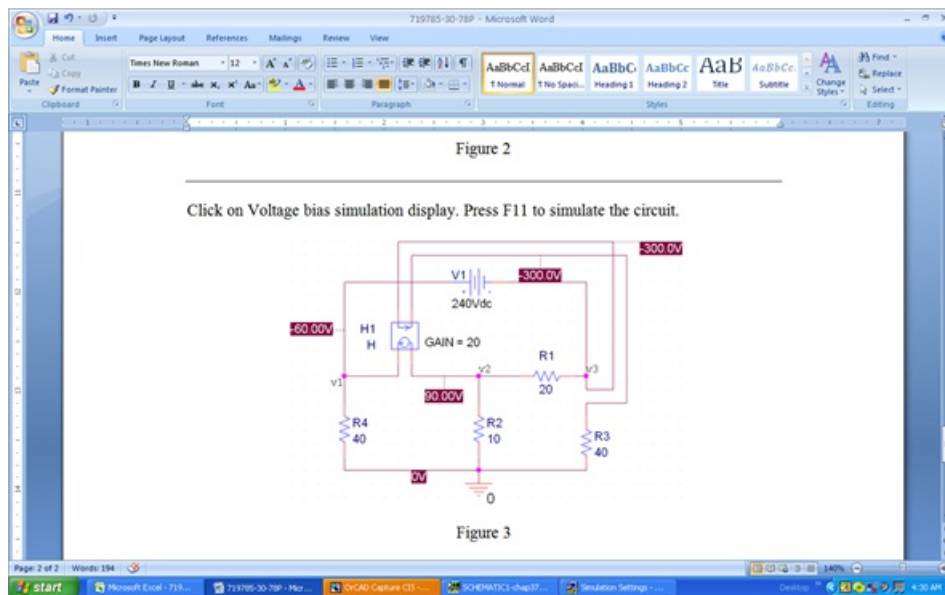


Figure 3

Therefore, the values of the voltages  $v_1$ ,  $v_2$  and  $v_3$  are  $-60\text{ V}$ ,  $90\text{ V}$  and  $-300\text{ V}$  respectively.