


## Problem

Rework Prob. 3.28 using *PSpice* or *MultiSim*.

## Step-by-step solution


## Step 1 of 5

The given circuit is

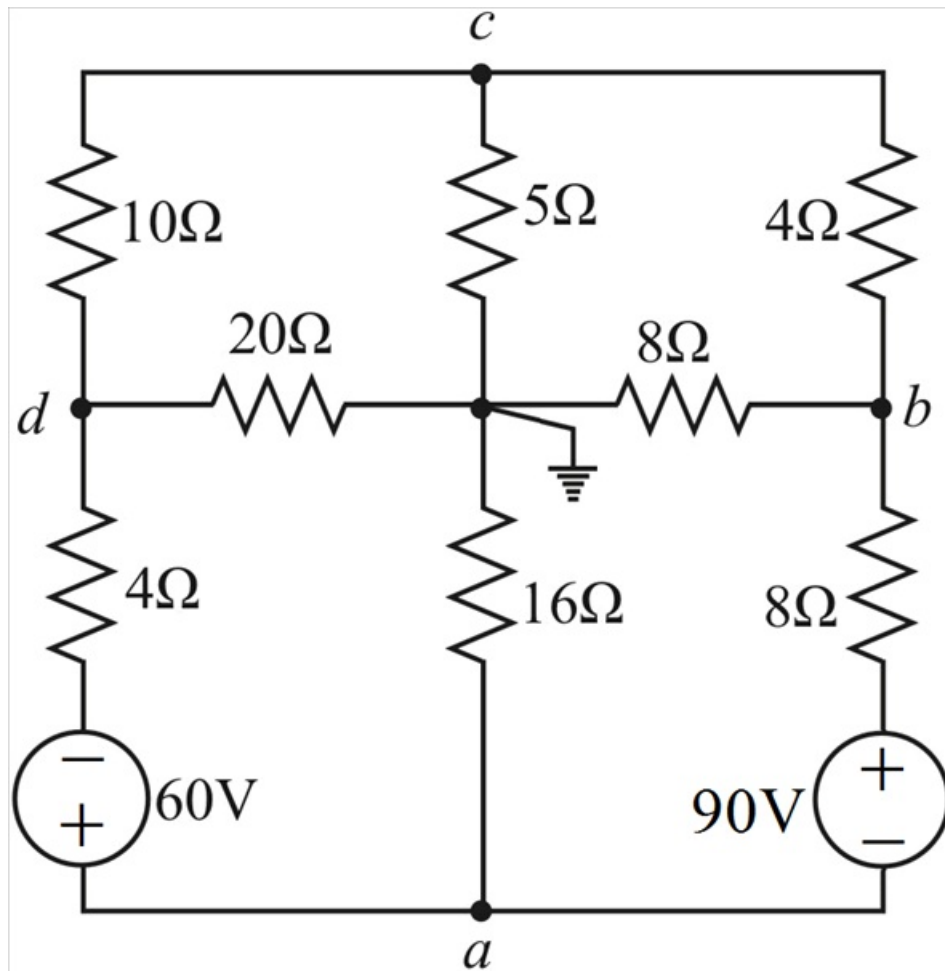
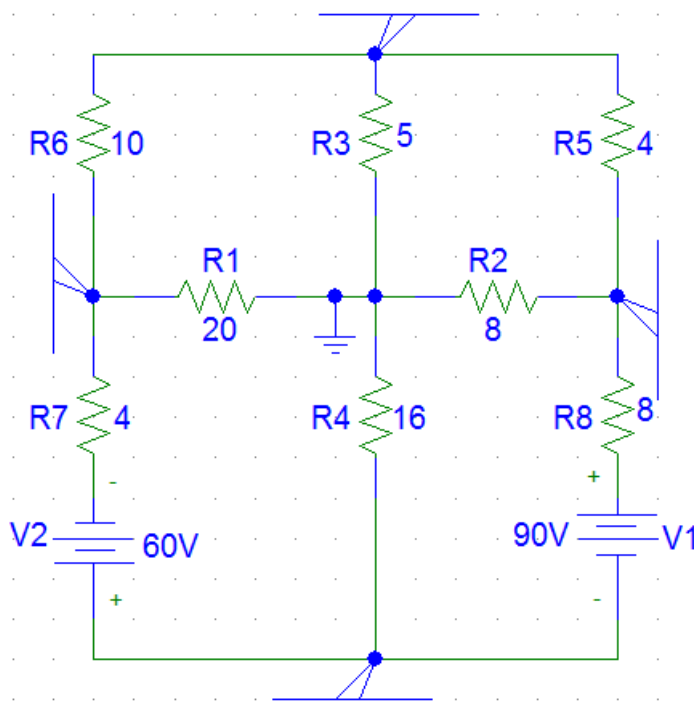
## Step 2 of 5

The first step is to draw the given circuit using schematics as shown:



### Step 3 of 5


Since it is a dc analysis, we use voltage source VDC and current source IDC.

The pseudocomponent VIEWPOINTS are added to display the required node voltages.

Once the circuit is drawn and the file is saved. Now, run PSPICE by selecting **Analysis/Simulate**.

The circuit is simulated and the results are displayed on VIEWPOINTS as shown below and also saved in output file.

### Step 4 of 5

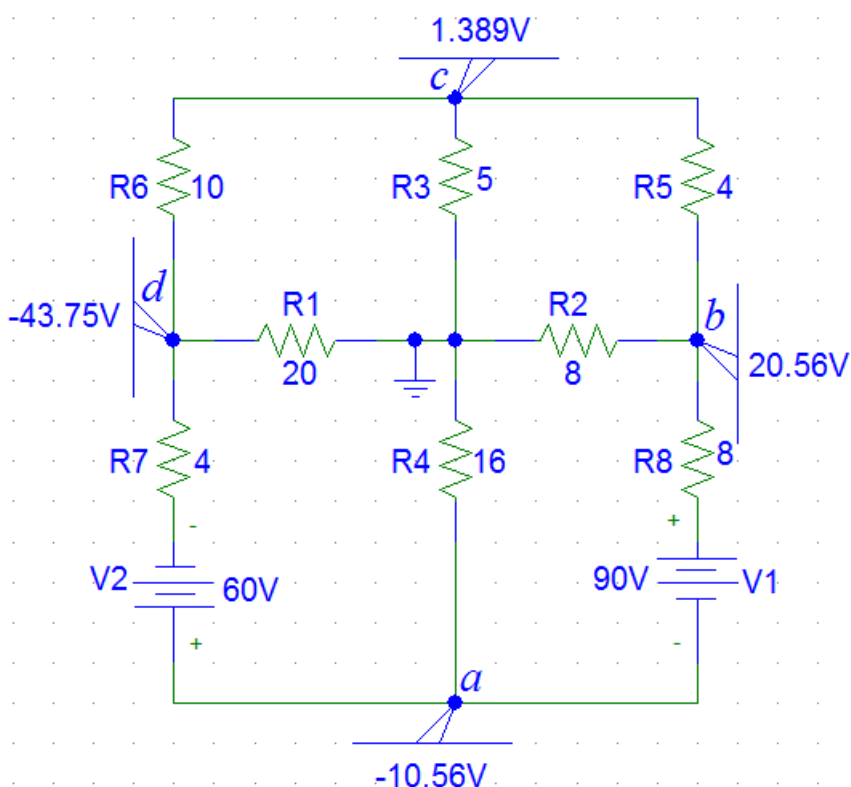

Therefore, from the output file or the VIEWPOINTS, we obtain

$$V_a = -10.56 \text{ V}$$

$$V_b = 20.56 \text{ V}$$

$$V_c = 1.389 \text{ V}$$

$$V_d = -43.75 \text{ V}$$