

Problem

The following program is the Schematics Netlist of a particular circuit. Draw the circuit and determine the voltage at node 2.

```

R_R1  1  2  20
R_R2  2  0  50
R_R3  2  3  70
R_R4  3  0  30
V_VS  1  0  20V
I_IS  2  0  DC   2A

```

Step-by-step solution

Step 1 of 4

From the SPICE code, resistor R_1 is between nodes 1 and 2. Resistor R_2 is between node 2 and ground. Resistor R_3 is between node 2 and node 3. Resistor R_4 is between node 3 and ground. Voltage source V_S is between node 1 and ground. Current source I_S is between node 2 and ground. Draw the circuit diagram.

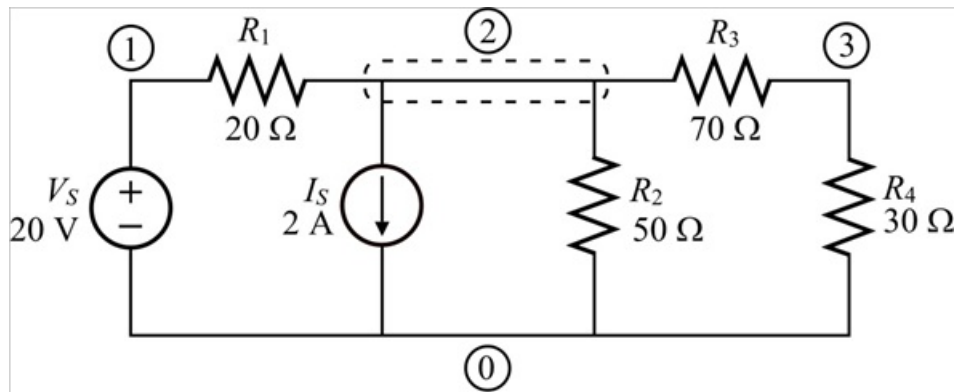


Figure 1

Step 2 of 4

From the circuit shown in Figure 1, the voltage at node 1 $V_1 = 20 \text{ V}$.

Apply Kirchhoff's current law at node 2.

$$\begin{aligned}\frac{V_2 - V_1}{20 \Omega} + 2 \text{ A} + \frac{V_2}{50 \Omega} + \frac{V_2 - V_3}{70 \Omega} &= 0 \\ \frac{V_2 - 20 \text{ V}}{20 \Omega} + 2 \text{ A} + \frac{V_2}{50 \Omega} + \frac{V_2 - V_3}{70 \Omega} &= 0 \quad [\text{since } V_1 = 20 \text{ V}] \\ \left(\frac{1}{20 \Omega} + \frac{1}{50 \Omega} + \frac{1}{70 \Omega} \right) V_2 - \frac{V_3}{70 \Omega} &= \frac{20 \text{ V}}{20 \Omega} - 2 \text{ A} \\ \left(\frac{1}{20 \Omega} + \frac{1}{50 \Omega} + \frac{1}{70 \Omega} \right) V_2 - \frac{V_3}{70 \Omega} &= 1 \text{ A} - 2 \text{ A}\end{aligned}$$

Multiply with 70 on both sides of the equation.

$$\begin{aligned}(70) \left(\frac{1}{20 \Omega} + \frac{1}{50 \Omega} + \frac{1}{70 \Omega} \right) V_2 - (70) \left(\frac{V_3}{70 \Omega} \right) &= (1 \text{ A} - 2 \text{ A})(70) \\ (70)(0.0843) V_2 - V_3 &= (-1 \text{ A})(70) \\ 5.9 V_2 - V_3 &= -70 \text{ V} \dots\dots (1)\end{aligned}$$

Step 3 of 4

Apply Kirchhoff's current law at node 3.

$$\begin{aligned}\frac{V_3 - V_2}{70 \Omega} + \frac{V_3}{30 \Omega} &= 0 \\ -\frac{V_2}{70 \Omega} + \left(\frac{1}{70 \Omega} + \frac{1}{30 \Omega} \right) V_3 &= 0 \\ -\frac{3V_2}{210 \Omega} + \left(\frac{3+7}{210 \Omega} \right) V_3 &= 0 \\ -3V_2 + 10V_3 &= 0 \\ V_3 &= 0.3V_2 \dots\dots (2)\end{aligned}$$

Step 4 of 4

Calculate the voltage at node 2.

Recall equation (1).

$$5.9V_2 - V_3 = -70 \text{ V}$$

Substitute $0.3V_2$ for V_3 .

$$5.9V_2 - 0.3V_2 = -70 \text{ V}$$

$$5.6V_2 = -70 \text{ V}$$

$$\begin{aligned}V_2 &= \frac{-70 \text{ V}}{5.6} \\ &= -12.5 \text{ V}\end{aligned}$$

Therefore, the voltage, V_2 at node 2 is -12.5 V .