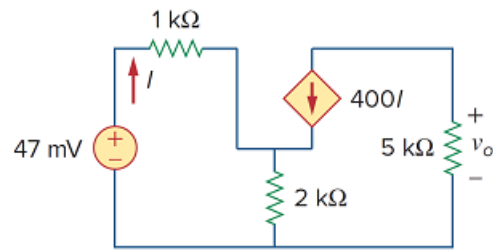


Problem

For the simplified transistor circuit of Fig. 3.122, calculate the voltage v_o .

Figure 3.122:




Step-by-step solution

Step 1 of 3

Refer to Figure 3.122 in the circuit.

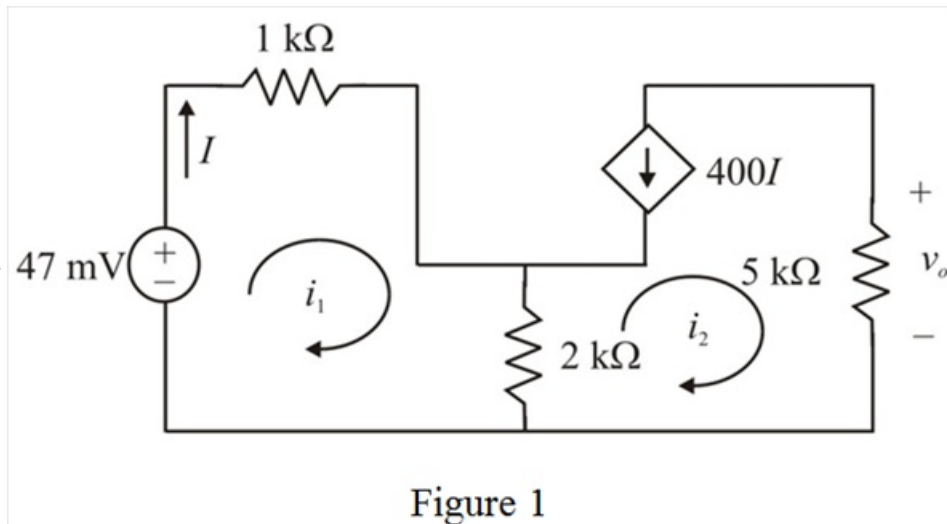Draw the circuit diagram with loop currents.



Step 2 of 3

From Figure 1, it is clear that,

$$I = i_1$$

$$400I = -i_2$$

$$400i_1 = -i_2$$

$$i_2 = -400i_1$$

Apply Kirchhoff's voltage law to loop1.

$$-(47 \times 10^{-3}) + (1 \times 10^3)i_1 + (2 \times 10^3)(i_1 - i_2) = 0$$

$$3 \times 10^3 i_1 - 2 \times 10^3 i_2 = 47 \times 10^{-3}$$

$$3000i_1 - 2000i_2 = 47 \times 10^{-3}$$

$$3i_1 - 2i_2 = 47 \times 10^{-6}$$

Substitute $-400i_1$ for i_2 .

$$3i_1 - 2(-400i_1) = 47 \times 10^{-6}$$

$$803i_1 = 47 \times 10^{-6}$$

$$i_1 = \frac{47 \times 10^{-6}}{803}$$

$$= 58.53 \times 10^{-9}$$

$$= 58.53 \text{ nA}$$

Step 3 of 3

Calculate the value of the current, i_2 .

$$i_2 = -400i_1$$

Substitute 58.53 nA for i_1 .

$$i_2 = -400(58.53 \times 10^{-9})$$

$$= -23.412 \times 10^{-6}$$

$$= -23.412 \text{ } \mu\text{A}$$

Calculate the output voltage.

$$v_o = i_2(5000)$$

Substitute $-23.412 \text{ } \mu\text{A}$ for i_2 .

$$v_o = (-23.412 \times 10^{-6})(5000)$$

$$= -117.06 \times 10^{-3}$$

$$= -117.06 \text{ mV}$$

Thus, the output voltage is $\boxed{-117.06 \text{ mV}}$.