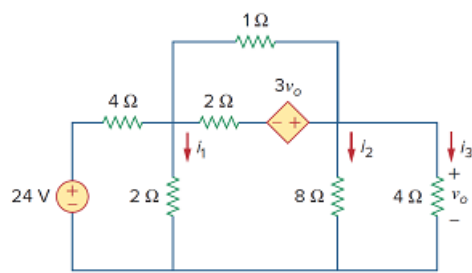


Problem

Rework Example 3.11 with hand calculation.

Example 3.11:


In the circuit of Fig. 3.34, determine the currents i_1 , i_2 , and i_3 .

Figure 3.34:**Solution:**

The schematic is shown in Fig. 3.35. (The schematic in Fig. 3.35 includes the output results, implying that it is the schematic displayed on the screen *after* the simulation.) Notice that the voltage-controlled voltage source E1 in Fig. 3.35 is connected so that its input is the voltage across the 4-Ω resistor; its gain is set equal to 3. In order to display the required currents, we insert pseudocomponent IPROBES in the appropriate branches. The schematic is saved as *exam311.sch* and simulated by selecting **Analysis/Simulate**. The results are displayed on IPROBES as shown in Fig. 3.35 and saved in output file *exam311.out*. From the output file or the IPROBES, we obtain $i_1 = i_2 = 1.333$ A and $i_3 = 2.667$ A.


Figure 3.35

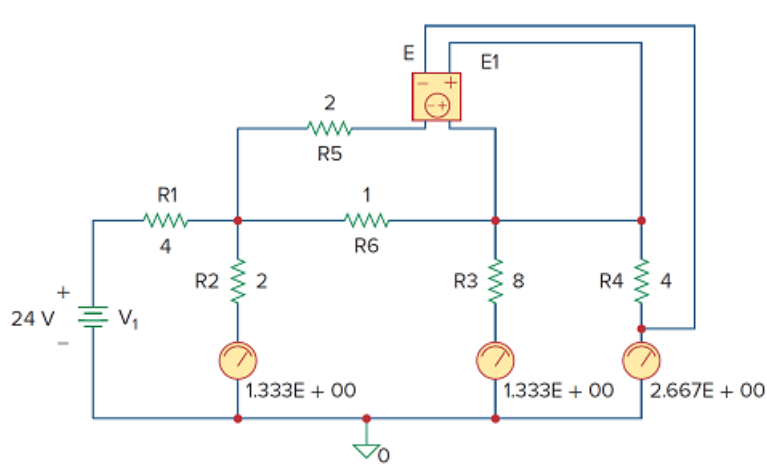The schematic of the circuit in Fig. 3.34.



Step-by-step solution

Step 1 of 1

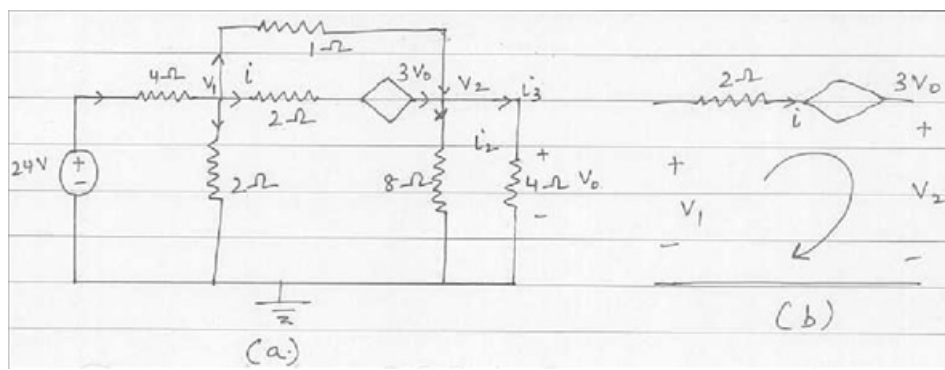

From (b),

$$-V_1 + 2i - 3V_0 + V_2 = 0 \quad \text{Which leads to} \quad i = \frac{(V_1 + 3V_0 - V_2)}{2}$$

At node 1 in (a),

$$\left(\frac{24 - V_1}{4} \right) = \left(\frac{V_1}{2} \right) + \left(\frac{(V_1 + 3V_0 - V_2)}{2} \right) + \left(\frac{(V_1 - V_2)}{1} \right),$$

Where $V_0 = V_2$ Or,

$24 = 9V$, Which leads to $V_1 = 2.667$ Volts.

At node 2,

$$\left(\frac{(V_1 - V_2)}{1} \right) + \left(\frac{(V_1 + 3V_0 - V_2)}{2} \right) = \left(\frac{V_2}{8} \right) + \left(\frac{V_2}{4} \right), \quad V_0 = V_2,$$

$$V_2 = 4V_1 = 10.66 \text{ Volts}.$$

Now we can solve for the currents,

$$i_1 = \frac{V_1}{2} = 1.333 \text{ A},$$

$$i_2 = 1.333 \text{ A} \quad \text{And}$$

$$i_3 = 2.6667 \text{ A}.$$