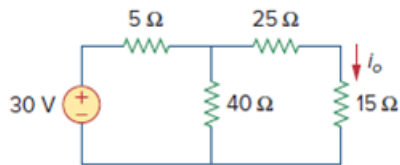


Problem

Calculate the current i_o in the circuit of Fig. 4.69. What value of input voltage is necessary to make i_o equal to 5 amps?

Figure. 4.69:



Step-by-step solution

Step 1 of 3

Refer to Figure 4.69 in the textbook.

Redraw the circuit diagram showing with loop currents are shown in Figure 1.

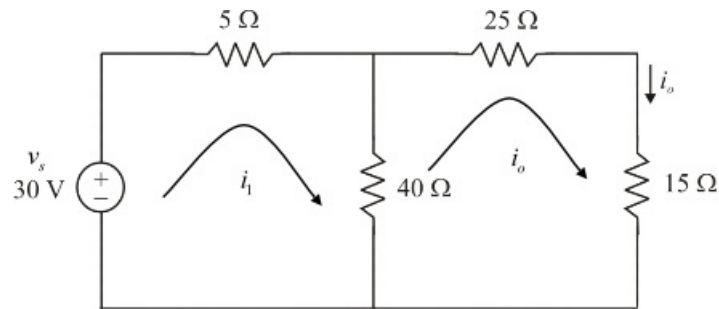


Figure 1

Step 2 of 3

Apply Kirchhoff's voltage law to loop 1 in Figure 1.

$$-v_s + 5i_1 + 40(i_1 - i_o) = 0$$

$$45i_1 - 40i_o = v_s \quad \dots\dots (1)$$

Apply Kirchhoff's voltage law to loop 2 in Figure 1.

$$40(i_o - i_1) + 25i_o + 15i_o = 0$$

$$80i_o - 40i_1 = 0$$

$$i_1 = 2i_o$$

Substitute $2i_o$ for i_1 in equation (1).

$$45(2i_o) - 40i_o = v_s$$

$$50i_o = v_s \quad \dots\dots (2)$$

Substitute 30 V for v_s in equation (2).

$$50i_o = 30$$

$$i_o = \frac{30}{50}$$

$$= 600 \text{ mA}$$

Therefore, the current i_o is 600 mA.

Step 3 of 3

If $i_o = 5 \text{ A}$, the input voltage is,

From Equation (2)

$$\begin{aligned} v_s &= 50(5) \\ &= 250 \text{ V} \end{aligned}$$

Therefore, the required input voltage v_s , is 250 V.