

Chapter 4, Problem 1RQ

Problem

The current through a branch in a linear network is 2 A when the input source voltage is 10 V. If the voltage is reduced to 1 V and the polarity is reversed, the current through the branch is:

- (a) – 2 A
- (b) – 0.2 A
- (c) 0.2 A
- (d) 2 A
- (e) 20 A

Step-by-step solution

Step 1 of 1

Answer: (b)

- 0.2