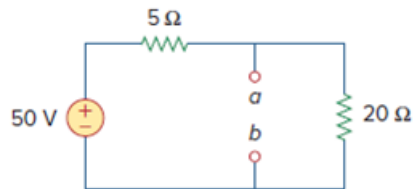


Problem

Refer to Fig. 4.67. The Thevenin resistance at terminals a and b is:

- (a) $25\ \Omega$
- (b) $20\ \Omega$
- (c) $5\ \Omega$
- (d) $4\ \Omega$


Figure. 4.67:



Step-by-step solution

Step 1 of 2

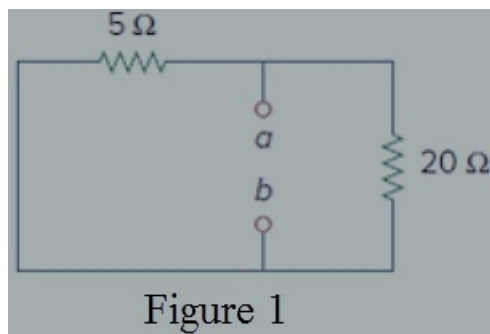Find the Thevenin resistance at terminals a and b by short circuit the voltage source 50 V .



Step 2 of 2

The two resistors $20\ \Omega$ and $5\ \Omega$ are in parallel.

$$R_{th} = \frac{20 \times 5}{20 + 5} \\ = 4\ \Omega$$

Thus, Thevenin resistance at terminals a and b is $4\ \Omega$.

Correct option is **d**.