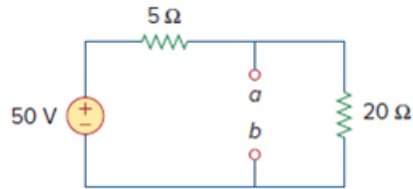


Problem

The Thevenin voltage across terminals a and b of the circuit in Fig. 4.67 is:

- (a) 50 V
- (b) 40 V
- (c) 20 V
- (d) 10 V

Figure. 4.67:



Step-by-step solution

Step 1 of 2

Refer to the circuit diagram in Figure 4.67 in the textbook.

The Thevenin voltage at terminals a and b is same as voltage across $20\ \Omega$ resistor. Since terminals $a - b$ and $20\ \Omega$ resistor are in parallel.

Identify voltage v_T at resistor $20\ \Omega$.

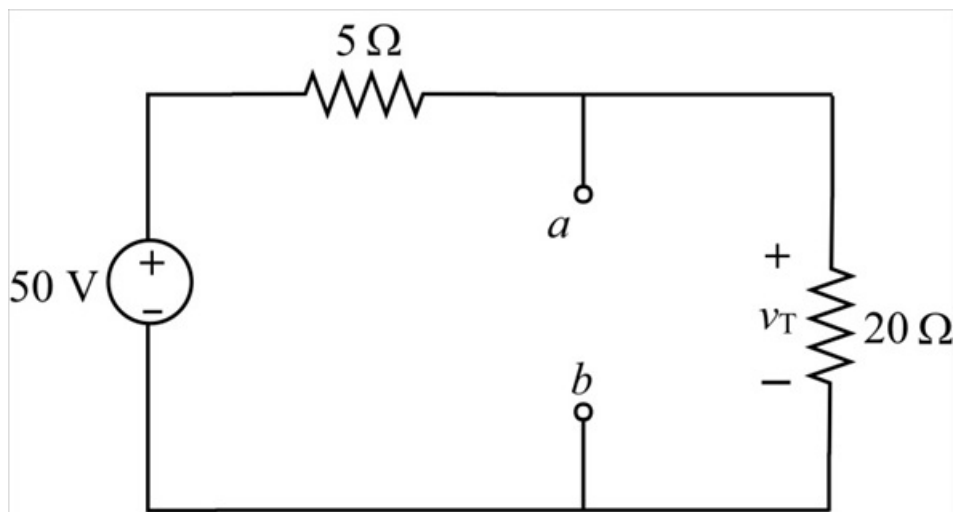


Figure 1

Step 2 of 2

From Figure 1, find the thevenin voltage at terminals a - b using voltage division rule.

$$\begin{aligned}v_T &= 50 \left(\frac{20}{20+5} \right) \\&= 50 \left(\frac{20}{25} \right) \\&= 50 \left(\frac{4}{5} \right) \\&= 40 \text{ V}\end{aligned}$$

Thus, thevenin voltage v_T at the terminals a and b is 40 V .

So correct option is ☒ b.