

Chapter 4, Problem 7RQ

Problem

The Norton resistance R_N is exactly equal to the Thevenin resistance R_{Th} .

- (a) True
- (b) False

Step-by-step solution

Step 1 of 1

Answer: (a)

True