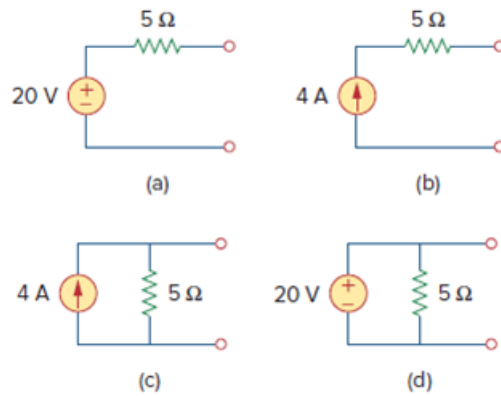


Problem

Which pair of circuits in Fig. 4.68 are equivalent?

- (a) a and b
- (b) b and d
- (c) a and c
- (d) c and d

Figure 4.68:



Step-by-step solution

Step 1 of 1

Answer: (c)

a and c