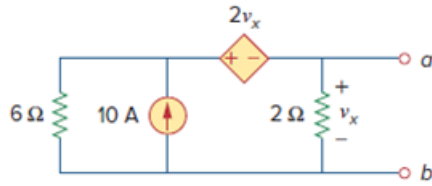


Problem

Find the Norton equivalent circuit of the circuit in Fig. 4.45 at terminals a - b .

Figure. 4.45:



Step-by-step solution

Step 1 of 7

Refer to figure 4.45 given in the textbook.

Short circuit the terminals a and b . And the current flowing through the same short circuited path is $i_{sc} = I_N$ as shown in figure 1.

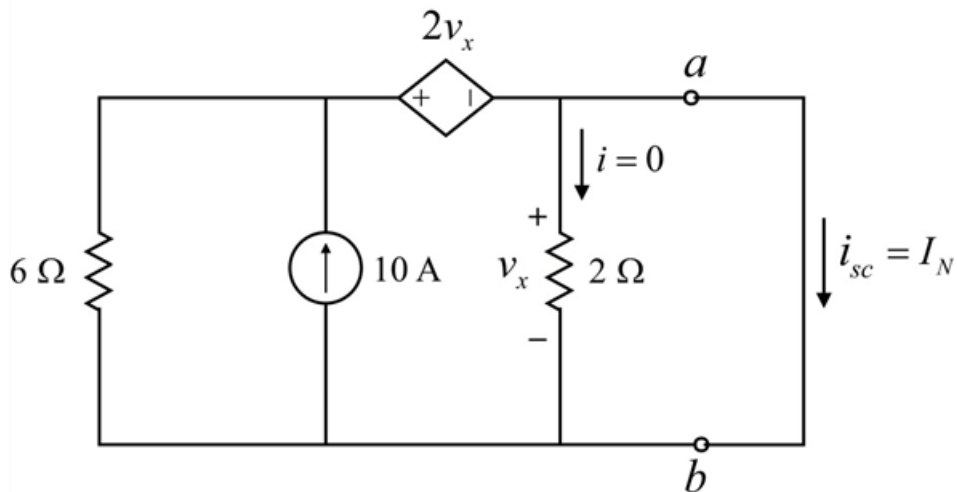


Figure 1

Step 2 of 7

Consider the circuit shown in figure 1.

As no current flows through the resistance of $2\ \Omega$, open circuit it as shown in figure 2.

Also,

$$v_x = 0$$

Short circuit the dependent voltage source of $2v_x$ as shown in figure 2.

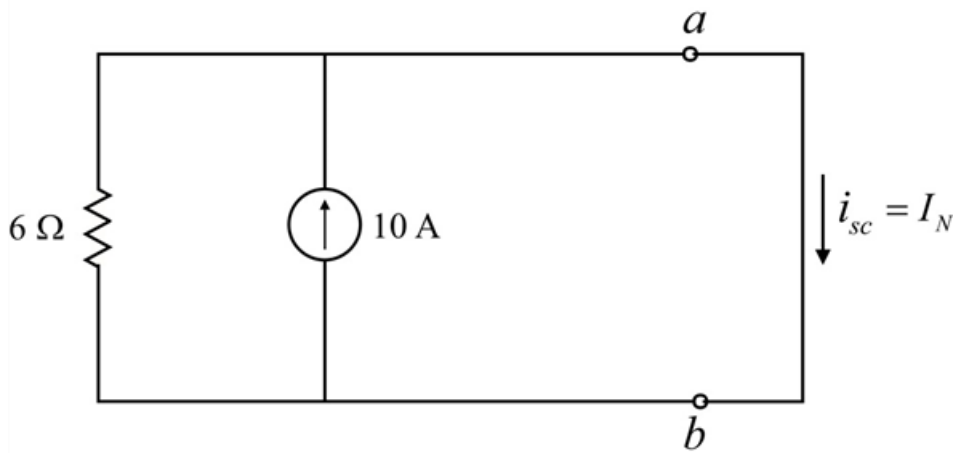


Figure 2

Step 3 of 7

Consider the circuit shown in figure 2.

The current always flow in a low resistance path.

Therefore, the Norton current I_N is 10 A .

Step 4 of 7

Refer to figure 4.45 given in the textbook.

Determine the Norton resistance R_N .

Place a voltage source of 1 V across the terminals a and b as shown in figure 3.

Open circuit the independent current source of 10 A as shown in figure 3.

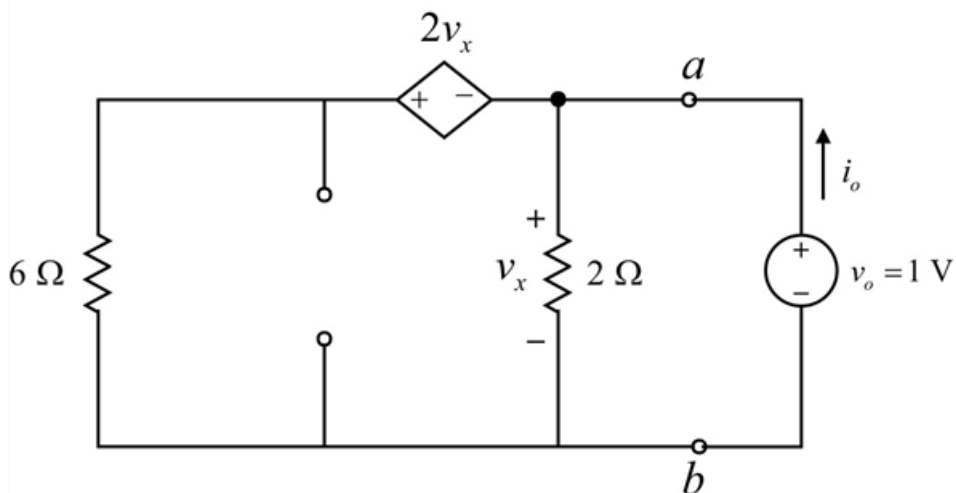


Figure 3

Step 5 of 7

Apply Nodal analysis at node- a .

$$\frac{v_x + 2v_x}{6} + \frac{v_x}{2} - i_o = 0$$

Substitute 1 for v_x .

$$\frac{1 + 2(1)}{6} + \frac{1}{2} - i_o = 0$$

$$i_o = \frac{3}{6} + \frac{1}{2}$$

$$i_o = 1 \text{ A}$$

Step 6 of 7

Calculate the Norton resistance R_N .

$$R_N = \frac{v_o}{i_o}$$

Substitute 1 for i_o , and 1 for v_o .

$$R_N = \frac{1}{1}$$
$$= 1 \Omega$$

Therefore, the Norton resistance R_N is 1Ω .

Step 7 of 7

Draw the Norton equivalent circuit as shown in figure 4.

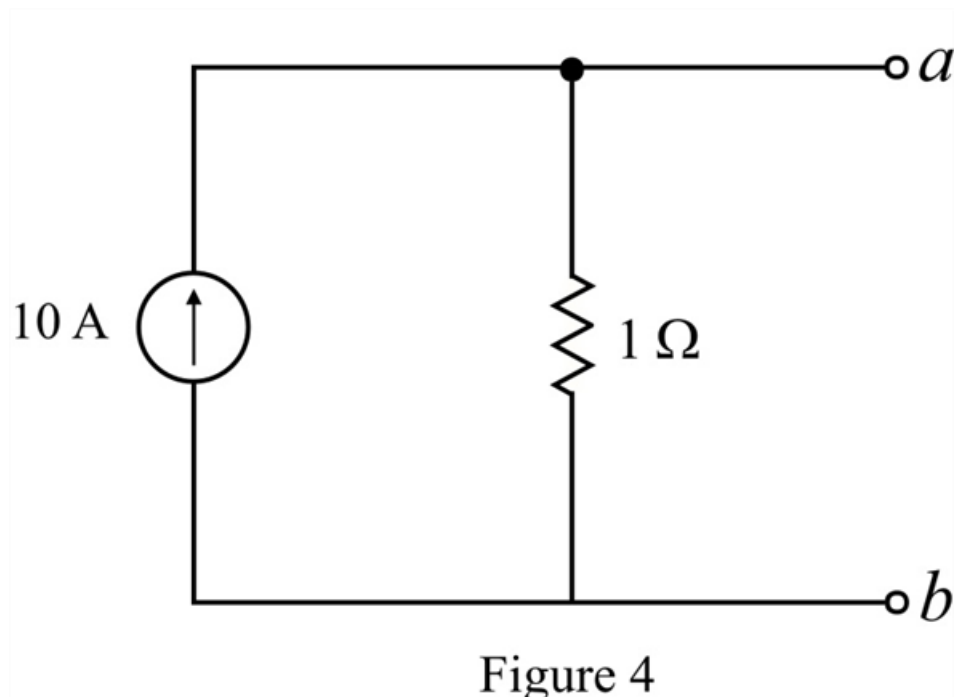


Figure 4