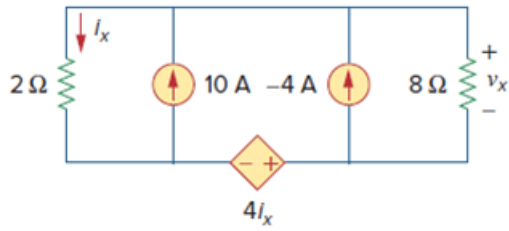


## Problem

Use superposition to solve for  $v_x$  in the circuit of Fig. 4.87.

Figure 4.87:



## Step-by-step solution

## Step 1 of 11

Refer to circuit diagram in Figure 4.87 in the text book.

The circuit has two independent sources, assume that the output voltage is,

$$v_x = V_1 + V_2$$

Here,  $V_1$  and  $V_2$  are the voltage responses due to  $-4$  A current source and  $10$  A current source respectively.

To obtain  $V_1$ , set the  $10$  A current source to zero, the modified circuit is shown in Figure 1.

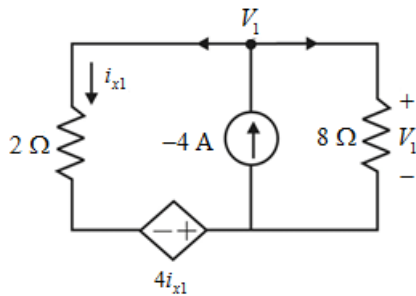


Figure 1

## Step 2 of 11

From the circuit shown in Figure 1, the current  $i_{x1}$  is,

$$i_{x1} = \frac{V_1 - (-4i_{x1})}{2}$$

$$2i_{x1} = V_1 + 4i_{x1}$$

$$-2i_{x1} = V_1$$

$$i_{x1} = -\frac{V_1}{2} \dots\dots (1)$$

Apply nodal analysis at node  $V_1$ .

$$\frac{V_1 - (-4i_{x1})}{2} + \frac{V_1}{8} = -4$$

Substitute  $-\frac{V_1}{2}$  for  $i_{x1}$ .

$$\frac{V_1 + 4\left(-\frac{V_1}{2}\right)}{2} + \frac{V_1}{8} = -4$$

$$\frac{V_1 - 2V_1}{2} + \frac{V_1}{8} = -4$$

$$\frac{-4V_1 + V_1}{8} = -4$$

$$-3V_1 = -32$$

$$V_1 = \frac{32}{3} \text{ V}$$

### Step 3 of 11

To obtain  $V_2$ , set the  $-4 \text{ A}$  current source to zero, the modified circuit is shown in Figure 2.

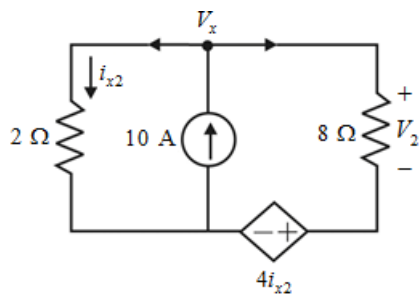


Figure 2

### Step 4 of 11

From the circuit shown in Figure 2, the current  $i_{x2}$  is,

$$i_{x2} = \frac{V_x}{2} \dots\dots (2)$$

Apply nodal analysis at node  $V_x$ .

$$\frac{V_x}{2} + \frac{V_x - 4i_{x2}}{8} = 10$$

Substitute  $\frac{V_x}{2}$  for  $i_{x2}$ .

$$\frac{V_x}{2} + \frac{V_x - 4\left(\frac{V_x}{2}\right)}{8} = 10$$

$$\frac{V_x}{2} + \frac{V_x - 2V_x}{8} = 10$$

$$\frac{4V_x - V_x}{8} = 10$$

$$3V_x = 80$$

$$V_x = \frac{80}{3}$$

#### Step 5 of 11

Apply Kirchhoff's voltage law to the right side loop.

$$-V_x + V_2 + 4i_{x2} = 0$$

Substitute  $\frac{V_x}{2}$  for  $i_{x2}$ .

$$-V_x + V_2 + 4\left(\frac{V_x}{2}\right) = 0$$

$$-V_x + V_2 + 2V_x = 0$$

$$V_2 + V_x = 0$$

$$V_2 = -V_x$$

$$V_2 = -\frac{80}{3} \text{ V}$$

Now, calculate the voltage  $v_x$  due to both sources acting.

$$v_x = V_1 + V_2$$

Substitute  $\frac{32}{3} \text{ V}$  for  $V_1$ , and  $-\frac{80}{3} \text{ V}$  for  $V_2$ .

$$v_x = \frac{32}{3} - \frac{80}{3} \text{ V}$$

$$= -\frac{48}{3} \text{ V}$$

$$= -16 \text{ V}$$

Therefore, the voltage  $v_x$  in the circuit is -16 V.

#### Step 6 of 11

ORCAD simulation:

Let the  $-4\text{ A}$  current source be active and disconnect the  $10\text{ A}$  current source.

Construct the circuit diagram in ORCAD as shown in Figure 3.

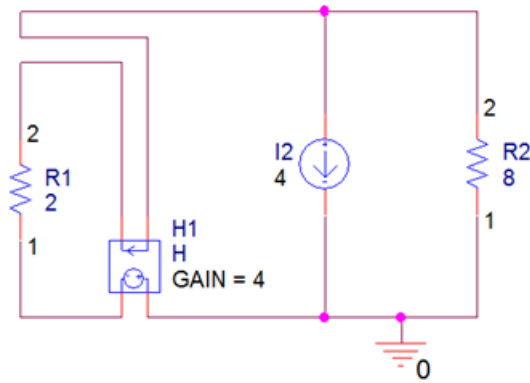


Figure 3

#### Step 7 of 11

Go to Pspice and create a new simulation profile. Edit the simulations profile and select 'Bias point' simulation as shown in Figure 4. Click on ok.

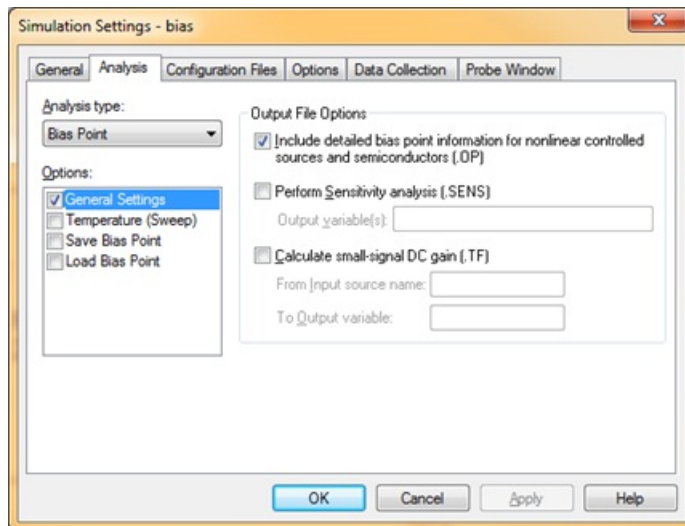


Figure 4

#### Step 8 of 11

Click on voltage bias simulation display. Press F11 to simulate the circuit.

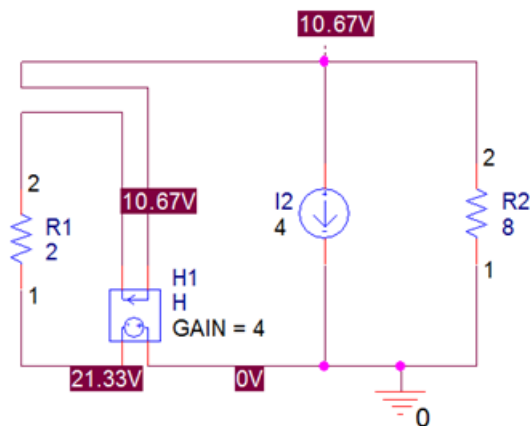


Figure 5

The value of the voltage  $v_{x1}$  due to  $-4\text{ A}$  current source is  $10.67\text{ V}$ .

#### Step 9 of 11

Let the  $10\text{ A}$  current source be active and disconnect the  $-4\text{ A}$  current source.

Construct the circuit diagram in ORCAD as shown in Figure 6.

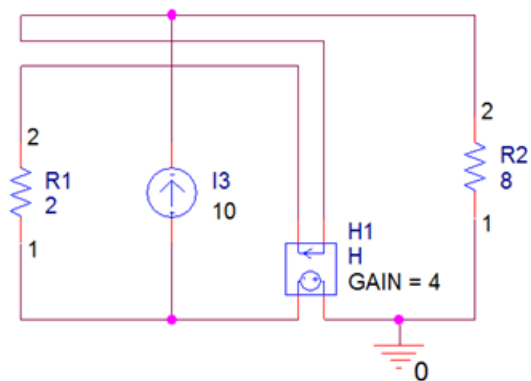


Figure 6

#### Step 10 of 11

Click on voltage bias simulation display. Press F11 to simulate the circuit.

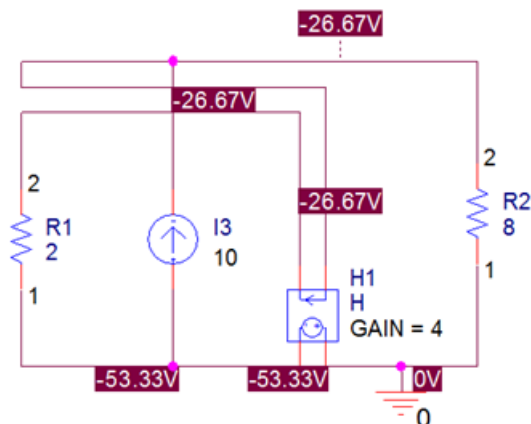


Figure 7

The value of the voltage  $v_{x2}$  due to  $10\text{ A}$  current source is  $-26.67\text{ V}$ .

#### Step 11 of 11

Calculate the value of the voltage  $v_x$  due to both sources activated.

$$v_x = v_{x1} + v_{x2}$$

Substitute  $10.67 \text{ V}$  for  $v_{x1}$  and  $-26.66 \text{ V}$  for  $v_{x2}$ .

$$\begin{aligned} v_x &= 10.67 - 26.67 \text{ V} \\ &= -16 \text{ V} \end{aligned}$$

Therefore, the value of the voltage,  $v_x$  due to both sources activated is  $\boxed{-16 \text{ V}}$ .