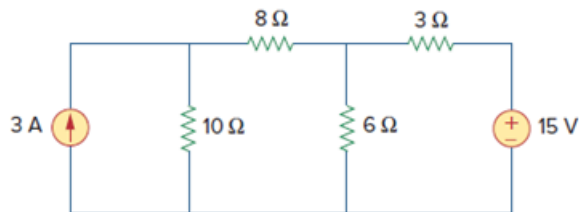


Problem

Referring to Fig. 4.91, use source transformation to determine the current and power absorbed by the $8\text{-}\Omega$ resistor.

Figure. 4.91:



Step-by-step solution

Step 1 of 5

Refer to figure 4.91 given in the textbook.

Apply Source transformation technique to 3-A source and $10\text{ }\Omega$ resistor; and apply the same to 15 V source and $3\text{ }\Omega$ resistor as shown in figure 1.

Replace the combination of 3-A source and $10\text{ }\Omega$ resistor with a voltage source of $(3 \times 10) = 30\text{ V}$ and the combination of 15 V source and $3\text{ }\Omega$ resistor with a current source of $\left(\frac{15}{3}\right) = 5\text{ A}$ as shown in figure 1.

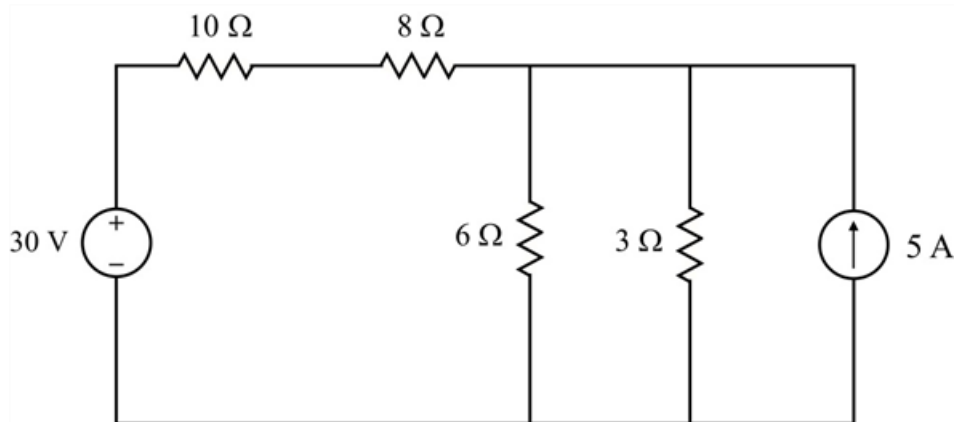


Figure 1

Step 2 of 5

Consider the circuit shown in figure 1.

The resistors $3\text{ }\Omega$ and $6\text{ }\Omega$ are in parallel to each other.

$$(3\text{ }\Omega \parallel 6\text{ }\Omega) = \frac{3 \times 6}{3 + 6}$$

$$(3\text{ }\Omega \parallel 6\text{ }\Omega) = \frac{18}{9}$$

$$(3\text{ }\Omega \parallel 6\text{ }\Omega) = 2\text{ }\Omega$$

Step 3 of 5

Redraw the circuit by replacing the resistances $3\ \Omega$ and $6\ \Omega$ with $2\ \Omega$ as shown in figure 2.

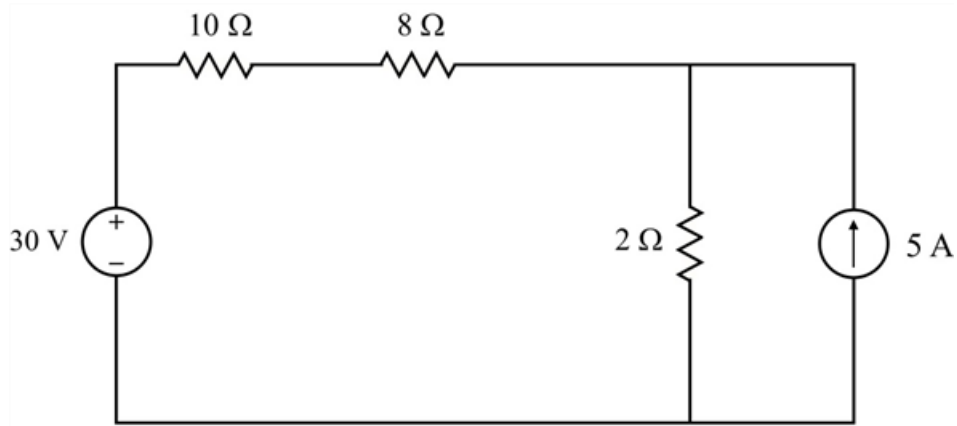


Figure 2

Step 4 of 5

Consider the circuit shown in figure 2.

Apply source transformation technique to the combination of 5 A source and $2\ \Omega$ resistor and replace the current source by a voltage source of $5 \times 2 = 10\ \text{V}$ as shown in figure 3.

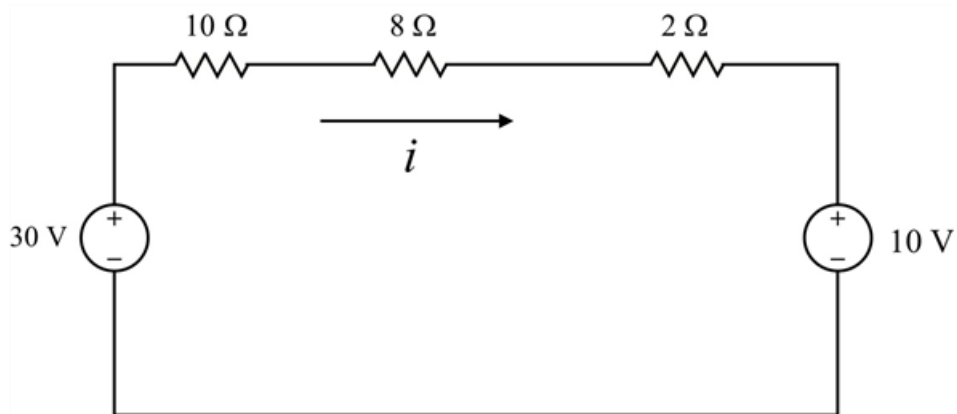


Figure 3

Step 5 of 5

Consider the circuit shown in figure 3.

Apply Kirchhoff's voltage law.

$$30 - 10i - 8i - 2i - 10 = 0$$

$$20i = 20$$

$$i = 1\ \text{A}$$

Assume that the power absorbed by the $8\ \Omega$ resistor is $P_{8\ \Omega}$.

The power absorbed by the $8\ \Omega$ resistor is,

$$P_{8\ \Omega} = i^2 \times 8$$

Substitute 1 for i .

$$\begin{aligned} P_{8\ \Omega} &= 1^2 \times 8 \\ &= 8\ \text{W} \end{aligned}$$

Therefore, the power absorbed by the $8\ \Omega$ resistor is 8 W.