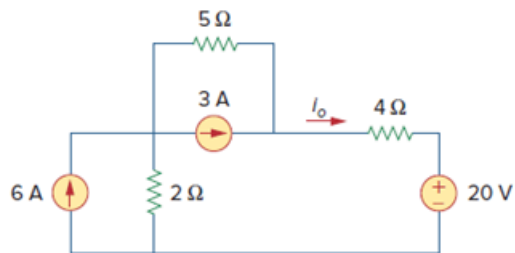


Problem

Use source transformation to find i_o in the circuit of Fig. 4.94.


Figure 4.94:



Step-by-step solution

Step 1 of 1

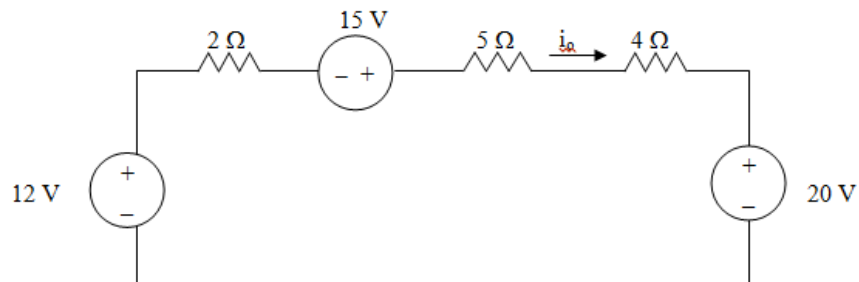Transforming the current sources gives the circuit below.



$$-12 + 11i_o - 15 + 20 = 0 \text{ or } 11i_o = 7 \text{ or } i_o = \mathbf{636.4 \text{ mA}}$$