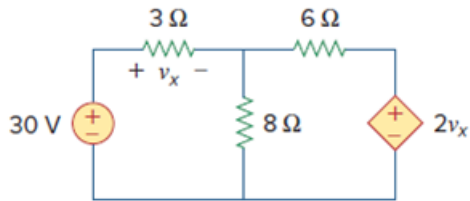


Problem

Determine v_x in the circuit of Fig. 4.99 using source transformation.

Figure 4.99:



Step-by-step solution

Step 1 of 7

Refer to Figure 4.99 in the textbook.

The independent source cannot be transformed as the dependent parameter v_x would be lost due to the source transformation operation.

Only the dependant source is transformed to determine the output.

Convert the dependent source in series with a resistance to the current source with a parallel resistance using source transformation as shown in Figure 1.

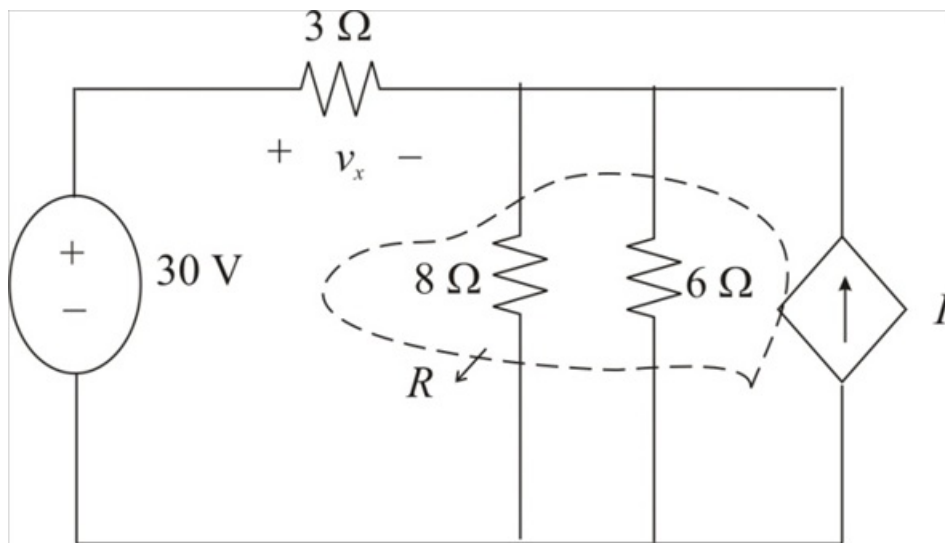


Figure 1

Step 2 of 7

Calculate the value of the current, I .

$$I = \frac{2v_x}{6}$$

Therefore, the value of the current I is $\frac{2v_x}{6}$.

Step 3 of 7

Calculate the equivalent resistance of the parallel connected resistors.

$$\begin{aligned} R &= 6 \parallel 8 \\ &= \frac{(6)(8)}{6+8} \\ &= \frac{48}{14} \\ &= \frac{24}{7} \Omega \end{aligned}$$

Therefore, the value of the resistance R is $\frac{24}{7} \Omega$.

Step 4 of 7

Redraw the circuit diagram as shown in Figure 2.

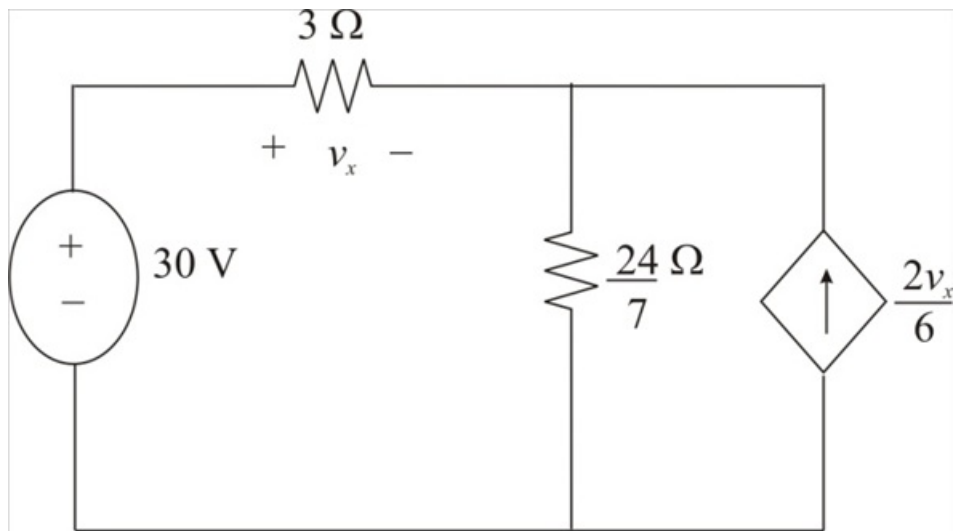


Figure 2

Step 5 of 7

Convert the dependent current source to voltage source using source transformation as shown in Figure 3.

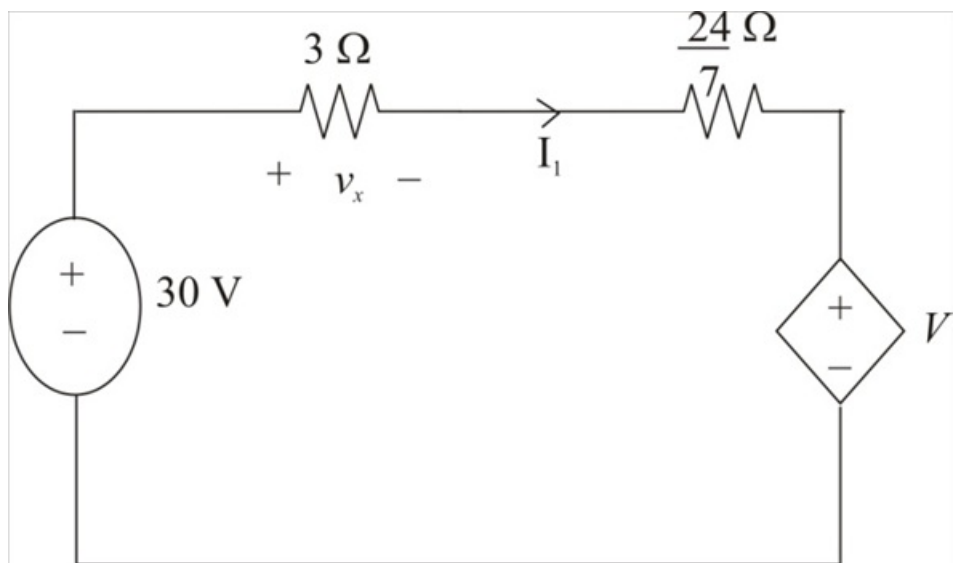


Figure 3

Step 6 of 7

Calculate the value of the dependent voltage source V .

$$V = I \left(\frac{24}{7} \right)$$

Substitute $\frac{2v_x}{6}$ for I .

$$\begin{aligned} V &= \left(\frac{2v_x}{6} \right) \left(\frac{24}{7} \right) \\ &= \frac{8v_x}{7} \end{aligned}$$

Therefore, the value of the dependent voltage source is $\frac{8v_x}{7}$.

Consider the expression from the voltage, v_x .

$$v_x = I_1 (3)$$

$$I_1 = \frac{v_x}{3}$$

Therefore, the expression for the current I_1 is, $\frac{v_x}{3}$.

Step 7 of 7

Apply Kirchhoff's Voltage Law in the Loop.

$$-30 + I_1 \left(3 + \frac{24}{7} \right) + \frac{8v_x}{7} = 0 \quad \text{Substitute } \frac{v_x}{3} \text{ for } I_1 \text{ in the equation.}$$

$$-30 + \left(\frac{v_x}{3} \right) \left(3 + \frac{24}{7} \right) + \frac{8v_x}{7} = 0$$

$$-30 + \left(\frac{v_x}{3} \right) \left(\frac{21 + 24}{7} \right) + \frac{8v_x}{7} = 0$$

$$-30 + \left(\frac{v_x}{3} \right) \left(\frac{45}{7} \right) + \frac{8v_x}{7} = 0$$

$$-30 + \frac{15v_x}{7} + \frac{8v_x}{7} = 0$$

$$-30 + \frac{23v_x}{7} = 0$$

$$\frac{-210 + 23v_x}{7} = 0$$

$$-210 + 23v_x = 0$$

$$23v_x = 210$$

$$\begin{aligned} v_x &= \frac{210}{23} \\ &= 9.13 \text{ V} \end{aligned}$$

Therefore, the value of the voltage v_x is 9.13 V.