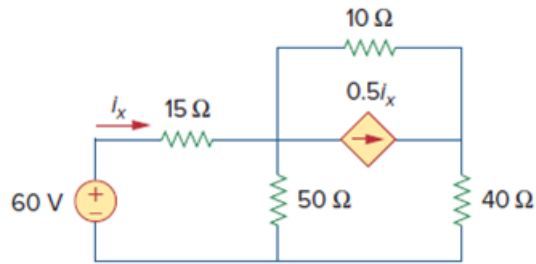


Problem

Use source transformation to find i_x in the circuit of Fig. 4.100.

Figure. 4.100:



Step-by-step solution

Step 1 of 7

As shown in Fig-(a), we transform the dependent current source to a voltage source,

Step 2 of 7


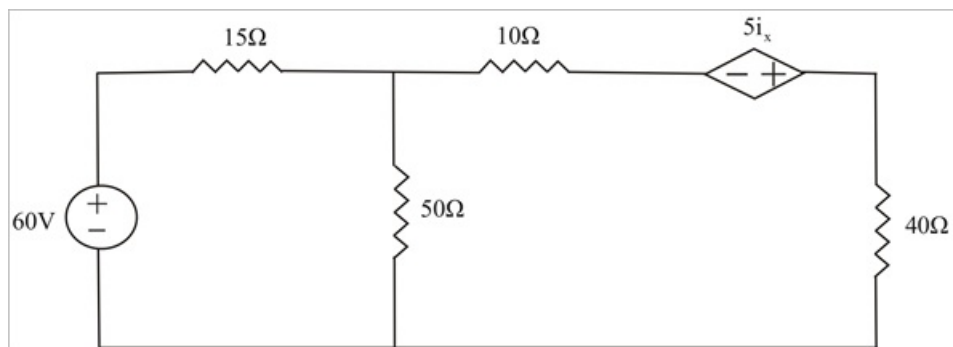


Fig-(a)

Step 3 of 7

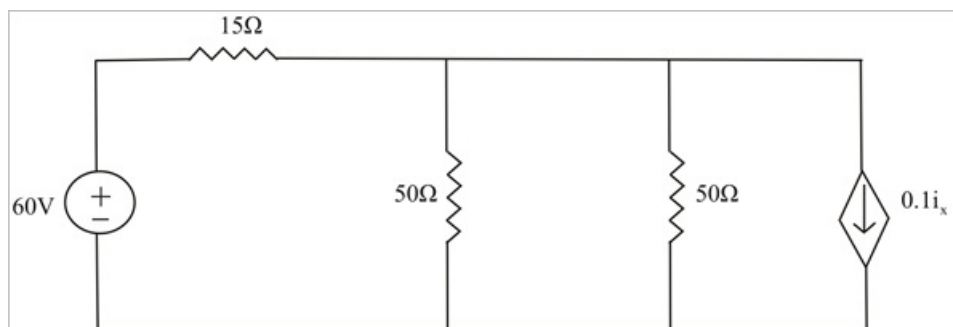As shown in Fig-(b), we transform the dependent voltage source to a current source.



Step 4 of 7

Fig-(b)

Step 5 of 7

$$50\Omega \parallel 50\Omega = \frac{50 \times 50}{50 + 50}$$

$$50\Omega \parallel 50\Omega = \frac{2500}{100}$$

$$50\Omega \parallel 50\Omega = 25\Omega$$

Step 6 of 7

As shown in Fig-(c), we transform the dependent current source to a voltage source,

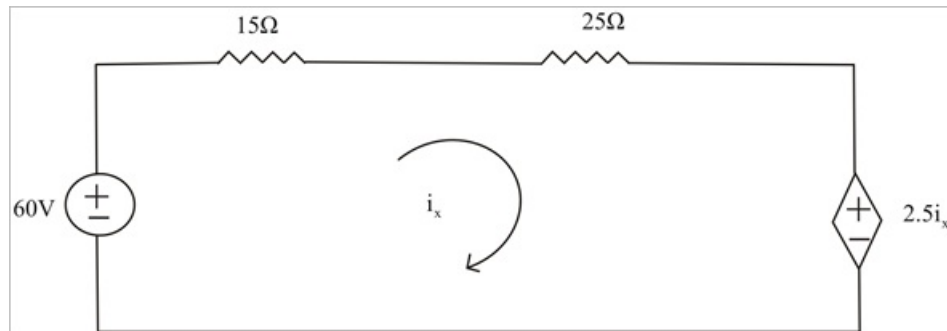


Fig-(c)

Step 7 of 7

Applying KVL in Fig-(c),

$$-60 + 40i_x - 2.5i_x = 0$$

$$-60 = -37.5i_x$$

$$\therefore \boxed{i_x = 1.6 \text{ A}}$$