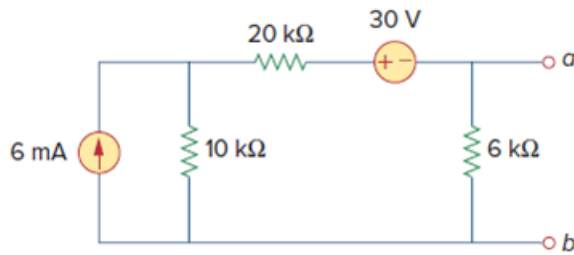


Problem

Find the Norton equivalent with respect to terminals a - b in the circuit shown in Fig. 4.104.

Figure. 4.104:



Step-by-step solution

Step 1 of 6

Refer to circuit diagram in Figure 4.104 in the text book.

To calculate the short circuit current, short circuit the terminals a and b . The modified circuit is shown in Figure 1.

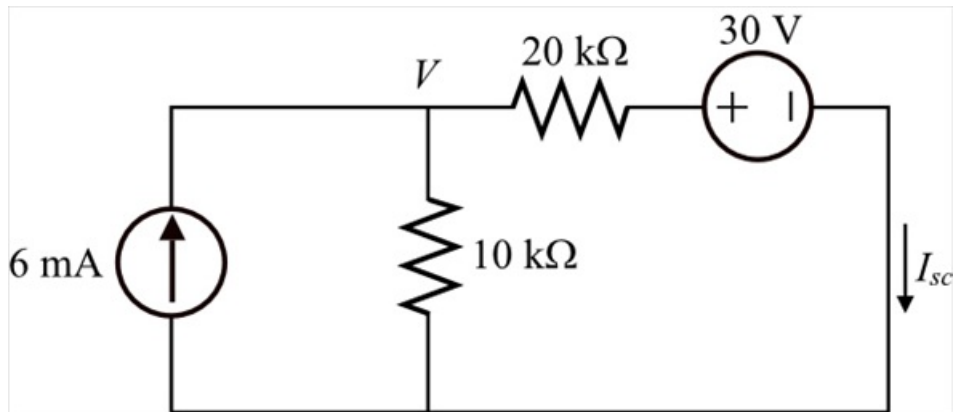


Figure 1

Step 2 of 6

Apply Kirchhoff's Current Law at node 1.

$$\frac{V}{10 \text{ k}} + \frac{V - 30}{20 \text{ k}} - 6 \text{ m} = 0$$

$$\frac{2V + V - 30 - 120}{20 \text{ k}} = 0$$

$$2V + V - 30 - 120 = 0$$

$$3V - 150 = 0$$

$$3V = 150$$

$$V = \frac{150}{3}$$

$$V = 50 \text{ V}$$

Step 3 of 6

Calculate the value of the Norton's current I_N .

$$I_N = \frac{V - 30}{20 \text{ k}}$$

Substitute 50 V for V .

$$\begin{aligned} I_N &= \frac{50 - 30}{20 \text{ k}} \\ &= \frac{20}{20 \text{ k}} \\ &= 1 \text{ mA} \end{aligned}$$

Therefore, the value of the Norton's current I_N is 1 mA.

Step 4 of 6

To calculate the Thevenin's resistance, open circuit the current source and short circuit the voltage source. The modified circuit is shown in Figure 2.

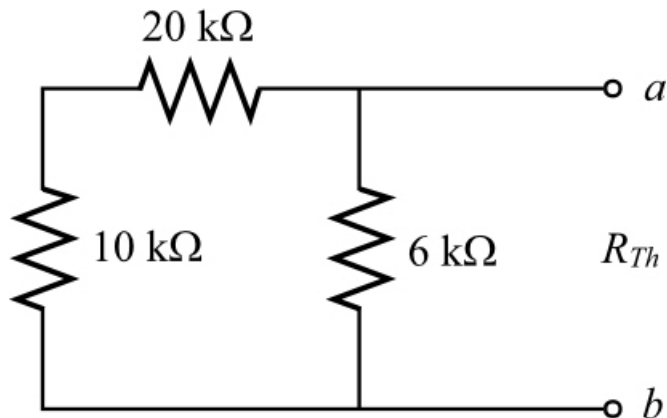


Figure 2

[Comments \(2\)](#)



Anonymous

where did the 6k come from?



Anonymous

its in the problem...

Step 5 of 6

Calculate the value of the Norton's resistance R_N .

$$\begin{aligned} R_N &= (10 \text{ k}\Omega + 20 \text{ k}\Omega) \parallel (6 \text{ k}\Omega) \\ &= (30 \text{ k}\Omega) \parallel (6 \text{ k}\Omega) \\ &= \frac{(30 \text{ k}\Omega)(6 \text{ k}\Omega)}{30 \text{ k}\Omega + 6 \text{ k}\Omega} \\ &= \frac{180 \text{ k}\Omega}{36} \\ &= 5 \text{ k}\Omega \end{aligned}$$

Therefore, the value of the Norton's resistance R_N is 5 kΩ.

Step 6 of 6

Draw the Norton's equivalent circuit diagram as shown in Figure 3.

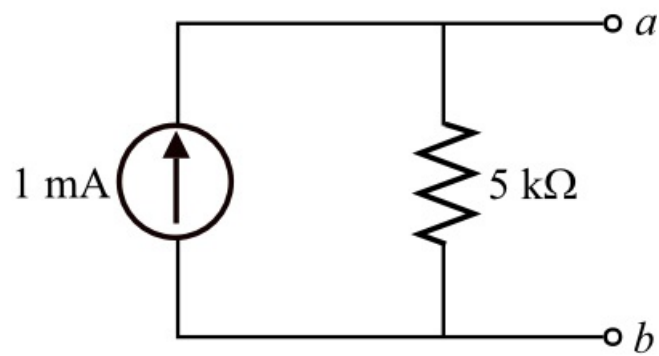


Figure 3

Therefore, the Norton's equivalent circuit is shown in Figure 3.