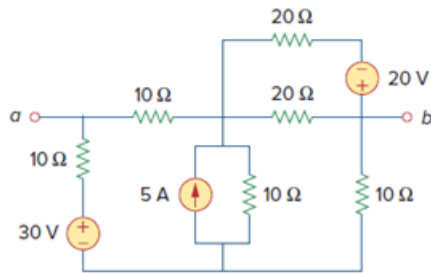


Problem

For the circuit in Fig. 4.109, find the Thevenin equivalent between terminals a and b .

Figure 4.109:



Step-by-step solution

Step 1 of 10

Refer to the Figure 4.109 in the text book.

Draw the circuit diagram to determine the Thevenin voltage.

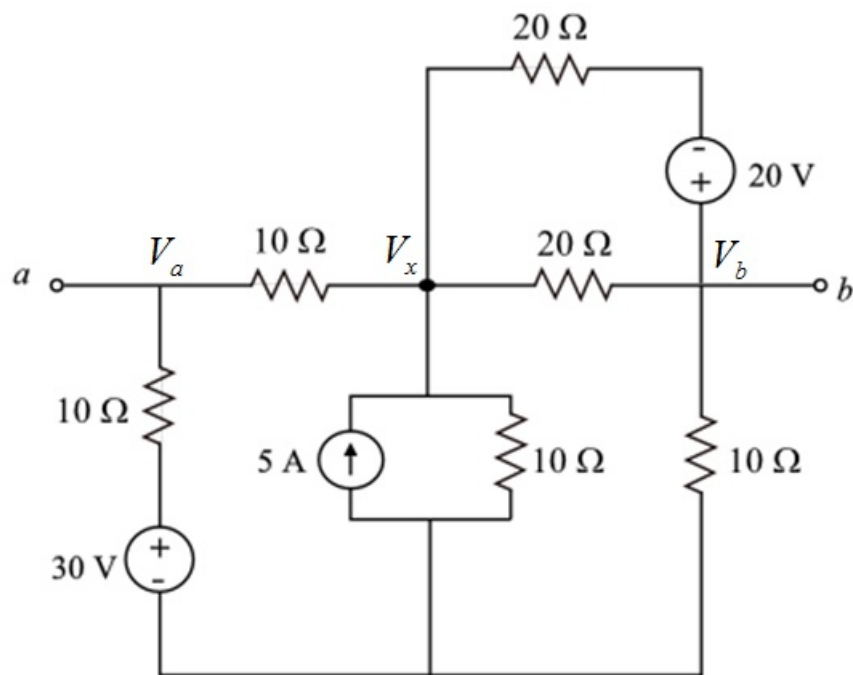


Figure 1

Step 2 of 10

Apply Kirchhoff's current law at node V_a .

$$\frac{V_a - 30}{10} + \frac{V_a - V_x}{10} = 0$$

$$\frac{V_a - 30 + V_a - V_x}{10} = 0$$

$$2V_a - V_x = 30 \dots\dots (1)$$

Apply Kirchhoff's current law at node V_b .

$$\frac{V_b - 20 - V_x}{20} + \frac{V_b}{10} + \frac{V_b - V_x}{20} = 0$$

$$\frac{V_b - 20 - V_x + 2V_b + V_b - V_x}{20} = 0$$

$$4V_b - 2V_x = 20 \dots\dots (2)$$

Apply Kirchhoff's current law at node V_x .

$$\frac{V_x - V_a}{10} + \frac{V_x}{10} - 5 + \frac{V_x - V_b}{20} + \frac{V_x + 20 - V_b}{20} = 0$$

$$\frac{2(V_x - V_a) + 2V_x - 100 + (V_x - V_b) + (V_x + 20 - V_b)}{20} = 0$$

$$2V_x - 2V_a + 2V_x - 100 + V_x - V_b + V_x + 20 - V_b = 0$$

$$-2V_a - 2V_b + 6V_x = 80 \dots\dots (3)$$

Step 3 of 10

Solve equations (1), (2) and (3).

$$V_a = 30 \text{ V}$$

$$V_b = 20 \text{ V}$$

$$V_x = 30 \text{ V}$$

Determine the value of Thevenin voltage.

$$V_{TH} = V_a - V_b$$

Substitute 30 V for V_a and 20 V for V_b in the equation.

$$V_{TH} = 30 \text{ V} - 20 \text{ V}$$

$$= 10 \text{ V}$$

Thus, the value of Thevenin voltage, V_{TH} is 10 V .

Step 4 of 10

Draw the circuit diagram to determine the Thevenin resistance.

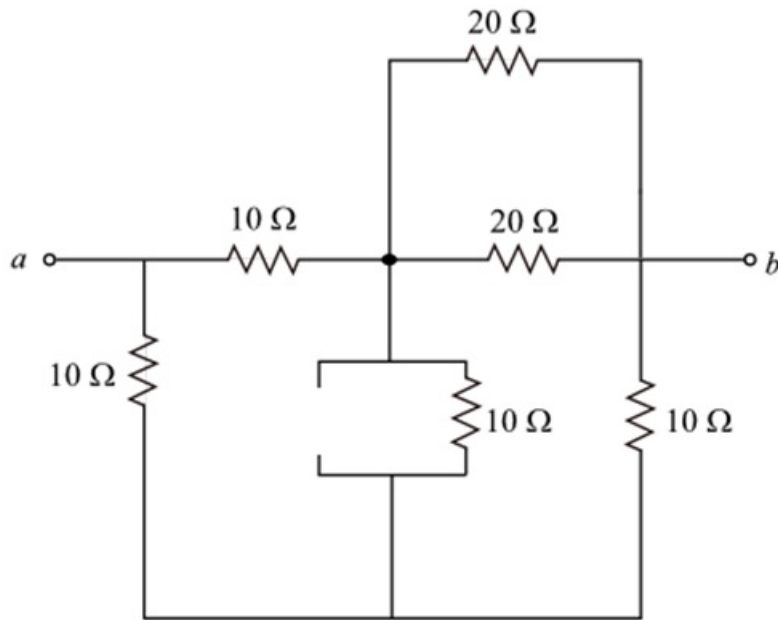


Figure 2

Step 5 of 10

In Figure 2, the resistors 20Ω and 20Ω are in parallel.

$$\begin{aligned} (20\Omega \parallel 20\Omega) &= \frac{(20\Omega)(20\Omega)}{(20\Omega) + (20\Omega)} \\ &= \frac{20\Omega}{2} \\ &= 10\Omega \end{aligned}$$

The simplified circuit diagram is shown in Figure 3.

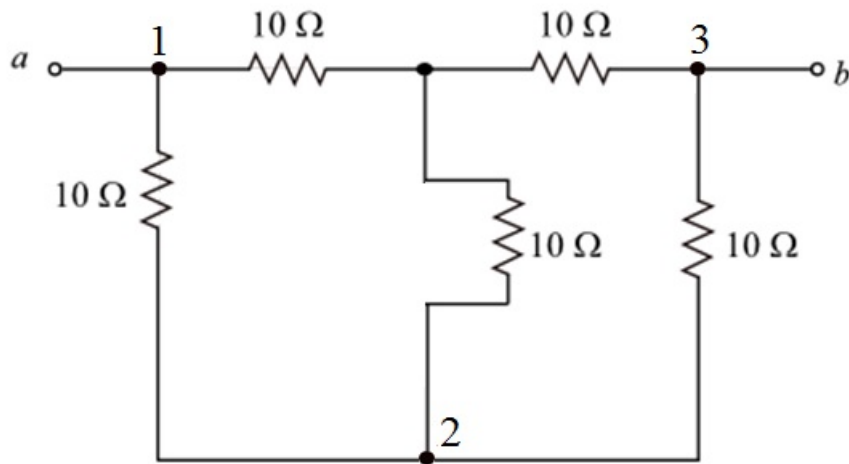


Figure 3

Step 6 of 10

Convert star network to delta network in Figure 3.

Find the resistance in between node-1 and node-2.

$$\begin{aligned} R_a &= \frac{(10\Omega)(10\Omega) + (10\Omega)(10\Omega) + (10\Omega)(10\Omega)}{(10\Omega)} \\ &= \frac{3(10\Omega)(10\Omega)}{(10\Omega)} \\ &= 30\Omega \end{aligned}$$

Find the resistance in between node-2 and node-3.

$$\begin{aligned} R_b &= \frac{(10\Omega)(10\Omega) + (10\Omega)(10\Omega) + (10\Omega)(10\Omega)}{(10\Omega)} \\ &= \frac{3(10\Omega)(10\Omega)}{(10\Omega)} \\ &= 30\Omega \end{aligned}$$

Find the resistance in between node-3 and node-1.

$$\begin{aligned} R_c &= \frac{(10\Omega)(10\Omega) + (10\Omega)(10\Omega) + (10\Omega)(10\Omega)}{(10\Omega)} \\ &= \frac{3(10\Omega)(10\Omega)}{(10\Omega)} \\ &= 30\Omega \end{aligned}$$

Step 7 of 10

The simplified circuit diagram is shown in Figure 4.

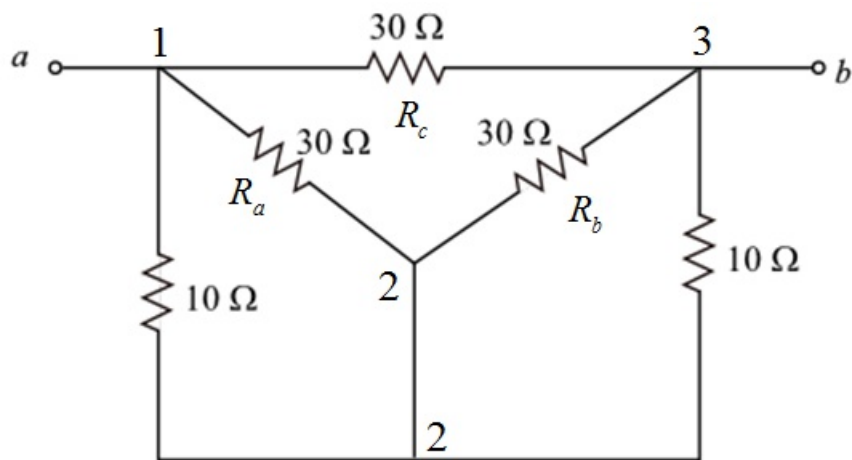


Figure 4

Step 8 of 10

In Figure 4, the resistors 10Ω and 30Ω are in parallel.

$$10\Omega \parallel 30\Omega = \frac{(10\Omega)(30\Omega)}{10\Omega + 30\Omega} \\ = 7.5\Omega$$

Draw the following modified circuit diagram.

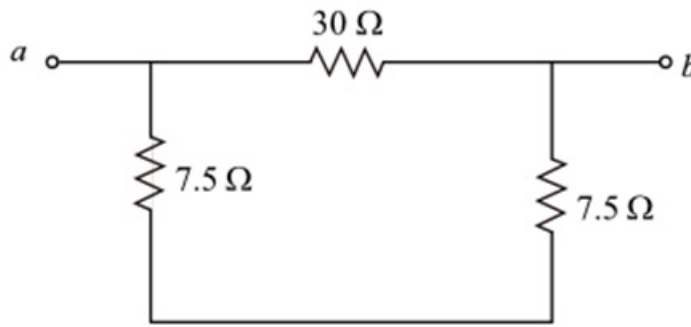


Figure 5

Step 9 of 10

Determine the value of Thevenin's resistance.

$$R_{TH} = R_{ab} \\ = (7.5\Omega + 7.5\Omega) \parallel 30\Omega \\ = 15\Omega \parallel 30\Omega \\ = \frac{(15\Omega)(30\Omega)}{15\Omega + 30\Omega}$$

$$R_{TH} = 10\Omega$$

Thus, the value of Thevenin resistance, R_{TH} is 10Ω .

Step 10 of 10

Draw the Thevenin equivalent circuit.

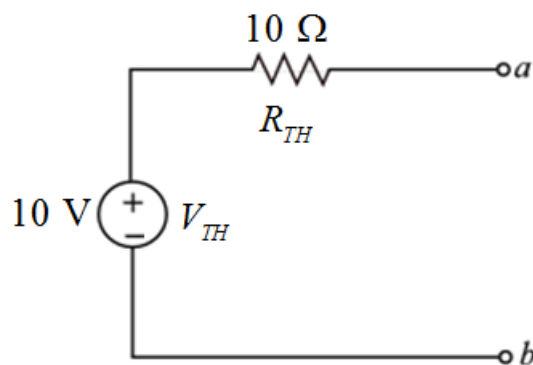


Figure 6

Thus, the required Thevenin equivalent circuit is sketched as shown in Figure 6.