


Problem

For the circuit in Fig. 4.111, obtain the Thevenin equivalent as seen from terminals:

(a) $a-b$

(b) $b-c$

Figure 4.111:

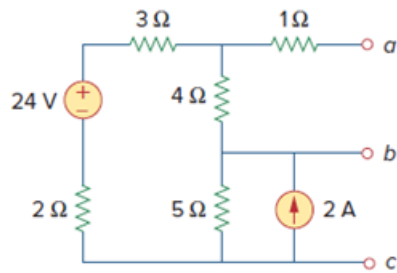

Step-by-step solution

Step 1 of 7

(a)

For R_{TH} , consider the circuit in Fig-(a).

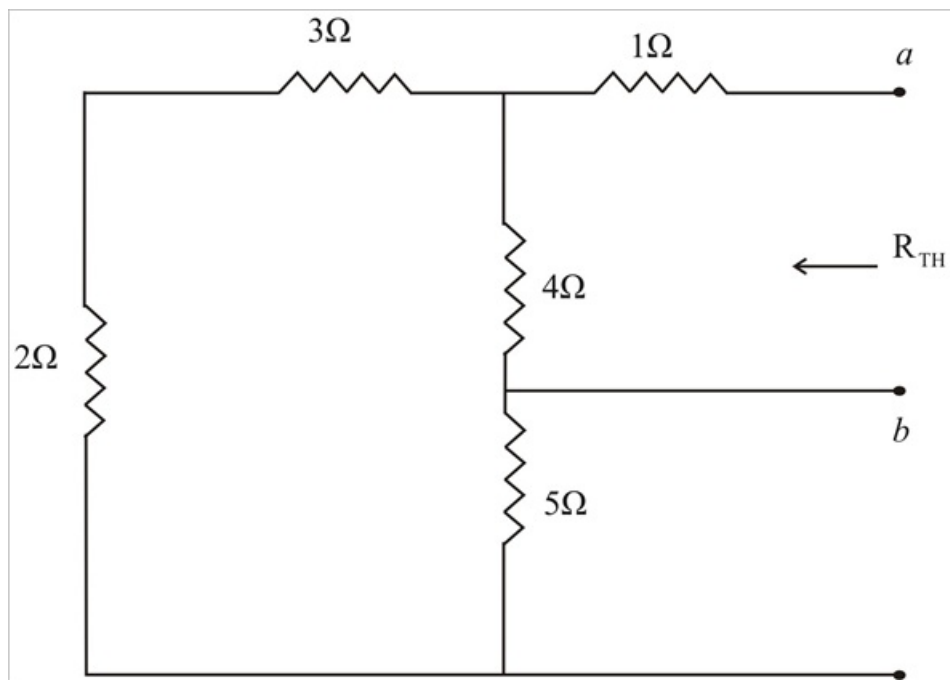


Fig-(a)

Step 2 of 7

$$R_{Th} = 1\Omega + (4\Omega \parallel (2\Omega + 3\Omega + 5\Omega))$$

$$R_{Th} = 1 + \frac{4 \times 10}{4 + 10}$$

$$R_{Th} = 1 + \frac{40}{14}$$

$$R_{Th} = 1 + 2.857$$

$$R_{Th} = 3.857\Omega$$

Step 3 of 7

For V_{Th} , Consider the circuit in Fig-(b).

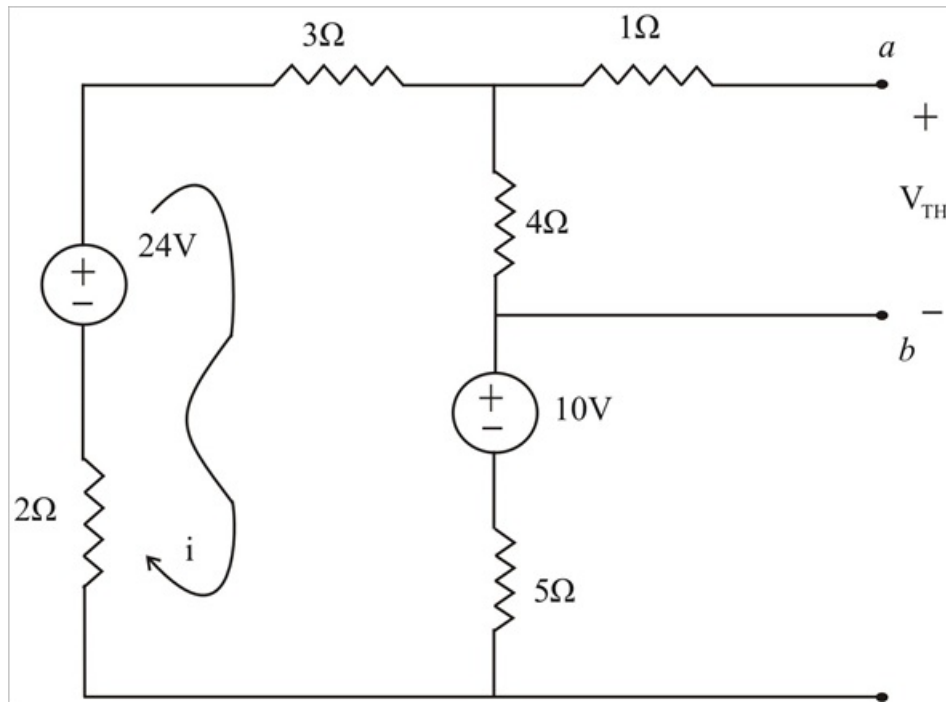


Fig-(b)

Step 4 of 7

Applying KVL gives,

$$10 - 24 + i(3 + 4 + 5 + 2) = 0$$

$$-14 + i(14) = 0$$

$$i = 1\text{A}$$

Therefore,

$$V_{Th} = 4 \times i$$

$$V_{Th} = 4 \times 1$$

$$V_{Th} = 4\text{V}$$

Step 5 of 7

(b)

For R_{Th} , consider the circuit in Fig-(c).

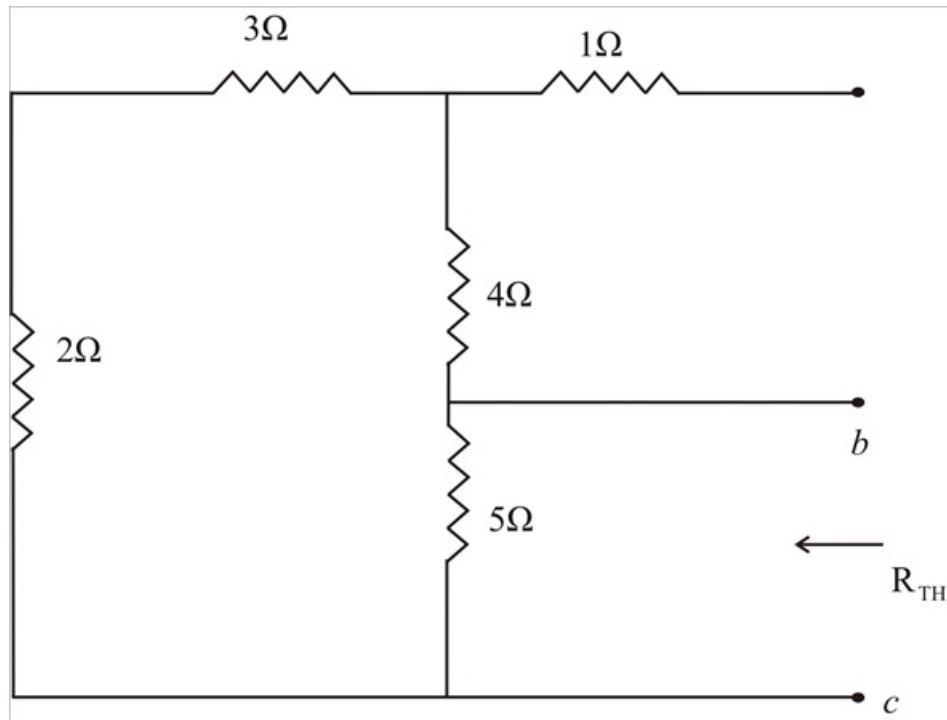


Fig-(c)

Step 6 of 7

$$R_{Th} = 5\Omega \parallel (2\Omega + 3\Omega + 4\Omega)$$

$$R_{Th} = \frac{5 \times 9}{5 + 9}$$

$$R_{Th} = 3.21\Omega$$

Step 7 of 7

For V_{Th} , Consider the circuit in Fig-(d).

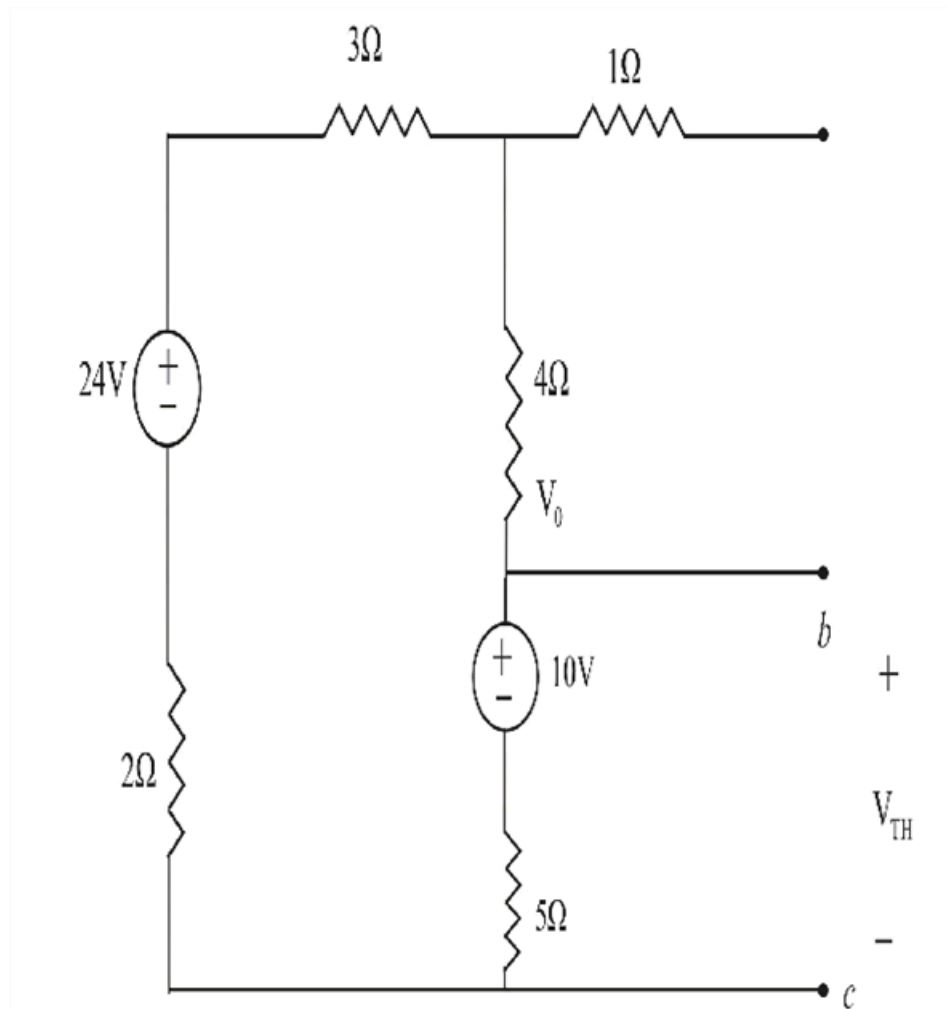


Fig-(d)

Applying KVL gives,

$$10 - 24 + i(3 + 4 + 5 + 2) = 0$$

$$-14 + i(14) = 0$$

$$i = 1A$$

Therefore,

$$V_{Th} = 10 + 5 \times i$$

$$V_{Th} = 10 + 5 \times 1$$

$$V_{Th} = 15V$$