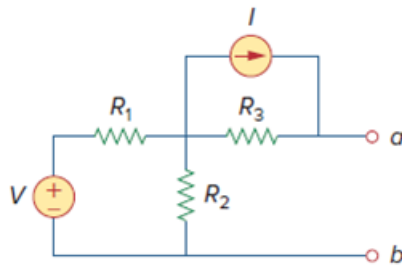


Problem

Find the Norton equivalent looking into terminals a - b of the circuit in Fig. 4.102. Let $V = 40\text{ V}$, $I = 3\text{ A}$, $R_1 = 10\ \Omega$, $R_2 = 40\ \Omega$, and $R_3 = 20\ \Omega$.

Figure. 4.102:



Step-by-step solution

Step 1 of 5

To find R_{Th} , Consider the circuit in Fig-(a).

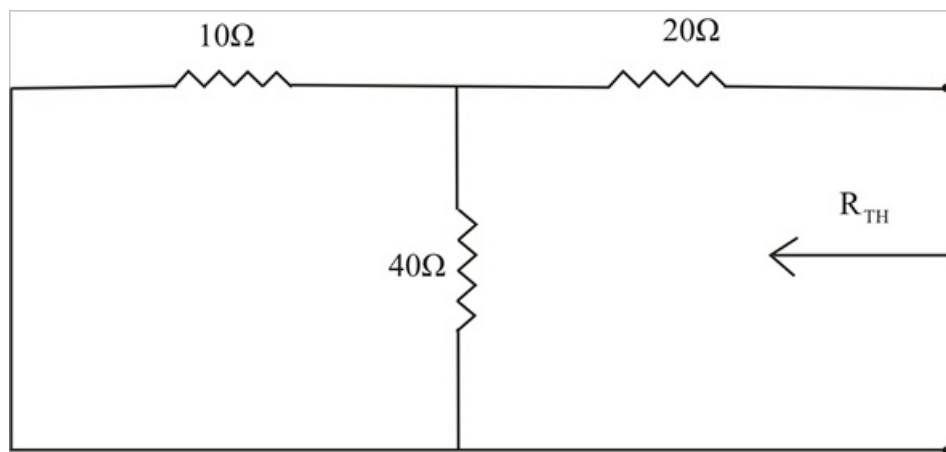


Fig-(a)

Step 2 of 5

$$R_N = 20 + (10 \parallel 40)$$

$$R_N = 20 + \frac{10 \times 40}{10 + 40}$$

$$R_N = 20 + \frac{400}{50}$$

$$R_N = 20 + 8$$

$$R_N = 28\ \Omega$$

Step 3 of 5

To find I_N , consider the Fig-(b)

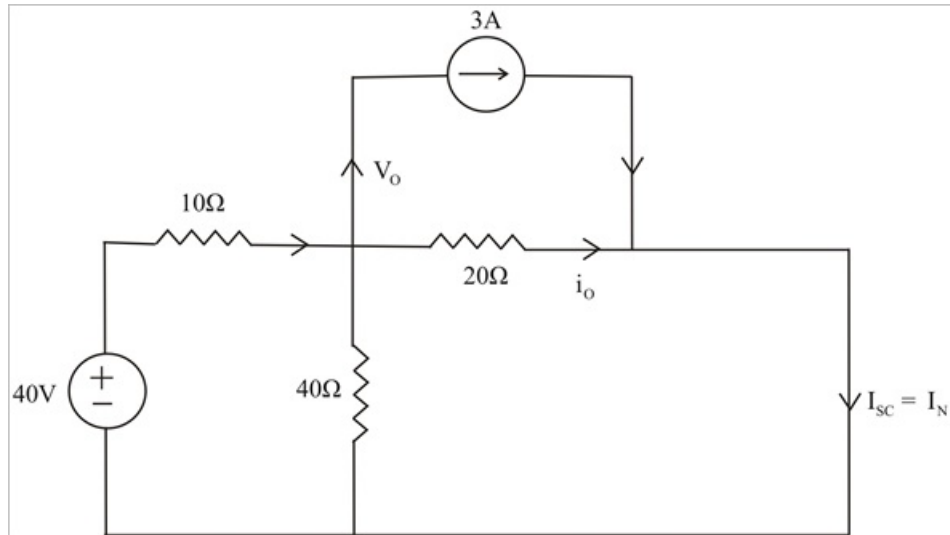


Fig-(b)

Step 4 of 5

At the node,

$$\frac{(40 - V_o)}{10} = 3 + \left(\frac{V_o}{40}\right) + \left(\frac{V_o}{20}\right)$$

$$160 - 4V_o = 120 + V_o + 2V_o$$

$$40 = 7V_o$$

$$V_o = \frac{40}{7} \text{ V}$$

Therefore,

$$i_o = \frac{V_o}{20}$$

$$i_o = \frac{\frac{40}{7}}{20}$$

$$i_o = \frac{2}{7} \text{ A}$$

But,

$$I_N = I_{SC} = i_o + 3$$

$$I_N = \frac{2}{7} + 3$$

$$I_N = \frac{23}{7}$$

$$I_N = 3.286 \text{ A}$$

Step 5 of 5

Therefore, the Norton equivalent circuit as shown in below;

