


Problem

Given the circuit in Fig. 4.117, obtain the Norton equivalent as viewed from terminals:

(a) a - b

(b) c - d

Figure 4.117

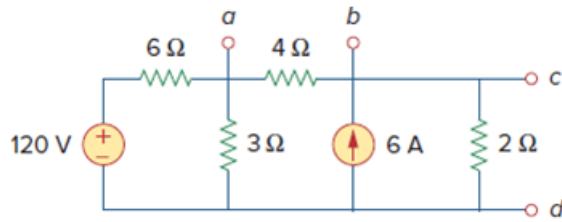

Step-by-step solution

Step 1 of 6

(a)

Find Norton equivalent circuit viewed from a and b terminals.

Find Norton resistance by short circuit the voltage source and open circuit the current source.

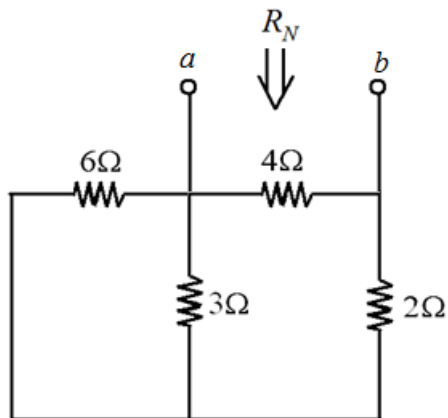


Figure 1

Norton resistance is,

$$R_N = 4\Omega \parallel (2\Omega + (6\Omega \parallel 3\Omega))$$

$$R_N = 4 \parallel \left(2 + \left(\frac{6 \times 3}{6 + 3} \right) \right)$$

$$R_N = 4 \parallel (2 + 2)$$

$$R_N = \frac{4 \times 4}{4 + 4}$$

Norton resistance viewed from terminals a and b is, $R_N = 2\Omega$.

Step 2 of 6

Find Norton current.

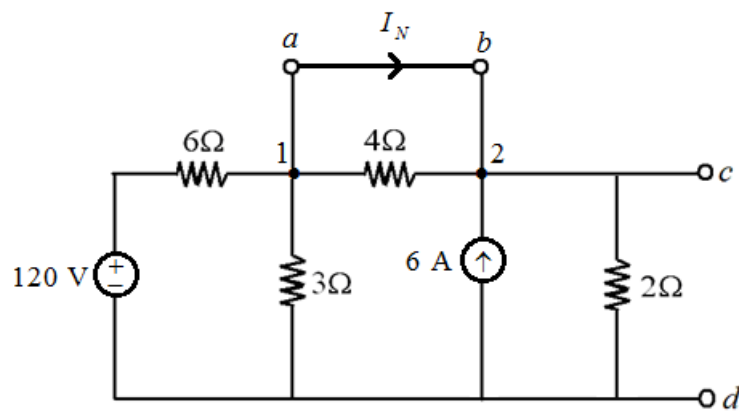


Figure 2

Observe that both

Apply KCL at node 1.

$$\frac{v_1}{3} + \frac{v_1 - 120}{6} + I_N = 0 \dots\dots (1)$$

Observe that nodes 1 and 2 are short circuited. Thus,

$$v_1 = v_2$$

Apply KCL at node 2.

$$I_N + 6 = \frac{v_2}{2}$$

Substitute v_1 for v_2 in the equation.

$$I_N = \frac{v_1}{2} - 6$$

Substitute $\frac{v_1}{2} - 6$ for I_N in equation (1).

$$\frac{v_1}{3} + \frac{v_1 - 120}{6} + \frac{v_1}{2} - 6 = 0$$

$$v_1 \left(\frac{1}{3} + \frac{1}{6} + \frac{1}{2} \right) = 6 + \frac{120}{6}$$

$$v_1 \left(\frac{2+1+3}{6} \right) = 6 + 20$$

$$v_1 = 26 \text{ V}$$

Step 3 of 6

Substitute 26 V for v_1 in equation (1).

$$\frac{v_1}{3} + \frac{v_1 - 120}{6} + I_N = 0$$

Substitute 26 for v_1 in the equation.

$$\frac{26}{3} + \frac{26 - 120}{6} + I_N = 0$$


$$I_N = 7 \text{ A}$$

Thus, Norton current viewed from terminals a and b is, $I_N = 7 \text{ A}$.


Step 4 of 6

(b)

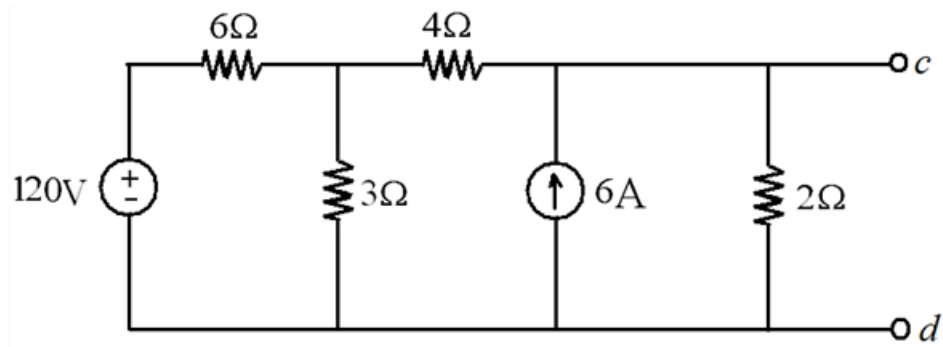Find the Norton equivalent viewed from terminals c and d.



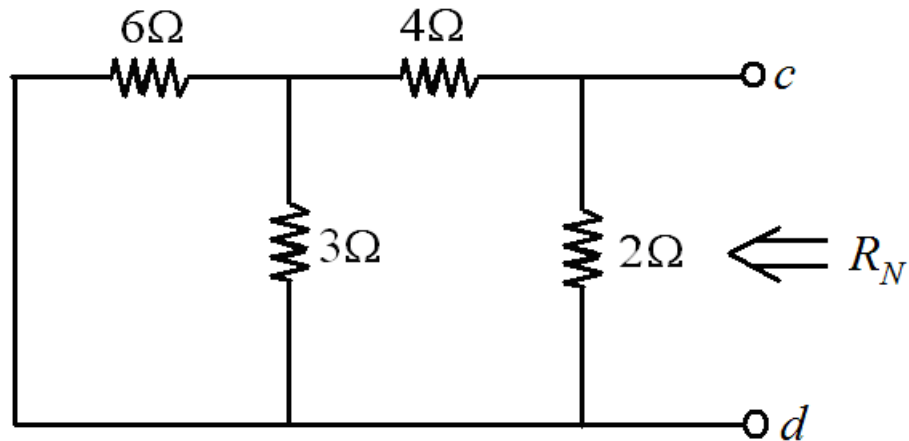Find the Norton resistance viewed from terminals c and d.



Norton resistance is,

$$R_N = [(6 \parallel 3) + 4] \parallel 2$$

$$R_N = [2 + 4] \parallel 2$$


$$R_N = 6 \parallel 2$$

$$R_N = \frac{6 \times 2}{6 + 2}$$


$$\boxed{R_N = 1.5\Omega}$$

Norton resistance viewed from terminals c and d is, $\boxed{R_N = 1.5\Omega}$.

Find Norton's current.

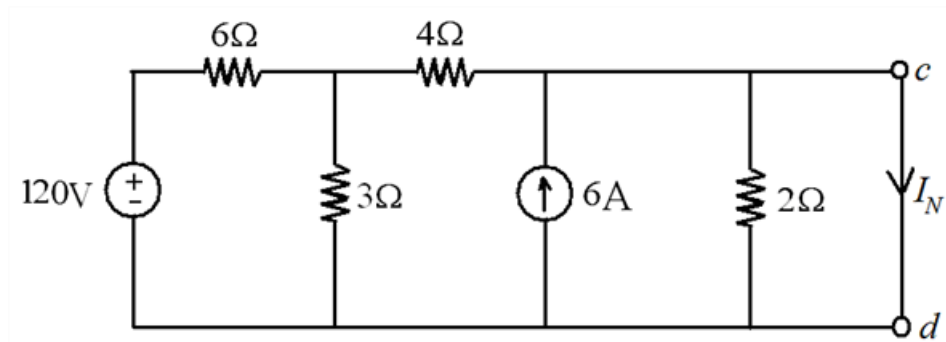

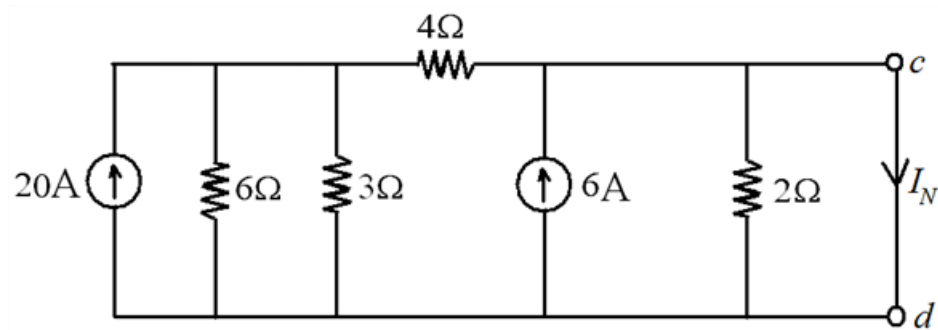Apply source transformation to convert the 120 V and 6Ω resistor into current source in parallel with the resistor.




In this 6Ω and 3Ω are in parallel

$$6\Omega \parallel 3\Omega = \frac{6 \times 3}{6 + 3}$$

$$6\Omega \parallel 3\Omega = 2\Omega$$

Replace the 6Ω and 3Ω with the equivalent 2Ω resistor.

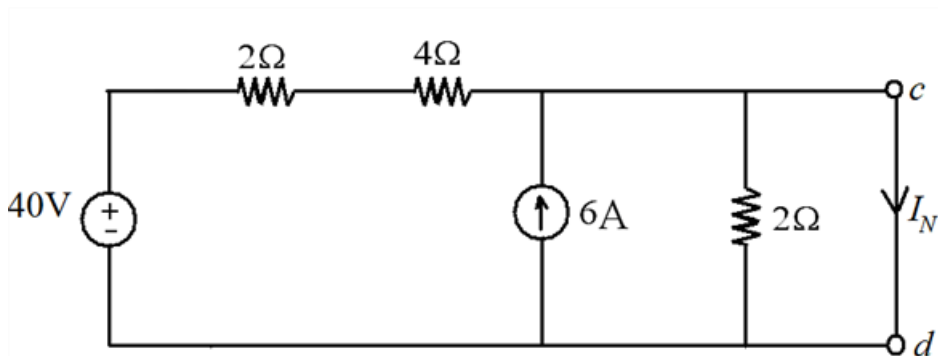Now, apply source transformation to convert the 20 A and the 2Ω resistor into voltage source in series with the resistor.




Resistors 2Ω and 4Ω are in series.

$$2\Omega + 4\Omega = 6\Omega$$

Replace the $2\ \Omega$ and $4\ \Omega$ with the equivalent $6\ \Omega$ resistor.

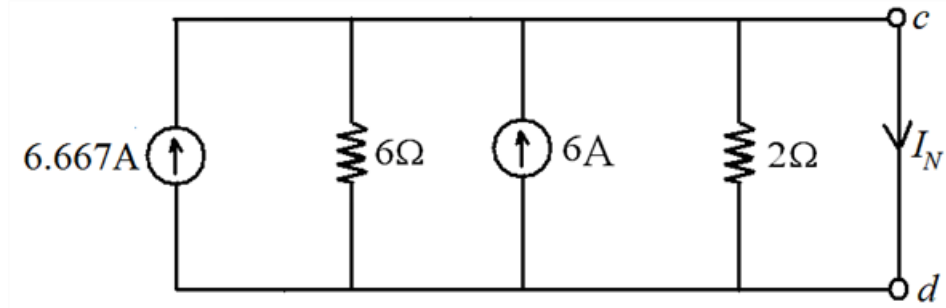Now, apply source transformation to convert the voltage source $40\ \text{V}$ and resistor $6\ \Omega$ into current source in parallel with the resistor.



From the circuit, due to short-circuit terminals across c and d , the total current generated from the sources flow through the short circuit terminals c and d . No current flow through $6\ \Omega$ and $2\ \Omega$ resistors.

$$I_N = 6 + 6.667$$

$$I_N = 12.667\text{A}$$