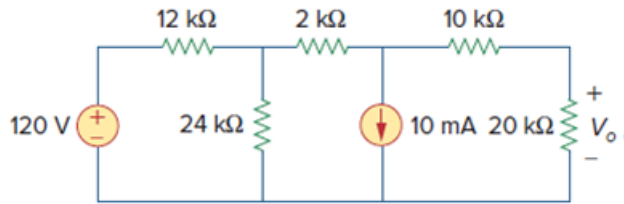


Problem

Use Norton's theorem to find V_o in the circuit of Fig. 4.122.

Figure 4.122:



Step-by-step solution

Step 1 of 8

Refer to circuit diagram in Figure 4.122 in the text book.

Disconnect the load resistance and short the output terminals to calculate the Norton's current.

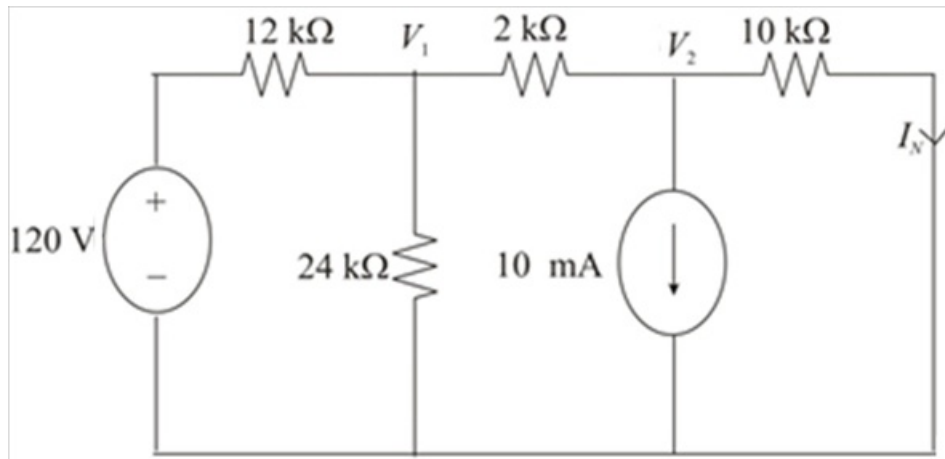


Figure 1

Step 2 of 8

Apply Kirchhoff's current law at node 1.

$$\frac{V_1 - 120}{12 \text{ k}} + \frac{V_1}{24 \text{ k}} + \frac{V_1 - V_2}{2 \text{ k}} = 0$$

$$\frac{2V_1 - 240 + V_1 + 12V_1 - 12V_2}{24 \text{ k}} = 0$$

$$15V_1 - 240 - 12V_2 = 0$$

$$15V_1 = 240 + 12V_2$$

$$V_1 = \frac{240 + 12V_2}{15}$$

$$V_1 = \frac{80 + 4V_2}{5} \dots\dots (1)$$

Step 3 of 8

Apply Kirchhoff's current law at node 2.

$$10 \text{ m} + \frac{V_2 - V_1}{2 \text{ k}} + \frac{V_2}{10 \text{ k}} = 0$$

$$\frac{100 + 5V_2 - 5V_1 + V_2}{10 \text{ k}} = 0$$

$$100 + 6V_2 - 5V_1 = 0$$

Substitute $\frac{80 + 4V_2}{5}$ for V_1 .

$$100 + 6V_2 - 5\left(\frac{80 + 4V_2}{5}\right) = 0$$

$$100 + 6V_2 - 80 - 4V_2 = 0$$

$$2V_2 + 20 = 0$$

$$2V_2 = -20$$

$$V_2 = -\frac{20}{2}$$

$$= -10 \text{ V}$$

Step 4 of 8

Calculate the value of the Norton's current, I_N .

$$I_N = \frac{V_2}{10 \text{ k}}$$

Substitute -10 V for V_2 .

$$I_N = \frac{-10 \text{ V}}{10 \text{ k}\Omega}$$

$$= -1 \text{ mA}$$

Therefore, the value of the Norton's current I_N is -1 mA.

Step 5 of 8

Set the value of the sources to zero to calculate the Norton's resistance.

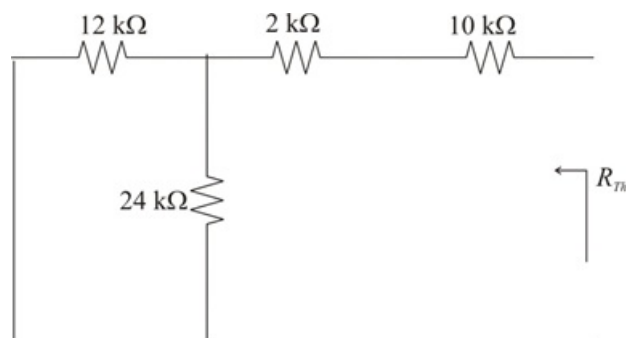


Figure 2

Step 6 of 8

Calculate the value of the Norton's resistance R_N .

$$\begin{aligned}R_N &= 10 \text{ k}\Omega + 2 \text{ k}\Omega + (12 \text{ k}\Omega) \parallel (24 \text{ k}\Omega) \\&= 12 \text{ k}\Omega + \frac{(12 \text{ k}\Omega)(24 \text{ k}\Omega)}{12 \text{ k}\Omega + 24 \text{ k}\Omega} \\&= 12 \text{ k}\Omega + 8 \text{ k}\Omega \\&= 20 \text{ k}\Omega\end{aligned}$$

Therefore, the value of the Norton's resistance R_N is $20 \text{ k}\Omega$.

Step 7 of 8

Draw the Norton's equivalent circuit diagram.

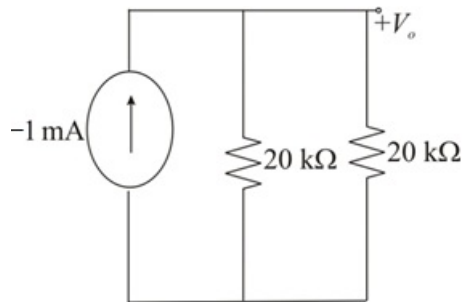


Figure 3

Step 8 of 8

Calculate the value of the voltage, V_o using current division rule.

$$\begin{aligned}V_o &= (-1 \text{ mA})(20 \text{ k}\Omega) \parallel (20 \text{ k}\Omega) \\&= (-1 \text{ mA}) \left(\frac{(20 \text{ k}\Omega)(20 \text{ k}\Omega)}{20 \text{ k}\Omega + 20 \text{ k}\Omega} \right) \\&= (-1 \text{ mA}) \left(\frac{400 \text{ k}\Omega}{40} \right) \\&= (-1 \text{ mA})(10 \text{ k}\Omega) \\&= -10 \text{ V}\end{aligned}$$

Therefore, the value of the voltage V_o is -10 V .